

- Introduction
- Puissance absorbée par une charge triphasée
- Puissance dans un système symétrique à charge équilibrée
- Conclusion

Electrotechnique II

Hello and welcome to this lesson dedicated to three-phase electric power. We will define what the instantaneous three-phase power is in a symmetric system and will study using two examples the power with a balanced charge, or rather, the powers in a balanced charge.

Notes

Summary



0m 04s

4 types de puissance : $p(t) = \text{puissance instantanée}$

$P = \text{puissance active} = \overline{p(t)} = UI \cos \varphi \text{ [W]}$

$Q = \text{'' réactive} = UI \sin \varphi \text{ [Var]}$

$S = \text{'' apparente} = UI \text{ [VA]}$

Pan symétrique : Puissance totale $\equiv \sum 3 \times P_{\text{phase}}$

Electrotechnique II

Notes

To define the instantaneous power within a symmetric three-phase system, I would like to start with a short reminder of the different types of power that exist. We can count four types of powers, starting with the first type, if one may say, of power. The instantaneous power, which is the power depending on time. We have then defined the active power by the letter P. This active power, we have seen that, by definition, it is the average of the instantaneous power and it is also equal to $U \cdot I \cdot \cos(\varphi)$ and all this is measures in watts. Then, we defined another type of power that defines the round trip of the target non-convertible power called reactive power, and is by definition equal to $U \cdot I \cdot \sin(\varphi)$, written in reactive volt-amperes. Last but not least, the power called apparent power is equal to $U \cdot I$ and is written in volt-amperes. Now, how do we solve the power problems in a three-phase system ? We have seen that by symmetry, all these values are equal in each branch. We also know that the total power in a system is simply the sum of these powers. We can then say that by symmetry we can write the total power as equal to the sum of all three powers in each phase.

Summary



$$p = u_{ux} \cdot i_{ux} + u_{vy} \cdot i_{vy} + u_{wz} \cdot i_{wz}$$

$$p = u_{ux} I_{ux} \cos \varphi + u_{vy} I_{vy} \cos \varphi + u_{wz} I_{wz} \cos \varphi$$

$$= 3 u_{ph} \cdot I_{ph} \cdot \cos \varphi$$

Electrotechnique II

We will be able to write for each of these types, or each of these powers. Firstly, for the instantaneous power, we can write that it is U_{ux} which multiplies I_{ux} , which are here instantaneous values depending on time. We then have the second phase U_{vy} which multiplies I_{vy} , and the third phase U_{wz} which multiplies I_{wz} . We will see later how this instantaneous power is finally defined and what conclusion we can draw in the end. For the active power, as mentioned earlier, it is three times the active power in each branch. Therefore, we will write U_{ux} and I_{ux} which multiply $\cos(\varphi)$, and we have the same for the other two branches U_{vy} times $\cos(\varphi)$ and U_{wz} times $\cos(\varphi)$. Three times this which will give us, since these three values by being symmetrical, are equal to three times the phase voltage times the phase current times $\cos(\varphi)$. You will probably remark "yes, but if one of these assemblies is a wye or delta, will that change the result?" Well no, since each time either the line voltage is equal to the phase voltage, or the line current is equal to the phase current. This is always true and can even be replaced by the line voltage and current voltage by writing with the relation $\sqrt{3} U_I I_I, \cos(\varphi)$.

Notes

Summary



2m 23s

$$p = u_{ux} \cdot i_{ux} + u_{uy} \cdot i_{uy} + u_{uz} \cdot i_{uz}$$

$$P = U_{ux} I_{ux} \cos \varphi + U_{uy} I_{uy} \cos \varphi + U_{uz} I_{uz} \cos \varphi$$

$$= 3 U_{ph} \cdot I_{ph} \cdot \cos \varphi = \sqrt{3} U_l I_l \cos \varphi$$

$$Q = 3 U_{ph} \cdot I_{ph} \cdot \sin \varphi = \sqrt{3} U_l \cdot I_l \sin \varphi$$

$$S = 3 U_{ph} \cdot I_{ph} = \sqrt{3} U_l \cdot I_l$$

Montage
en étoile
ou
en
triangle

Electrotechnique II

Notes

Therefore, for the active power in a three-phase system, we have a simple relation letting us focus on one phase only and not on the more complicated system since it is simply three times each phase. We can now write, in the exact same way, the reactive power that we have three times the phase voltage: phase current times the sine of the angle and in the same way write this depending on the line voltage and line current. We will then have, for the apparent power, three times the voltage phase times the current phase or $\sqrt{3}$ times the line voltage times the line current. All this we can say is valid whatever the setup, so wye or delta.

Summary



4m 09s

$$p = u_{ux} \cdot i_{ux} + u_{vy} \cdot i_{vy} + u_{wz} \cdot i_{wz}$$

$$u_{ux} = \sqrt{2} U_{ph} \sin(\omega t + \alpha)$$

$$i_{ux} = \sqrt{2} I_{ph} \sin(\omega t + \alpha - \varphi)$$

$$u_{vy} = \sqrt{2} U_{ph} \sin\left(\omega t + \alpha - \frac{2\pi}{3}\right)$$

$$i_{vy} = \sqrt{2} I_{ph} \sin\left(\omega t + \alpha - \varphi - \frac{2\pi}{3}\right)$$

$$u_{wz} = \sqrt{2} U_{ph} \sin\left(\omega t + \alpha - \frac{4\pi}{3}\right)$$

$$i_{wz} = \sqrt{2} I_{ph} \sin\left(\omega t + \alpha - \varphi - \frac{4\pi}{3}\right)$$

Electrotechnique II

We will now find interest in the instantaneous power, as described previously, that I will rewrite here. Each of these values U, I and in each phase corresponds to an equation that describes, depending on time, the voltage and the current. We will concentrate on the first term U_{ux} and I_{ux} and describe in a faster way the two other terms that are simply out of phase by $2\pi/3$ and $4\pi/3$ respectively. For the first voltage U_{ux} , by definition, we know that it is a sine or cosine. I will describe here $\sqrt{2}$ times the phase voltage, which gives the peak voltage, and for example lets take the sine of ωt with an additional random phase shift which will define the zero of the voltage. We have for the current in the same way, $\sqrt{2}$ times the phase current times a sine that will be shifted by another angle which will be either β , either $(\alpha - \varphi)$. We can describe the other two values U_{vy} and U_{vz} and the other two values of current I_{vy} , I_{vz} in the following way. The instantaneous power is the sum of the product of these two functions of these two functions and these two functions. All this seems very complicated here and we will apply a relatively simple general trigonometry formula that I will show you here.

Notes

Summary



5m 09s

$$\sin a \cdot \sin b = \frac{1}{2} \left[\cos(a-b) - \cos(a+b) \right]$$

$$P = 3 U_{ph} \cdot I_{ph} \cos \varphi - U_{ph} I_{ph}$$



Electrotechnique II

We know that the sine of a multiplied by the sine of b is really equal to a sum of cosines. It is the cosine of the difference of arguments minus the cosine of the sum of arguments. This can seem more complicated than before, but you will see that it will make everything easier. By adding up all the terms of previous U, I that we have seen, we get: First of all, we do the difference of the arguments. By doing this, we have the term $\omega t + \alpha$ that disappears each time. In each element, we always do (a-b) and the $\omega t + \alpha$ is found in each of them, so it disappears. Thus, this instantaneous power that is finally equal to three times the phase voltage times the current phase and, since the ωt plus α disappears each time, there is only the cosine of φ left. We then have a minus sign that appears here and this minus will also be interesting since we have here a phase voltage, a phase current that multiply this time the sum of arguments (a+b), and we have this three times. I will write them down for you. We have the cosine of $2\omega t$ plus 2α minus φ then another cosine of $2\omega t$ plus 2α minus φ , minus $4\pi/3$ and then one more cosine of $2\omega t$ plus 2α , minus φ that is out of phase of $-2\pi/3$.

Notes

Summary



7m 20s

$$\sin a \cdot \sin b = \frac{1}{2} [\cos(a-b) - \cos(a+b)]$$

$$p = 3 U_{ph} \cdot I_{ph} \cos \varphi - U_{ph} I_{ph} \left(\cos(2\omega t + 2\alpha - \varphi) + \cos(2\omega t + 2\alpha - \varphi - \frac{2\pi}{3}) + \cos(2\omega t + 2\alpha - \varphi - \frac{4\pi}{3}) \right)$$

$$p = 3 U_{ph} \cdot I_{ph} \cos \varphi = P$$

= constante égale à la puissance active


Electrotechnique II

Notes

All this, this sum of 3 cosine perfectly out of phase of $2\pi/3$ each, simply gives zero. In conclusion, we see that this instantaneous power, so the power as function of time comes down to because we have here in the first term, three times the phase voltage phase current, $\cos(\varphi)$, and this is none other than the active power that is also, and that is only an observation of this lesson that it is a constant. In other words, the power depending on time is always a constant and equal to the active power. This being so, if we imagine a future use of a three-phase network of a charge for an electromechanical conversion, this means that by converting this electromechanical energy, we can make a system that transfers and transforms a perfectly constant power, so without torque undulation or without a pulsing torque on the machine.

Summary



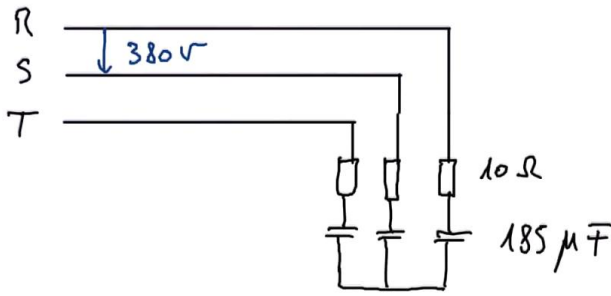

$$U_l = 380 \text{ V} \quad U_{ph} = \frac{U_l}{\sqrt{3}} = 220 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$\underline{I}_{ph} = \frac{\underline{U}_{ph}}{\underline{Z}} = 220 e^{j0}$$


Electrotechnique II

I would now like to give you two examples that will show you how we can calculate in a practical exercise the different powers that we have just described. We will then start with a first example described in the following way: we will connect on the lines R, S and T three completely identical and symmetrical charges. First of all, this charge will be made of three resistors having a value of 10 Ohm followed by a capacitance having a value of 185 μF . We will connect this at a symmetrical three-phase electrical system. We will now give different elements. First of all, we know that the line voltage is equal to 380 V. If the line voltage is equal to 380 V, I remind you that the phase voltage is then equal, in a wye circuit as here, to $\sqrt{3}$ times less so U_l divided by $\sqrt{3}$, namely 220 V. We imagine having a frequency of 50 Hz and we ask you to calculate the different powers that we have in this system. First of all, we can define the phase current that circulates in each branche with a different phasor or a different angle, this phase current will be equal to the phase voltage divided by the impedance Z . We can then write $220 \cdot e^{j(\alpha)}$. We will define α as zero and the reference on Z as the phase impedance.

Notes

Summary



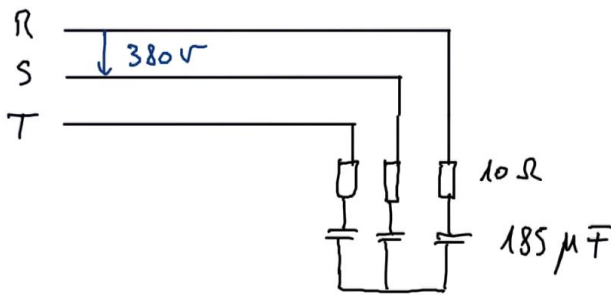

$$U_l = 380 \text{ V} \quad U_{ph} = \frac{U_l}{\sqrt{3}} = 220 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$\underline{I}_{ph} = \frac{U_{ph}}{Z} = \frac{220 e^{j0}}{Z_{ph}}$$

$$Z_{ph} = 10 - j \frac{1}{\omega \cdot 185 \cdot 10^{-6}} = 10 - 17.2 j = 19.9 e^{j(-60^\circ)}$$

$$\underline{I}_{ph} = \frac{220}{19.9} e^{j\frac{\pi}{3}}$$

$$P_{ph} = R \cdot I^2 = 10 \cdot 121 = 1.21 \text{ kW}$$

$$Q_{ph} = X I^2 = -\frac{1}{\omega C} \cdot I^2 = -17.2 \cdot 121 = -2.08 \text{ kVar}$$

Electrotechnique II

Notes

We see here that we first need to define this phase impedance. Let's define Z_{ph} as known, since we know that it is a resistor and a capacitor, namely $10 - j(1/\omega)$ multiplied by $185 \cdot 10^{-6}$. This is also equal to $10 - 17.2j$ or with Euler's formula $19.9 \cdot e^{j(-60^\circ)}$. It is a negative value and is then a good control since the system being capacitive, we must get a negative phase. The phase current is then equal to 220 V divided by 19.9 and this, e^{j} times 60° or $\pi/3$. What is the power then equal to? We can define the three types of power: active, reactive and apparent. Thus, the active power in one of the phases is equal to $R \cdot I^2$ namely $10 \cdot 121$ which gives 1.21 kW . We have the reactive in a phase that is equal to X , the reactance, times I^2 . This reactance, defined by the capacitance, so $(-1/\omega C)$ that multiplies I^2 and that is equal to, with the values in this example, $17.2 \cdot 121$ is negative, and that is normal since we have a capacitance, the reactive is negative. We now need to determine the total power in the whole system and not only in one of the phases.

Summary



$$P_{\text{tot}} = 3 P_{\text{ph}} = 3,63 \text{ kW}$$

$$Q_{\text{tot}} = 3 Q_{\text{ph}} = -6,24 \text{ kVar}$$

$$S_{\text{tot}} = \sqrt{P^2 + Q^2} = 7,21 \text{ VA}$$

Electrotechnique II


The total power is equal to three times the phase power namely 3.63 kW. The total reactive is simply three times the reactive of a single phase namely -6.24 kVAR. Finally, the total apparent power which, as we know it, is equal to the active power squared plus the reactive power squared, gives us 7.21 VA. We can then see that we just need to calculate the powers on a single phase and to multiply by 3 to get the values of the whole circuit.

Notes

Summary



14m 48s

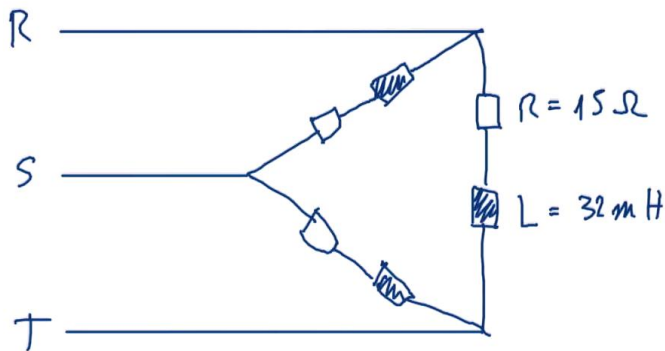

$$P = \sqrt{3} U_l \cdot I_l \cos \varphi$$

$$U_l = 380 \text{ V}$$

$$\underline{Z} = R + jX = R + j\omega L$$

$$= 15 + 10j$$

$$Z = \sqrt{15^2 + 10^2} = 18 \Omega$$

$$\cos \varphi = \frac{R}{Z} = \frac{15}{18} = 0,83$$

Electrotechnique II

Notes


A second example, this time on a delta system, will be suggested. We have here our three-phase electrical circuit on which we will connect a symmetrical charge, composed this time of an inductance and a resistor that are evidently perfectly symmetrical. R will be equal to 15 Ohm and L will be equal to 32 mH. Here too, we ask you to calculate the power given by this system on this charge. Lets write here R, S and T, and lets note that the line voltage is equal to 380 V. We can then define the impedance Z as a starting point, which is equal to $R + jx$, namely $R + j\omega L$ and with the numbers of this problem, it gives us the value of 15 plus $10j$. The norm of Z is equal to $\sqrt{15^2 + 10^2}$, namely about 18 Ohm. The cosine of the impedance, $\cos(\varphi)$ being the real part divided by the total impedance is equal to $15/18$ namely 0,83. We know that the active power, which is what is asked in this exercise, is $\sqrt{3}$ times the line voltage, the line current and $\cos(\varphi)$. We now have the cosine of the angle, the $\sqrt{3}$ and the line voltage, only the line current is missing. I remind you that the line current is the current circulating for example here in this line, and we are searching for the effective value, that is identical in R, in S or in T.

Summary



15m 37s

PUISSANCE EN RÉGIME TRIPHASÉ

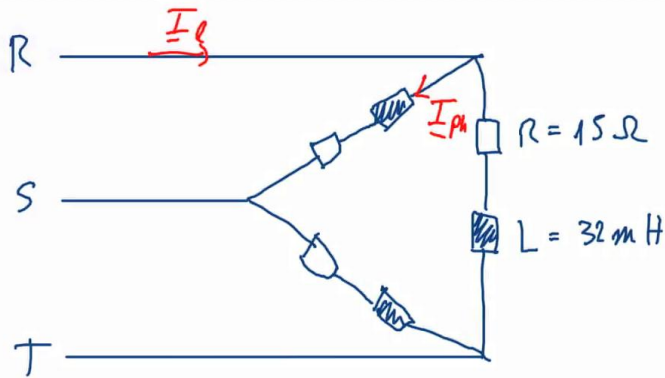

$$P = \sqrt{3} U_l \cdot I_l \cos \varphi$$

$$= 20 \text{ kW}$$

$$U_l = 380 \text{ V}$$

$$\underline{Z} = R + jX = R + j\omega L$$

$$= 15 + 10j$$

$$Z = \sqrt{15^2 + 10^2} = 18 \Omega$$

$$\cos \varphi = \frac{R}{Z} = \frac{15}{18} = 0,83$$

$$I_l = I_{ph} \cdot \sqrt{3} = \frac{U_{ph}}{Z} \sqrt{3} = \frac{U_l}{Z} \cdot \sqrt{3} = 36,6 \text{ A}$$

Electrotechnique II

We know that it is the ratio between the line voltage and the phase voltage here in the phase, it is $\sqrt{3}$. We can then write that the line current is equal to, in effective value, the phase current times $\sqrt{3}$. What is the phase current equal to ? It is the phase voltage divided by Z (the norm) and like always, multiplied by $\sqrt{3}$. This phase voltage, since we are in a delta system, is equal to the line $\sqrt{3}$ divided by Z times $\sqrt{3}$. We have here all the elements and this is equal to 36,6 A. Finally, we can say that our power is equal to exactly 20 kW and this finishes the exercise, where you can see, once again, that by looking at only one impedance of the balanced charge we resolve the whole system.

Notes

Summary



17m 47s



- Dans un système symétrique, la puissance instantanée est constante et vaut la puissance active
- Étudier un problème en triphasé symétrique revient à ne considérer qu'une phase

Electrotechnique II

To conclude, we can describe two important elements. The first one is that in every symmetrical three-phase system connected to a balanced charge, the instantaneous charge is always constant. The second point is that, to resolve a power exercise on a three-phase system, we concentrate on one of the branches and we simply multiply by three the result that we found to get the power of the whole system. See you soon.

Notes

Summary



18m 48s