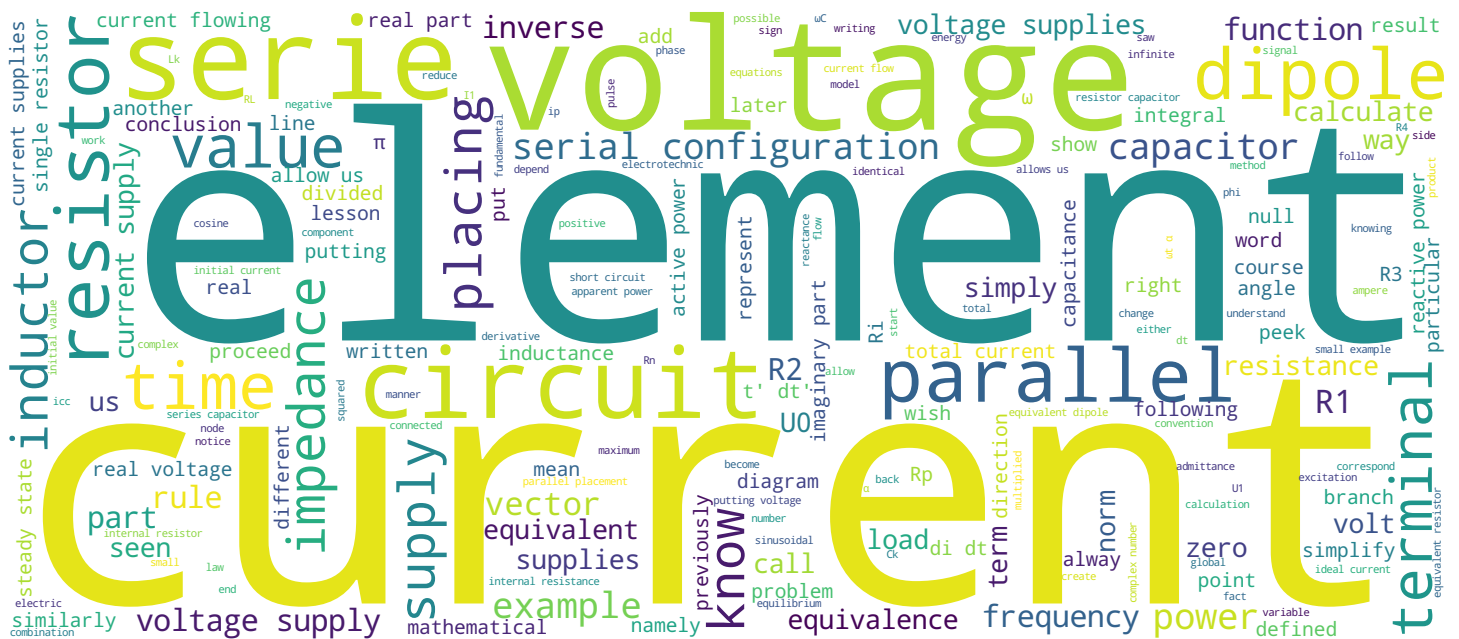


LEÇON 5

Yves PERRIARD & Paolo GERMANO
Laboratoire d'Actionneurs Intégrés



EPFL





- Introduction
- Combinaison simples d'éléments linéaires
- Élément en série
- Élément en parallèle
- Conclusion

Electrotechnique I

Hello and welcome to this lesson dedicated to the analysis and resolution of linear circuits. In this lesson, we will study the combination of simple linear elements. First of all what is an element, or elements, in series like a network. This elements in series for the resistor for the capacitor, for the inductor. We will do the same for these elements in parallel. And finally, we will make a conclusion of this lesson and chapter.

Notes


Summary



0m 03s

Définition : Dipôles équivalents

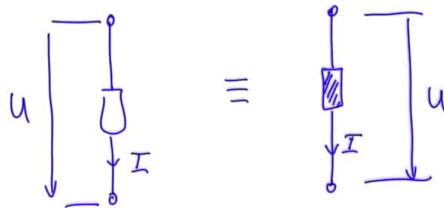Deux dipôles qui ont en tout temps le même courant lorsqu'ils sont soumis à la même tension



Electrotechnique I


Before starting with this combination in series or in parallel, I would like to define here, what an equivalent dipole is : Two equivalent dipoles have, at all times, by definition, the same current when they are submitted to the same voltage. It is important to define this to later on allow us to render objects equivalent in a Kirchhoff model. For example, we will have here an element, we know together that it's a resistor, but let's assume that we don't know that, a different element, that I write like so; well, these two elements, we can say that they are equivalent if, submitted to a voltage u and similarly for your first dipole u , we have a current I which is identical on both sides. In which case, we will say that these dipoles are equivalent.

Notes

Summary



Propriété fondamentale

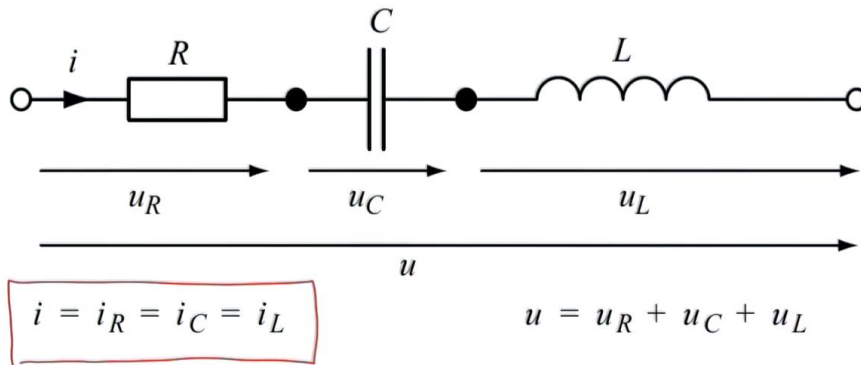

Electrotechnique I

Now, the series connection of elements. It is fundamental to understand, in a more complex circuit, the elements that can be put, or which are, in a serial configuration, or elements that are in a parallel configuration to, later on, reduce the circuit, and to know how to reduce it so as to not create more problems than we are solving. You have here the fundamental properties of putting elements in a serial configuration. We have on this line, in this model, put a resistor, a capacitor, and an inductor. The fundamental definition of putting in series, is to be able to say that the currents, the three currents of these three elements, are the same, or are identical. Thus, placing elements in series, means that the current flowing through each element is the same. And then, another property derived from Kirchhoff's equations, is that if these elements are in series and have the same current flowing through, the sum of the voltages, which is here between the resistor, capacitor and inductor this sum of voltages is also the voltage at the terminals of the complete dipole. Between this part of the dipole and this part of the dipole.


Notes

Summary



1m 28s

Propriété fondamentale

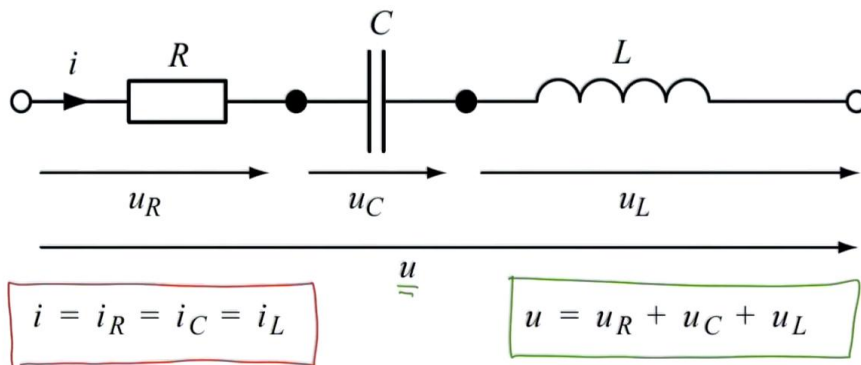

Electrotechnique I

We will thus have the voltage u present here which is equal to $u_R + u_C + u_L$. Now that we've defined what is the placing of elements in a serial configuration, we will focus on the three elements R , L , C to separately see what it means for each of these elements.


Notes

Summary



2m 48s

Mise en série de résistances

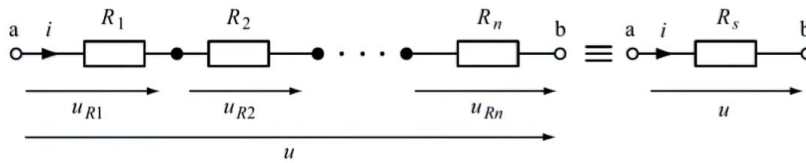

$$u = \sum_{k=1}^n u_{R_k} = \sum_{k=1}^n R_k \cdot i = R_s i \quad \Rightarrow \quad R_s = \sum_{k=1}^n R_k$$

Electrotechnique I

Let's start with the resistor and placing resistors in series. What we wish for, in the end, when we have resistors in series with the same current flowing through R_1 to R_n , is to replace this set of resistors with a single resistor known as equivalent, R_s , through which the same current flows and with the same voltage at the terminals, so, it is the equivalence of dipoles that we've seen earlier, and in that instant, what can we say about this new equivalent resistor ? Well, knowing that the voltage u is the sum of the partial voltages from k to 1 up to n of u_{R_k} , that this sum is equal to the complete u , but that we can also replace this u_{R_k} by this sum from 1 to n , of the R_k times I , the current being the same all the way through, and we want this to be equal to the R_s resistor times I , from this, ensues an obvious fact that most of you are already aware of, that this series resistor in a series, of several resistors in a series, is simply the mathematical sum from K 1 to n of the separate resistors R_k .


Notes

Summary



3m 10s

Mise en série de capacités

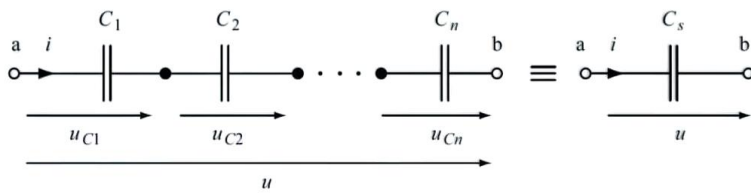

$$u_{C_k} = \frac{1}{C_k} \int_0^t i(t') dt' + u_{C_k}(0) \quad u =$$

Electrotechnique I

We will do the same for capacitors in a serial configuration. So once again, we have an equivalence of dipoles, we which to render equal these two dipoles. We have a dipole of several capacitors in a serial configuration, through which the same current flows, we have at the terminals of this complete dipole a voltage u and we which to replace this dipole with a single capacitor, in other words, a capacitor equal to the set of all the capacitors in the serial configuration, here. How do we do this ? we know that a voltage at the terminals of the capacitor k , is $1/C_k \int_0^t i(t') dt' + \text{the initial condition : } u_{C_k}(0)$ So know, we will sum all of these voltages, so we will have the global u of the sum of all the voltages. What is it ? It's : $1/C_1 + 1/C_2 + \text{etc until } 1/C_n$ of the integral(from 0 to t) of $i(t') dt' + \text{a set of initial conditions } [u_{C_1}(0) \text{ etc}]$ And we want this to be equal to $1/C$, the series capacitor C_s , integral(from 0 to t) $i(t') dt' + u(0)$ it of course follows that $1/C_s$ is equal to the sum of $k=1$ to n of the $1/C_k$ This is the same as writing that C_s is equal to $1 / \text{sum of } k=1 \text{ to } n \text{ of the } 1/C_k$ This is the rule of putting capacitors in series.


Notes

Summary



4m 43s

Mise en série de capacités

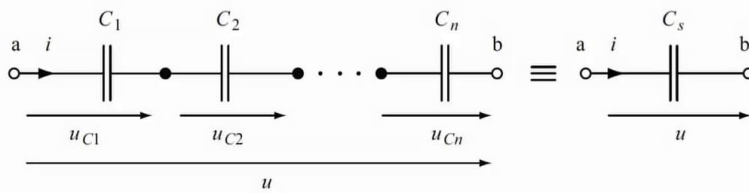

$$u_{C_k} = \frac{1}{C_k} \int_0^t i(t') dt' + u_{C_k}(0)$$

$$u = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right) \int_0^t i(t') dt' + [u_{C_1}(0) \dots]$$

$$= \frac{1}{C_s} \int_0^t i(t') dt' + u(0)$$

$$u(0) = \sum_{k=1}^n u_{C_k}(0)$$

$$\frac{1}{C_s} = \sum_{k=1}^n \frac{1}{C_k} \quad \equiv \quad C_s = \frac{1}{\sum_{k=1}^n 1/C_k}$$

Electrotechnique I

We say one more thing about the initial value of the voltage at the terminals of the circuit. This initial value, $u(0)$ is simply equal to the sum of all the values of $u_{C_k}(0)$. We can also say that the placing of capacitors in a serial configuration will insure that the final series capacitor of all the elements will in general, necessarily, according the equations here, be smaller than each of the partial capacitors.


Notes

Summary



6m 56s

Mise en série d'inductances

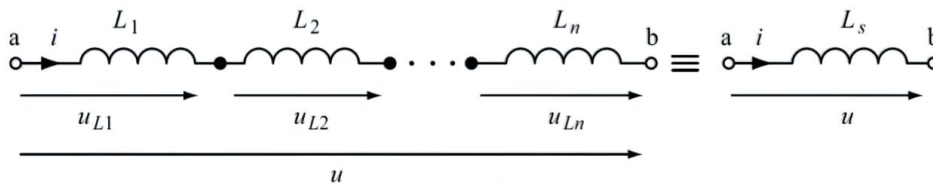

$$u = L \frac{di}{dt} \quad u = \sum_{k=1}^n u_{Lk} = (L_1 + L_2 + \dots + L_n) \frac{di}{dt} = L_s \frac{di}{dt}$$

$$L_s = \sum_{k=1}^n L_k$$

Electrotechnique I


Now, here is the placing of inductors in a serial configuration. So just like the previous ones, you have understood it now, between the resistor and capacitor, we have here an equivalence of two dipoles. We want this set of inductors in series to be equal to this single equivalent inductor. So then, we can write that, knowing u is equal to $L \frac{di}{dt}$ in a general manner for an inductor. we can write that the global u of placing in a serial configuration, is the sum of $k=1$ to n of the u_{Lk} , which is equal to $(L_1 + L_2 + \dots + L_n) \frac{di}{dt}$, the i being common to all, it's the same, and we want this to be equal to $L_s \frac{di}{dt}$. It follows that the rules are exactly the same as for the resistors, that L_s is the mathematical sum of k from 1 to n of the L_k .

Notes

Summary



Mise en série de sources de tension

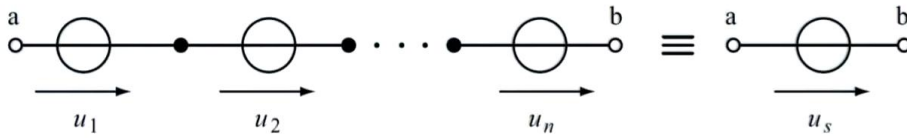

$$u_s = \sum_{k=1}^n u_k$$

Electrotechnique I

An important element now is putting voltage supplies in a serial configuration. What can we say when we put different supplies in series and that we want to, like previously for the equivalence of two dipoles, we wish to replace the set of supplies by a single equivalent supply U_s ? Well, here like previously, it's actually relatively obvious, this global u_s , this supply which replaces all the partial supplies in series, is the sum of k from 1 to n , of the partial supplies u_k .


Notes

Summary



8m 40s

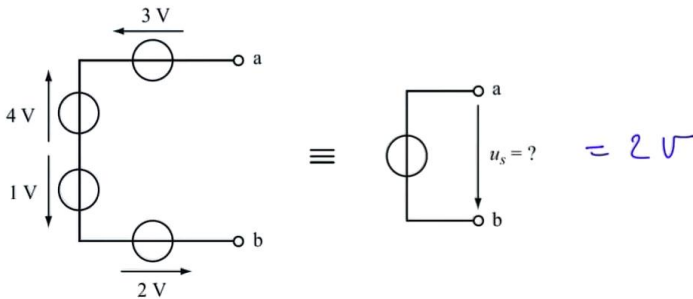Mise en série de sources de tension - exemple



Electrotechnique I

We can make a small example to convince ourselves, by saying : well here we are, we have an example of 4 supplies in a serial configuration. We wish to replace this element of 4 supplies in series by a single supply to simplify the diagram. What is the value of U_s , knowing that we have 3 volts, we have 4 volts, we have 1 volt and 2 volts, but with different directions. Well, we will have $3V - 4V + 1V + 2V$ and this gives us a $U_s = 2V$. So of course, take care with the direction of the mathematical voltages when we proceed with the sum and the placing in series of voltage supplies.

Notes

Summary



9m 19s

Mise en série de sources de courant

Impossible sauf si toutes les sources ont même valeur et signe

Electrotechnique I

It is obvious that it is not possible to consider placing several current supplies in series without violating Kirchhoff's first law, except if all the individual supply produce exactly the same current. In which case, the equivalent dipole will simply be equal to any one of the individual supplies. Thus, what we can say here is that the placing in series here is impossible, except if all the supplies are of the same value and sign. In this very particular case, it is possible to put current supplies in series.


Notes

Summary



10m 01s

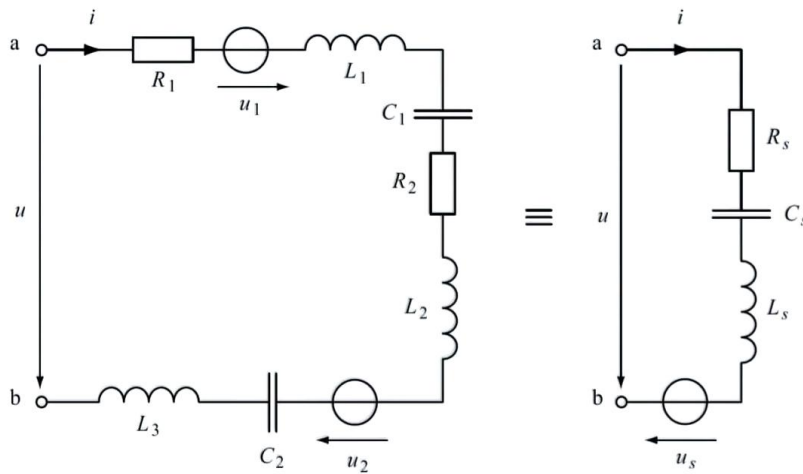Mise en série de plusieurs éléments de chaque type



Electrotechnique I


And finally, an example of placing several elements in series. Once again, we notice that all of these elements, it's true that it's pretty obvious here, having the same current flowing through, all of these elements in series. We group them based on families, in other words, all the resistors together, all the capacitors together and all the inductors together. We can then already proceed to a simplification of this model on the left through this equivalent model on the right with 3 elements which represent the placing in series of the all separate elements.

Notes

Summary



Propriété fondamentale

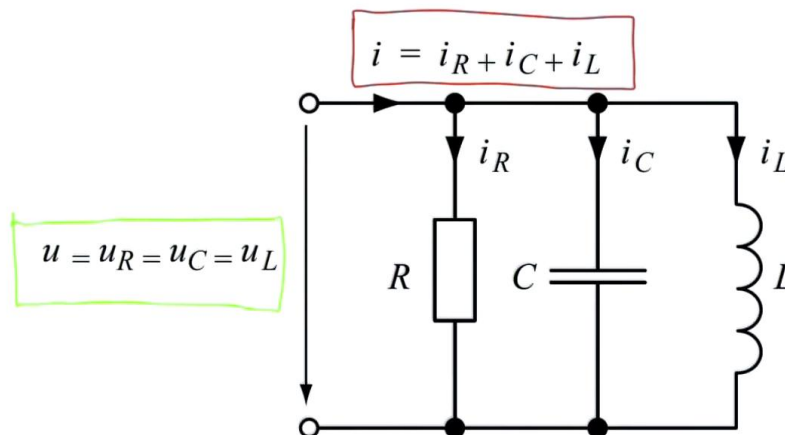

Electrotechnique I


Let us now proceed to parallel placement of elements. What is the definition of putting elements in parallel ? You have a diagram with a resistor, capacitor and inductor which are in parallel. The definition, is that the 3 elements R , L and C , have the same voltage at their terminals. So this is the definition. R and C are parallel, similarly R and L are parallel, similarly C and L are parallel. Because the voltage at their terminals is strictly equal. Thus, the three currents that flow through these elements are different, but, through Kirchhoff, the sum of these three currents is necessarily equal to the total current output here of the dipole, so we can also write that this current here, is the sum of i_R , of i_C and of i_L . We will now go back to R , C then L , and for each of these elements, see what are the rules to be able to simplify elements in parallel of R , of C or of L .

Notes

Summary



Mise en parallèle de résistance

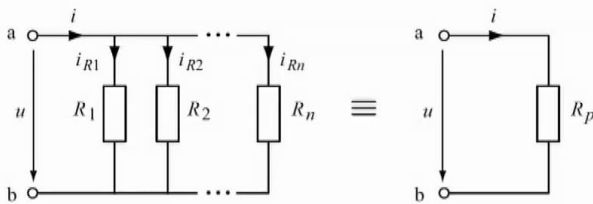

$$i = i_{R_1} + i_{R_2} + \dots + i_{R_n} = i$$

$$= \frac{u}{R_1} + \frac{u}{R_2} + \dots + \frac{u}{R_n} = \frac{u}{R_p}$$

$$\Rightarrow \frac{1}{R_p} = \sum_{k=1}^n \frac{1}{R_k} \quad \equiv \quad R_p = \frac{1}{\sum_{k=1}^n \frac{1}{R_k}}$$

Electrotechnique I


First of all, putting resistors in parallel. Once again, we decide to define 2 dipoles : the dipole with the number of resistors at n resistors placed parallel to each other, because, as you can see here, connected to the same voltage u_{AB} , and we wish to replace this with a single resistor equivalent to the previous dipole, and this parallel equivalent resistor, with a single resistor R_p . How do we do it ? We know that the current as written previously, is the current in R_1 + the current in R_2 + etc the current in R_n . It's the total current of the dipole that we have, i . We also know that this current must be equal to i of the right dipole, as written already here. If we replace i_{R_1} , i_{R_2} , i_{R_n} and so on, using Ohm's law, we have u/R_1 u/R_2 etc u/R_n and this must be equal to u/R_p We define then the rules of placing resistors in parallel, which is the following : it's that $1/R_p$ is equal to the sum of k from 1 to n of the $1/R_k$ In other words, we can also write this in another way, it's that R_p is equal to 1 over the sum of the inverses of R_k for k from 1 to n .

Notes

Summary



Mise en parallèle de capacités

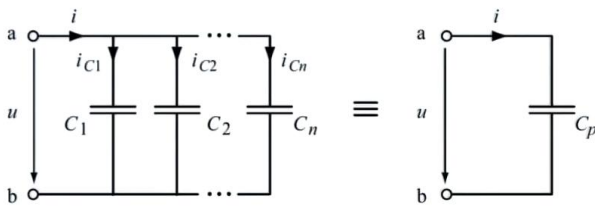

$$i = \sum_{k=1}^n i_{C_k} = (C_1 + C_2 + \dots + C_n) \frac{du}{dt} = C_p \frac{du}{dt}$$

$$C_p = \sum_{k=1}^n C_k$$

Electrotechnique I

We will now look at placing capacitors in parallel. We apply exactly the same rule. We know that the total current output here in this dipole, is the sum of each of the currents of each branch, We can thus write i is the sum of k from 1 to n of the i_{C_k} in other words $(C_1 + C_2 + \text{etc until } C_n)$ of the voltage variation over time. And we want this to be equal to C_p times du/dt Thus, we can write that C_p is equal to the sum of k from 1 to n of the C_k . So it's pretty simple to calculate the placing of capacitors in parallel. It's simply the sum.


Notes

Summary



14m 24s

Mise en parallèle d'inductances

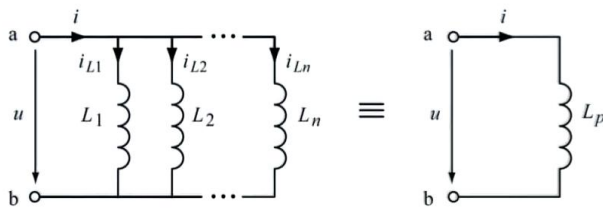

$$\frac{1}{L_p} = \sum_{k=1}^n \frac{1}{L_k} \quad \equiv \quad L_p = \frac{1}{\sum_{k=1}^n \frac{1}{L_k}}$$

$$i_{L_k}(t) = \frac{1}{L_k} \int_0^t u(t') dt' + i_{L_k}(0)$$

$$i = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right) \int_0^t u(t') dt' + [i_{L_1}(0) + \dots + i_{L_n}(0)]$$

$$= \frac{1}{L_p} \int_0^t u(t') dt' + i(0)$$

$$i(0) = \sum_{k=1}^n i_{L_k}(0)$$

Electrotechnique I


Finally, we need to calculate the placing in parallel elements of inductors before proceeding to supplies. So we proceed once again in the same manner. We know that a current i_{Lk} as a function of time is $1/L_k \int_0^t u(t') dt' + i_{Lk}(0)$. We can then write that this current i , that we want in the dipole on the right, is $1/L_1 + 1/L_2$ and so on until $1/L_n$ all of this in brackets, times the integral of $u(t')$ + all the initial currents, $[i_{L1}(0) \text{ etc until } i_{Ln}(0)]$. And this, we want it to be equal to $1/L_p \int_0^t u(t') dt' + i(0)$. What we can say and what we can see, is that placing in parallel will allow us to compute the equivalent L , L_p , $1/L_p$ is equal to the sum of k from 1 to n of the $1/L_k$. In other words, L_p is the inverse of the sum of inverses, from $k=1$ to n of L_k . And similarly, we will be able to say, just like the resistor, it's the inverse of the sum of inverses, for inductors in parallel, and add to this the fact that initial value of the current flowing through the circuit, and simply equal to the mathematical sum of the initial currents. So we will have $i(0)$ equal to a sum from $k=1$ to n of the $i_{Lk}(0)$. So now we have the rules of putting in parallel elements of R , L and C .

Notes

Summary



Mise en parallèle de sources de courant

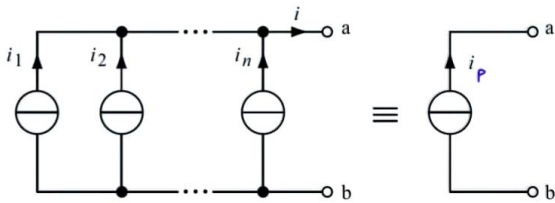

$$i_p = \sum_{k=1}^n i_k$$

Electrotechnique I

We will now see the placing in parallel of current supplies. So here also, it's pretty simple since we apply Kirchhoff. By wanting to equalize the left dipole with the right dipole, we can see that i , which is defined here, is we sum the currents, we will discover that i_p , we will call like this, is equal to the sum of i_k currents by taking $k=1$ to n , and we will thus define this i as i_p . So we have an equivalence here, which allows us to, once again, do a small example, to show you in a practical manner how this happens.


Notes

Summary



17m 42s

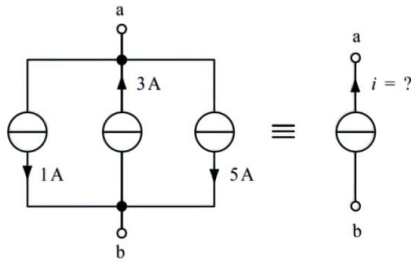Mise en parallèle de sources de courant - exemple



$$i = -3A$$

Electrotechnique I

So if you have here a dipole ab with 3 current supplies in parallel that we wish to replace with a single current supply. What is the value of the i_A current ? We will have 3 amperes which go up - 1 ampere, 2 remain, - 5 amperes. Well, the current i is of - 3 amperes. So this i is equal to -3A.

Notes

Summary



Mise en parallèle de sources de tension

Impossible, Sauf si elles ont toutes la même valeur et le même signe

Electrotechnique I

We continue with parallel placement of voltage supplies, and similarly, we have a problem with putting voltage supplies in parallel. We cannot do this parallel placement without violating Kirchhoff's second law and once again, here as well, except if they are all the same voltages. If they all have the same voltages, in this case we can simplify it to a single supply, which will be the same supply that each of these defines. And thus we can write that putting voltage supplies in parallel is impossible except if they all have the same value and sign.

Notes

Summary



19m 00s

CONCLUSION



	Montage série	Montage parallèle
Résistances	$R_s = \sum_{k=1}^n R_k$	$R_p = \left[\sum_{k=1}^n 1/R_k \right]^{-1}$
Capacités	$C_s = \left[\sum_{k=1}^n 1/C_k \right]^{-1}$	$C_p = \sum_{k=1}^n C_k$
Tension initiale	$u(0) = \sum_{k=1}^n u_{Ck}(0)$	
Inductances	$L_s = \sum_{k=1}^n L_k$	$L_p = \left[\sum_{k=1}^n 1/L_k \right]^{-1}$
Courant initial		$i(0) = \sum_{k=1}^n i_{Lk}(0)$
Sources de tension	$u_s = \sum_{k=1}^n u_k$	
Sources de courant		$i_p = \sum_{k=1}^n i_k$

Electrotechnique I

To conclude, we've seen the parallel and serial placement of all the elements R, L, C, of ideal current and voltage supplies. As a conclusion, I will show you here a table which sums up what we've just seen with serial configurations, the definition of resistors in series, capacitors in series, inductors in series, voltage supplies in series, and parallel configurations with the resistor, capacitor, inductor, and similarly for the ideal current supply. Thank you

Notes

Summary



19m 42s