

## LECON 6

Yves PERRIARD & Paolo GERMANO  
Laboratoire d'Actionneurs Intégrés





- Circuits combinés série-parallel
- Diviseurs de tension
- Diviseurs de courant
- Conclusion

Electrotechnique I

Hello and welcome to this MOOC or in this lesson dedicated to the analysis and resolution of linear circuits, the second part of our chapter. We will see in this second part combined, series and parallel circuits when we have multiple elements that are together, in series and in parallel. We will then see these two elements or two very special models that are finally very very common in the electrical circuits that are tension and current dividers.


Notes

Summary



0m 04s

## Exemple avec des résistances

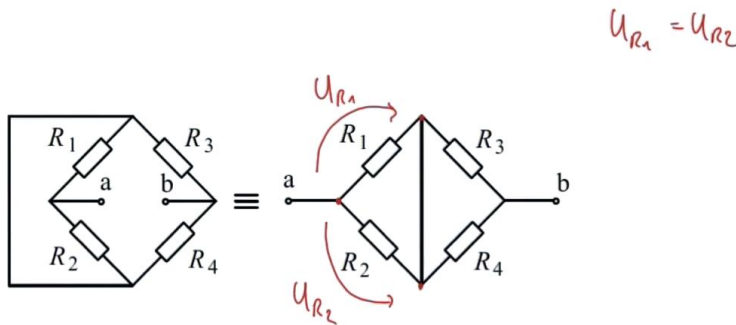

Electrotechnique I


Finally, we will have a conclusion for this lesson. We will start with an example. An example here with only resistors, an extremely clear example, to see that it is very difficult in this diagram to know if  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  are in series or in parallel knowing that we wish to calculate an equivalence of this dipole between  $a$  and  $b$ . When we are in such a case, the first thing to do is to redraw the circuit differently, to play with it, to inverse it, in order to find a more clear vision of the diagram. That is what we do here, by extracting  $a$  and  $b$  and by redrawing the same diagram. We still have the circuit between  $R_1$   $R_3$ , you have here between  $R_1$   $R_3$ , and  $R_2$   $R_4$  this diagram that closes and so strictly the same thing. We can then notice a certain number of things. We note that the voltage that is here on the boundaries of  $R_1$ , this voltage that we will call  $U_{R1}$ , is the same as this voltage here,  $U_{R2}$ . Why? Because this potential is the same as this one and this potential is the same for  $R_1$  and for  $R_2$ . So  $U_{R1}$   $U_{R2}$  being equivalent, we know that  $R_1$   $R_2$  is in parallel. We can do the same thing with  $R_3$  and  $R_4$  that are in parallel and we can then write that this diagrams transforms into  $R_{12}$  and  $R_{34}$  and these two are in series since the current that circulates between these two blocs will now be equivalent.

Notes

Summary



## Exemple avec des résistances

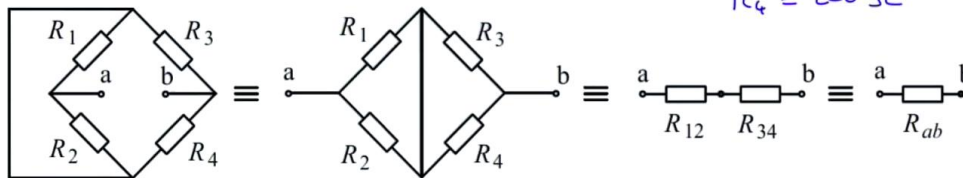

$$\begin{aligned} R_1 &= 2 \text{ k}\Omega \\ R_2 &= 8 \text{ k}\Omega \\ R_3 &= 5 \text{ k}\Omega \\ R_4 &= 200 \Omega \end{aligned}$$

$$R_{12} \Rightarrow R_{12} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad R_{34} = \frac{R_3 \cdot R_4}{R_3 + R_4}$$

$$R_{ab} = R_{12} + R_{34} = 1792 \Omega$$

Electrotechnique I


And to finish, we have the equivalence between a and b,  $R_{ab}$ . So how do we calculate this  $R_{ab}$ ? Well, for example for  $R_{12}$ . First,  $R_{12}$ . We know that to calculate  $R_{12}$ ,  $R_{12}$  is 1 over the inverse of the resistor's sum so 1 over  $R_1$  plus one over  $R_2$ . This lets us write that  $R_{12}$  is equal to  $R_1$  times  $R_2$  over  $R_1$  plus  $R_2$ . We can evidently write the same thing for  $R_{34}$  that will, in the same way, be written as  $R_3$  times  $R_4$  over  $R_3$  plus  $R_4$ . And finally,  $R_{ab}$  being  $R_{12}$  and  $R_{34}$  in series, it becomes the sum of  $R_{12}$  plus  $R_{34}$ , so  $R_{ab}$  is  $R_{12}$  plus  $R_{34}$ . We can now do a numerical example, we give for example  $R_1$  equal to 2 kilo-ohms,  $R_2$  to 8 kilo-ohms,  $R_3$  to 5 kilo-ohms and finally  $R_4$  equal to 200 ohms. We get a  $R_{ab}$ , if you do the whole calculation with all that was shown, you will find 1792 ohms.

Notes

Summary



## Exemple avec des capacités

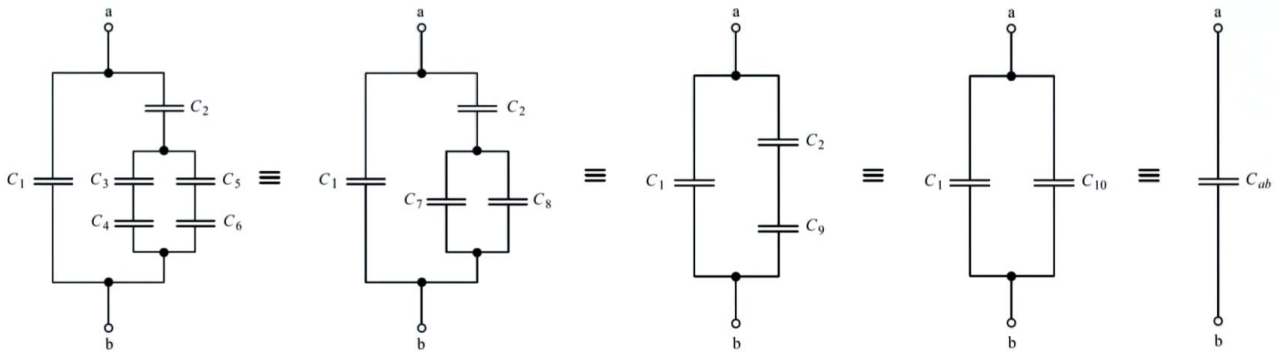

Electrotechnique I

We can now do the exact same things with capacitances and I will show you once again a quite complete diagram. How do we resolve such a diagram? To start with, here is the first question. Which elements will be in series and which will be in parallel? It is also very good to ask yourself the questions "Is this parallel?", "Is this in series?". First, we have a tension that we will call  $U_1$  that is exactly the same as  $U_1$  here. This means that  $C_3$   $C_4$  are in parallel with  $C_5$   $C_6$ . We also see that the current that circulates here, let's call it  $i_3$ , will be the same as the current passing here,  $i_4$ , so  $C_3$  and  $C_4$  are in series. In the same way,  $C_5$   $C_6$  are in series. Then, we ask ourselves these questions. We can then write that  $C_3$   $C_4$  being in series, we can replace them by  $C_7$ ,  $C_5$   $C_6$  can be replaced by  $C_8$ , we then have  $C_7$   $C_8$  in parallel that will become  $C_9$  and that will be in series with  $C_2$  and then in parallel with  $C_1$  and this finally gives us our capacitance  $C_{ab}$ . Then, we can evidently give the final elements. First, this  $C_7$  that we have written before.  $C_7$  being in series, so we have the inverse of the capacitance that is equal to the sum of the inverses; we find the same rules again, we have  $C_3$  times  $C_4$  over  $C_3$  plus  $C_4$ .


Notes

Summary



4m 08s

## Exemple avec des capacités

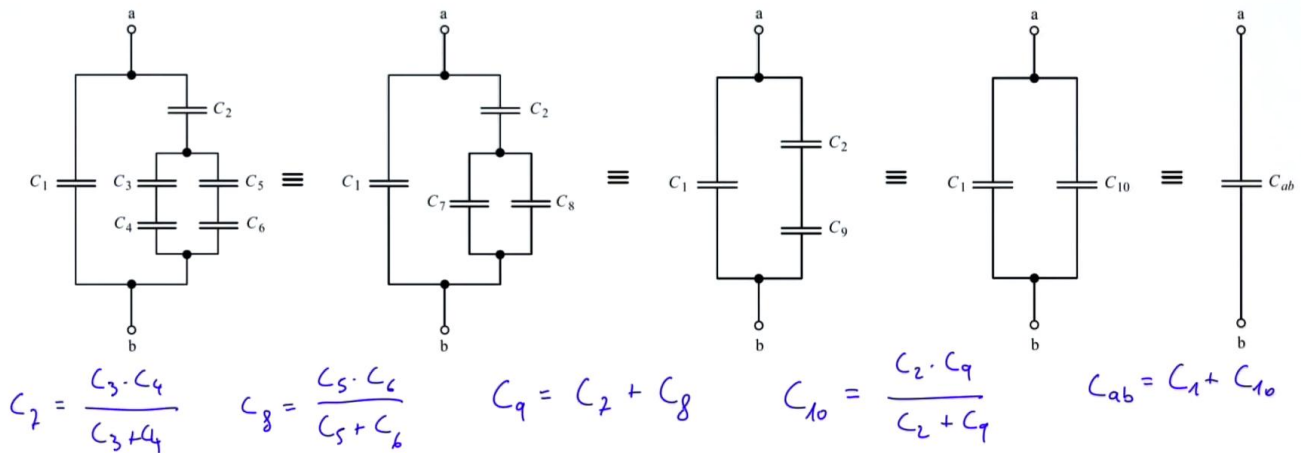

Electrotechnique I

Then, we have  $C_8$ , which in the same way can be calculated as being  $C_5$  times  $C_6$  over  $C_5$  plus  $C_6$ . We then have  $C_9$ . If you put  $C_7$  and  $C_8$  in parallel, you get  $C_9$ , so it is simply the sum of  $C_7$  and  $C_8$ . Finally, we have  $C_{10}$ . How do you find  $C_{10}$ ? You put  $C_2$  and  $C_9$  in series. We will then have  $C_2$  times  $C_9$  divided by  $C_2$  plus  $C_9$ . And finally, we put  $C_1$  and  $C_{10}$  in parallel to get  $C_{ab}$  and it is simply the sum of  $C_1$  plus  $C_{10}$  that we have just calculated. And that is how we simplify a diagram when we put various elements in parallel or in series like the capacitance here.


Notes

Summary



5m 49s

## Exemple de circuit en échelle

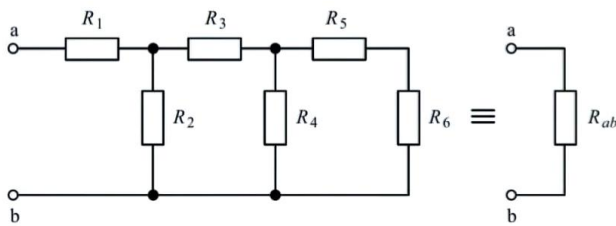

$$R_{ab} = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{\frac{1}{R_3} + \frac{1}{\frac{1}{R_4} + \frac{1}{R_5 + R_6}}}}$$

Electrotechnique I

I will also show you a specific example of a circuit that can make you think that we are neither in series nor in parallel. So, yes and no is what we call a ladder circuit. We can see here that R5 R6 are in series and then in parallel with R4 which is itself in series with R3 and then in parallel with R2, and so forth. We can then calculate this resistance Rab in a successive way, beginning with R1, R1 to which we add all of this, so we have 1 over R2 plus 1 over 1 over R3 plus 1 over 1 over R4 plus 1 over R5 plus R6. And finally there is that scaling of the different elements in series, which lets us simplify the problem and have only one equivalent resistor.


Notes

Summary



6m 47s

## Exemple de circuit complet

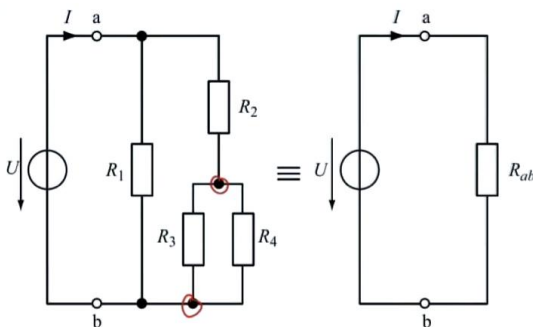

$$R_{34} = \frac{R_3 \cdot R_4}{R_3 + R_4}$$

$$R_{234} = R_2 + \frac{R_3 \cdot R_4}{R_3 + R_4}$$

$$R_{ab} = \frac{R_1 \cdot R_{234}}{R_1 + R_{234}}$$

$$U = 73.45 \text{ V}$$

$$R_1 = 22 \Omega$$

$$R_2 = 36 \Omega$$

$$R_3 = 18 \Omega$$

$$R_4 = 15 \Omega$$

Electrotechnique I

Here is another example of a complete circuit with resistors this time. Once again in this diagram, which resistors are in parallel and which of them are in series? We clearly have here  $R_3$  and  $R_4$  in parallel, then are at the same voltage; these two points here have the same potential for  $R_3$   $R_4$  and this one the same potential for  $R_3$   $R_4$ . Then, if we simplify this by  $R_{34}$ , this will be in series with  $R_2$ . Then the whole will be in parallel with  $R_1$ . So this is the way to resolve such a circuit. We can then summarise in this way, that we will have  $R_{34}$  which is equal to  $R_3$  times  $R_4$  over  $R_3$  plus  $R_4$ . We then have  $R_2$  in series with  $R_{34}$ , that we will call  $R_{234}$ , namely  $R_2$  plus what we have just calculated,  $R_3$  times  $R_4$  over  $R_3$  plus  $R_4$ . Finally,  $R_{ab}$  will be  $R_1$  and  $R_{234}$  in parallel. So  $R_{ab}$  finally is  $R_1$  times  $R_{234}$  over  $R_1$  plus  $R_{234}$ . We can now do a numerical calculation to give us an idea. We have, if we take a numerical example,  $U$  equal to 73,45 volts for example. A measurement example that was done lately on this type of circuit with  $R_1$  equal to 22 ohms,  $R_2$  equal to 36 ohms,  $R_3$  equal to 18 ohms et  $R_4$  equal to 15 ohms. So if we first ask ourselves, as suggested earlier, what is  $R_{ab}$  equal to, we find the final  $R_{ab}$  equal to 14,69 ohms.

Notes


Summary



7m 51s



## Exemple de circuit complet

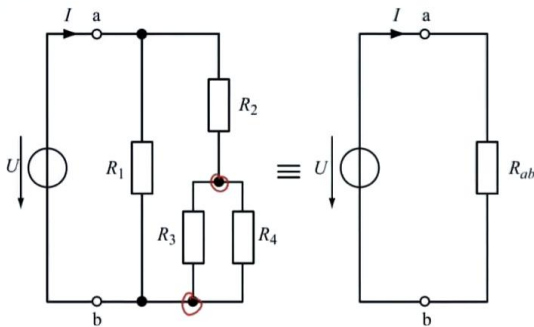

$$R_{34} = \frac{R_3 \cdot R_4}{R_3 + R_4}$$

$$R_{234} = R_2 + \frac{R_3 \cdot R_4}{R_3 + R_4}$$

$$R_{ab} = \frac{R_1 \cdot R_{234}}{R_1 + R_{234}}$$

$$U = 73.45 \text{ V}$$

$$R_1 = 22 \Omega$$

$$R_2 = 36 \Omega$$

$$R_3 = 18 \Omega$$

$$R_4 = 15 \Omega$$

$$R_{ab} = 14.69 \Omega$$

$$U = R_{ab} \cdot I$$

$$I = \frac{U}{R_{ab}} = 5 \text{ A}$$

Electrotechnique I


It is now evident to answer an initial question that we could ask ourselves: "What is the value of the current delivered by the supply?". We know that  $U$  is equal to  $R_{ab}$  times  $i$ . And, if we are looking for the current,  $i$  is equal to  $U$  over  $R_{ab}$ , we then find that this current is simply equal to 5 amperes.

Notes

Summary



## Diviseur de tension résistif

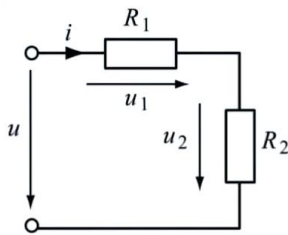

$$U_1 + U_2 = U$$

$$R_1 \cdot i + R_2 \cdot i = U$$

$$\Rightarrow i = \frac{U}{R_1 + R_2}$$

Electrotechnique I


We now pass to a familiar diagram that we often find in a more complete ensemble of an electrical model which is the resistive voltage divider. Why do we call this the resistive voltage divider? Well because if we have an initial voltage  $U$  with 2 resistors in series, at the boundaries of the second resistor, here, as it happens,  $U_2$ , we will have a  $U_2$  small than the initial  $U$  so this lets us uncouple, divide, separate, -- see it as you wish -- the initial voltage in a smaller voltage, more interesting for such and such a circuit. For example, you have 24 volts arriving from a supply but you would like to get 5 volts for this or that reason, well, with the judicious choice of  $R_1$  and  $R_2$ , we can calculate  $U_2$  in such a way that we will get exactly the 5 volts we are looking for. How do we define or how do we calculate this kind of thing? Well, we simply use Ohm's law. We know that the sum of the voltage  $U_1$  plus  $U_2$  is equal to  $U$ . We know that  $U_1$  is  $R_1$  times  $i$  and that  $U_2$  is  $R_2$  times  $i$ . All this being always equal to  $U$ , so  $i$  is equal to  $U$  over  $R_1$  plus  $R_2$ . Since  $U_1$  is equal to  $R_1$  times  $i$  and  $U_2$  is equal to  $R_2$  times  $i$ , we finally get that for  $U_2$ , which is here, and is equal to  $R_2$  times  $i$ , it is also equal to  $U$  times  $R_2$  over  $R_1$  plus  $R_2$ .

Notes

Summary



## Diviseur de tension résistif

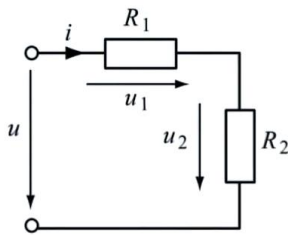

$$U_1 + U_2 = U$$

$$R_1 \cdot i + R_2 \cdot i = U$$

$$\Rightarrow i = \frac{U}{R_1 + R_2}$$

$$U_2 = R_2 \cdot i = U \cdot \frac{R_2}{R_1 + R_2}$$

Electrotechnique I


This lets us calculate, in a general and fast way, that this voltage  $U_2$ , if I have chosen rightly  $R_1$  and  $R_2$ , I can do a voltage divider. And this can evidently be done not only with resistors -- so it is here a resistive voltage divider -- but also with a capacitive voltage divider.

Notes

Summary



## Diviseur de tension capacitif

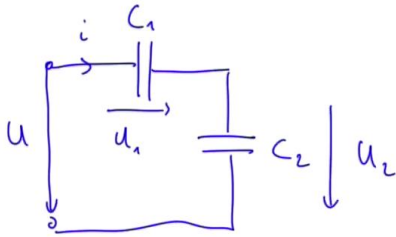

$$U_1 = U \frac{C_2}{C_1 + C_2}$$

Electrotechnique I

In this case, we take the exact same diagram as before so we will have here a voltage  $U$ , on whose boundaries we will have two capacitances that will let us,  $C_1$  and  $C_2$ , do the exact same thing then before, with still  $U_1$  and here  $U_2$ , and to divide this voltage here between  $C_1$  and  $C_2$ . In such a case, we can also easily convince ourselves that  $U_1$ , using Kirchhoff's law as we did before,  $U_1$  will be equal to  $U$  times  $C_2$  over  $C_1$  plus  $C_2$ . This will be the rule for a capacitive voltage divider.

Notes

Summary



12m 44s

## Diviseur de tension inductif

$$U_1 = U \frac{L_1}{L_1 + L_2} \quad U_2 = U \frac{L_2}{L_1 + L_2}$$

Electrotechnique I

Finally, the inductive voltage divider. Once again, we have the same diagram, I will not redraw it here, but we will find it again, since the rules to put things in series are the same as those for resistances with inductance, in the same way we see that  $U_1$  is equal to  $U$  times  $L_1$  over  $L_1$  plus  $L_2$ , and from there we can also write that  $U_2$  is equal to  $U$  times  $L_2$  over  $L_1$  plus  $L_2$ . It is then easy to remember that the final rule for the inductive voltage divider follows the same kind of relation as the resistive voltage divider.


Notes

Summary



13m 34s

## Circuits diviseurs de courant

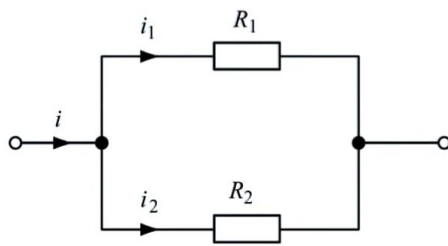

$$i = i_1 + i_2$$

$$U_1 = U_2 = R_1 \cdot i_1 = R_2 \cdot i_2$$

$$i_1 = i \frac{R_2}{R_1 + R_2}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

Electrotechnique I


Now the current divider. You have here another phenomenon, so the current arrives at the boundaries of this dipole, separates in two on two resistors. We very often have this kind of problematic in a circuit. We have  $R_1$  and  $R_2$  in parallel, but if we wish to calculate  $i_1$  or  $i_2$ , it is excluded to resolve this circuit by replacing  $R_1$  and  $R_2$  by a single resistor. We would then have  $i_1$  and  $i_2$  "drowned in the equivalent resistor". We must then keep these two resistors and calculate separately the values of  $i_1$  and  $i_2$ . Once again, we will do this in a very simple manner. We can apply here Kirchhoff's laws. We know that  $i$  is equal to  $i_1$  plus  $i_2$ . We also know that  $U_1$  which is equal to  $U_2$  is equal to  $R_1$  times  $i_1$  but it is also equal to  $R_2$  times  $i_2$ . From all this, we can easily find that  $i_1$  is equal to  $i$  total that multiplies  $R_2$  over  $R_1$  plus  $R_2$  and we also find that  $i_2$  is equal to  $i$  that multiplies  $R_1$  over  $R_1$  plus  $R_2$ . Then, in a very fast way, if we wonder how these two currents and two resistors finally separate, we can evidently see how to calculate the current  $i_1$  or the current  $i_2$ . A special case that we can see here, would be if  $R_1$  and  $R_2$  were equal.

Notes

Summary



## Circuits diviseurs de courant

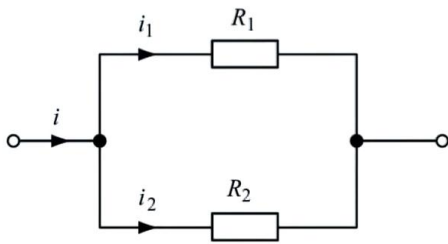

$$i = i_1 + i_2$$

$$U_1 = U_2 = R_1 \cdot i_1 = R_2 \cdot i_2$$

$$i_1 = i \frac{R_2}{R_1 + R_2}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

Electrotechnique I


For example, you take  $R_1$  and  $R_2$  equal to 100 ohms, you will have 100 divided by 200, which will be equal to 0,5, it is then logical that  $i_1$  and  $i_2$  are equal to 0,5 times the current. The current is then divided in a uniform manner on either side of these equal resistors. We can make an analogy with hydraulic circuits. If we have two pipes of same section, so of same hydraulic resistance, with only one tap bringing water, well we will get the same amount of water, an equivalent flow on both sides since the resistance is the same. Another special case that we can see here is the case where  $R_1$  is equal to 0. In such a case, we have a wire on one side and a resistor on the other. Now we have the question then where does the current go? You see straight away here in  $i_1$ .  $i_1$  is equal to  $i$  times  $R_2$  over  $R_2$ . If  $R_2$  is equal to 0, we have 1. This means that all the current  $i$ , whatever the resistor  $R_2$ , if  $R_1$  is equal to 0, all the current goes towards the top and so  $i_1$  is equal to  $i$ ,  $i_2$  is equal to 0.

Notes

Summary



# CONCLUSION

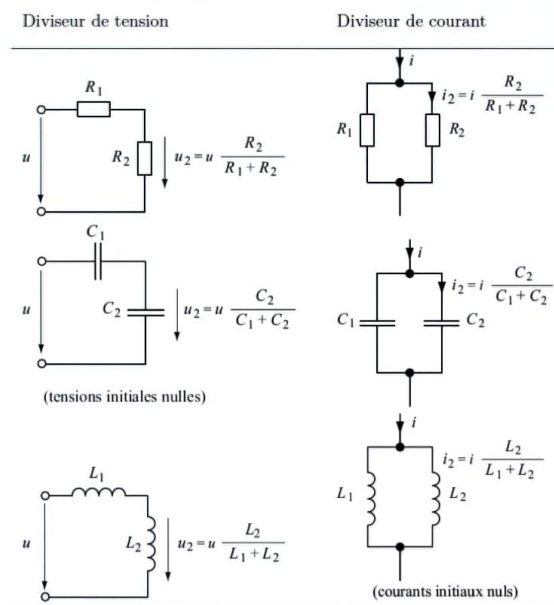

Electrotechnique I

In conclusion, I don't give you here the rules for the capacitive current divider and the inductive current divider, I prefer to give you a recapitulation with voltage dividers, current dividers, with the resistance, the capacitance and the inductance, and so in this table, you have all the necessary elements for the case where these elements appear in a circuit, to faster calculate the current division where you need it, the voltage  $U_2$  or the voltage  $U_1$  in general. Thank you.

Notes

Summary



17m 09s