


## TRANSFORMATION $\Pi$ -T

## LEÇON 10

## Électrotechnique I

Yves PERRIARD &amp; Paolo GERMANO


Laboratoire d'Actionneurs Intégrés

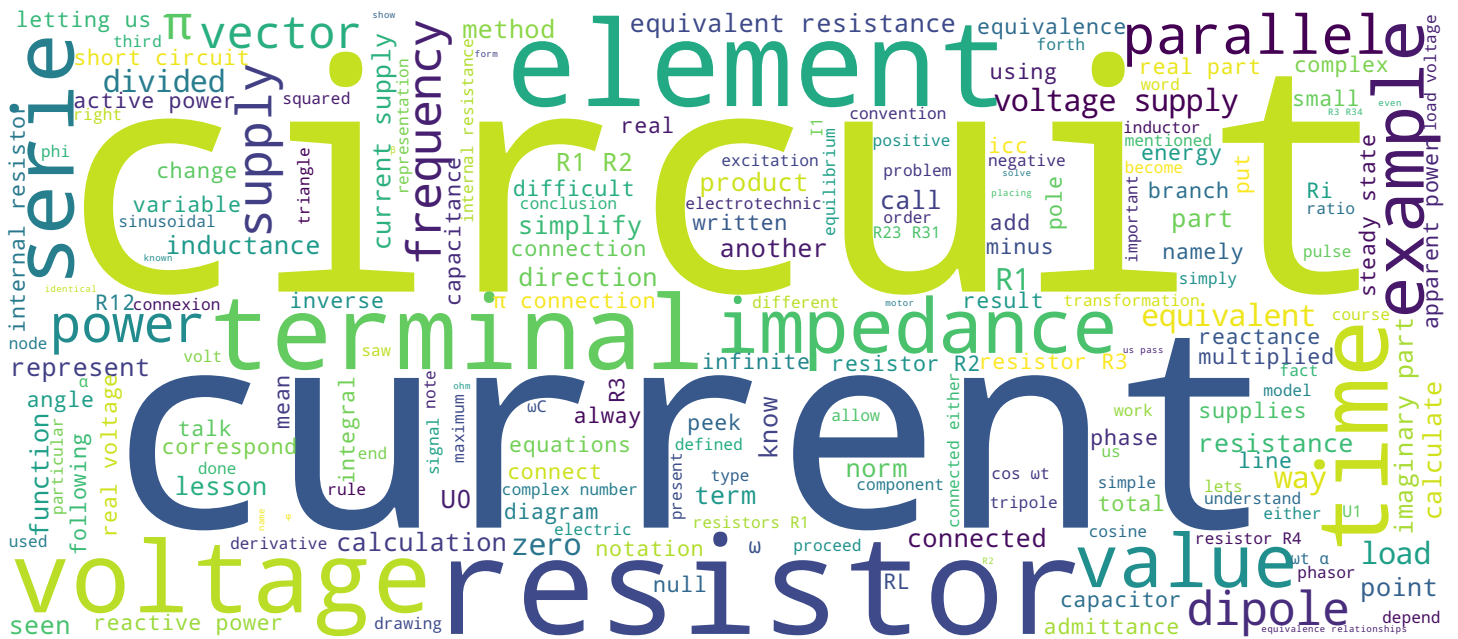

**EPFL**



## Généralités

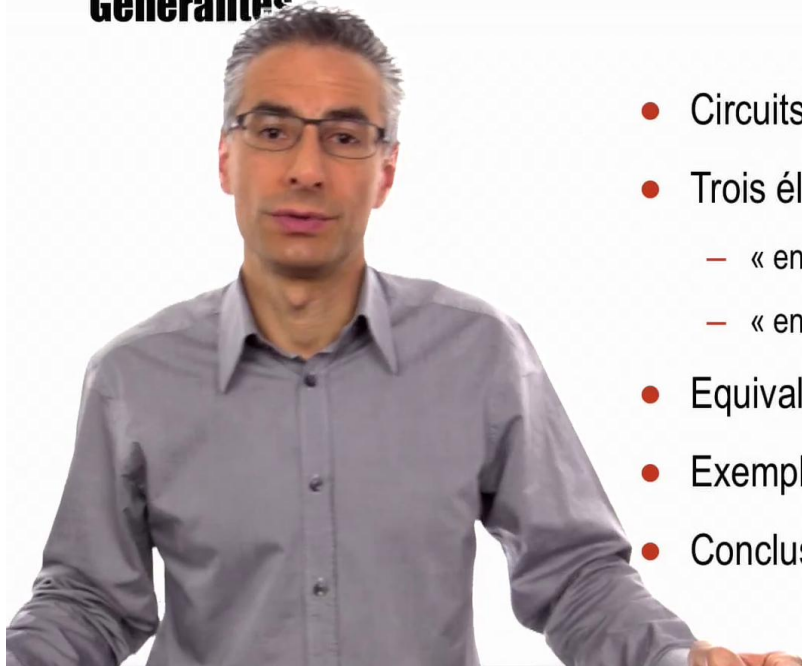

- Circuits particuliers
- Trois éléments (tripôle) connectés
  - « en  $\pi$  », « en triangle » ou « en  $\Delta$  »
  - « en T », « en étoile » ou « en Y »
- Equivalence
- Exemple
- Conclusion

Electrotechnique I

Hello. During this lesson, we will present a method that lets us handle tripoles. We will consider partial circuits composed of three elements. We will first see particular circuits whose element are difficult to combine or to simplify two by two. We will then consider three elements that can be connected either in "pi" or in "T". Then, we will see the equivalence between these two types of circuits in order to easily pass from one to the other and to then simplify the rest of the circuit. We will treat an example and then formulate a conclusion.



Notes

Summary



0m 04s
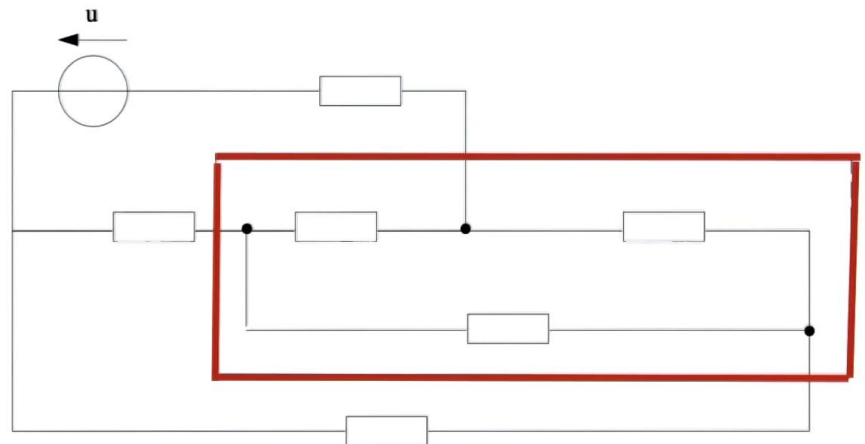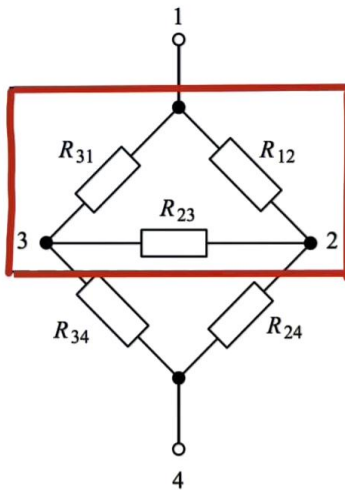
## Exemples de circuits difficiles à simplifier



Electrotechnique I


If we consider these two circuit examples, we can see that they are difficult to simplify. Why? Because if we consider this first circuit, we see that the elements are not in series for  $R_{31}$  and  $R_{32}$ . Why? Because there is an additional current coming here, and so it is more difficult to simplify the circuit. Ideally, for this circuit, that presents about the same topology. We will see a method letting us transform these circuits for simplification later on. We can evidently resolve these circuits by applying Kirchhoff's law at the knots and loops, but we will see a much simpler method.

Notes

Summary


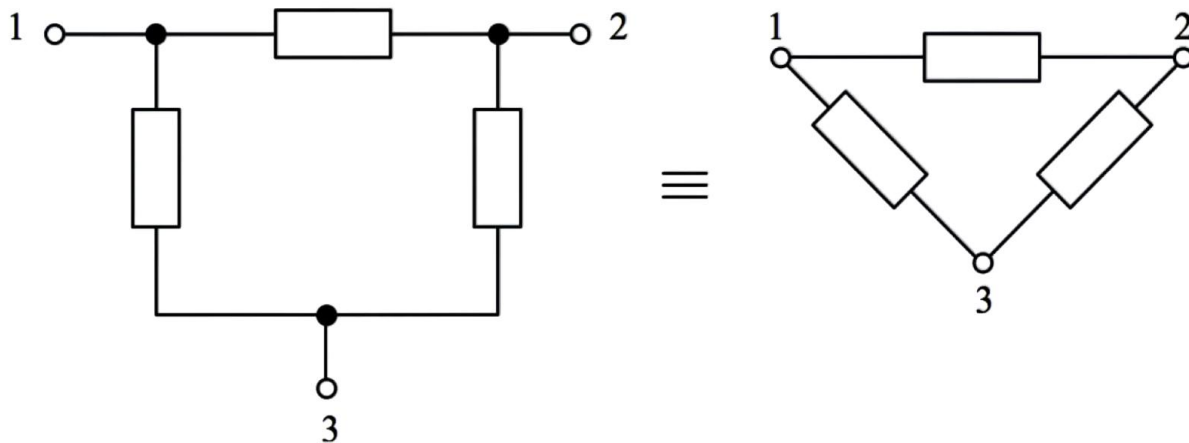
## Tripôles « en $\pi$ » ( ou « en triangle », « en $\Delta$ » ou « *Delta connection* » )



Electrotechnique I

Three elements can be connected between them in two ways. First way, is a " $\pi$ " connection such as represented in the first figure. We understand this notation because the circuit looks like a capital  $\pi$ . If we represent this same connection, drawn a little differently, we see that it resembles a triangle, which is why we also talk of "delta" connection. We also use this notation, the greek delta  $\Delta$  and in French literature, we rather talk of a connexion en triangle.


Notes

Summary



1m 40s
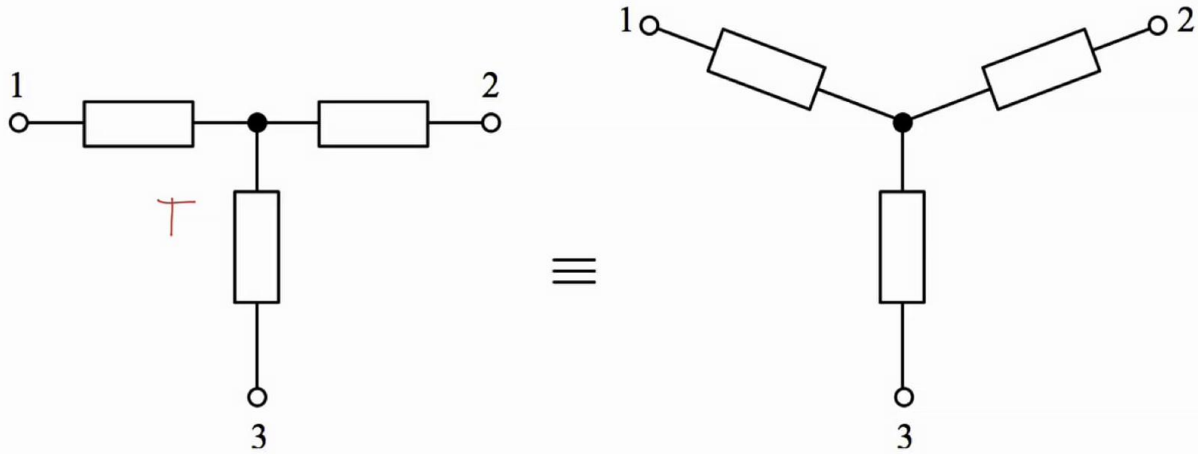
## Tripôles « en T » ( ou « en étoile », « en Y » ou « *Star connection* » )




Electrotechnique I

The second method to connect three elements between them is the "T" connection. On this drawing, we easily understand why we give it such a name, because the connection resembles the letter T. We also call it a "Y" connection or a "star" connection. On this drawing, we see that the same equivalent drawing resembles a Y shape. In French, we talk about "connexion en étoile".

Notes

Summary

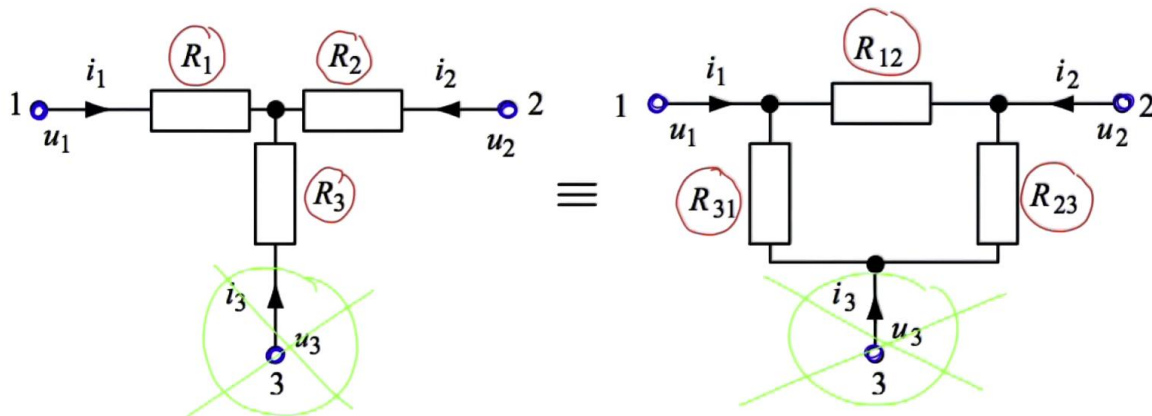

Équivalence de tripôles « en T » et « en  $\pi$  »


Electrotechnique I

On this drawing, we represent the two connections: either in "T", or in " $\pi$ ". We see that they are tripôles with a first pole here, a second pole and a third pole. On the second representation, we find these same poles. Between these tripôles, we connect the three elements, three resistors in this example as it happens. In T, we have a resistor  $R_1$  connected to the terminal 1; a resistor  $R_2$  connected to the terminal 2; a resistor  $R_3$  connected to the terminal 3. In delta or in  $\pi$ , we once again have three elements:  $R_{1-2}$  which is connected at the terminals 1 and 2, and so forth, the resistor 2-3 is connected at the terminals 2 and 3 and the resistor 31 is connected at the terminals 3 and 1. What we would like to do here, is find an equivalence between the resistors  $R_1$ ,  $R_2$ ,  $R_3$  and the resistors  $R_{12}$ ,  $R_{23}$ ,  $R_{31}$  so that both circuits are identical. To do so, we will proceed in the following manner: let's first consider that this terminal 3 doesn't exist, and we will write the equation of the resistance seen at the terminals 1 and 2 so that they are equivalent. We can write that, here, the equivalent resistance, they are in series since we deleted the terminal number 3,  $R_1 + R_2$  must be equal to this equivalent resistance in the  $\pi$  connection at the terminals 1 and 2.

Notes

Summary

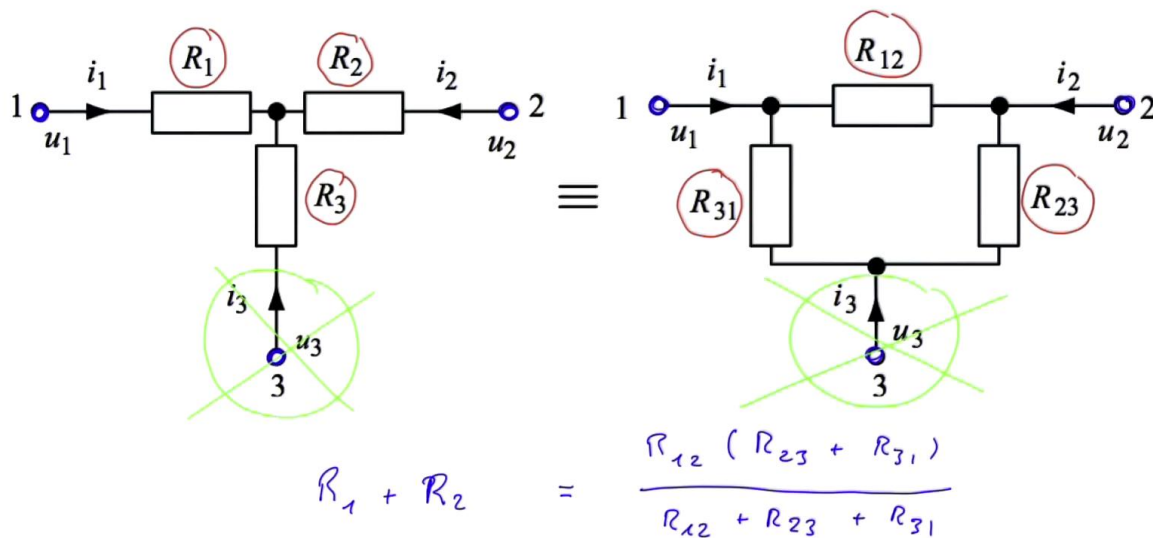

Équivalence de tripôles « en T » et « en  $\pi$  »


Electrotechnique I

And we see that these two resistors are in series, since this terminal is cancelled out, this equivalent resistance is in parallel with the resistor  $R_{12}$ . So we can write that the equivalent resistance is: the product of this resistor over the sum of these two divided by the sum of this resistor over the sum of these ones. We then write that  $R_{12}$  multiplied by  $R_{23} + R_{31}$  divided by the sum of these three resistors needs to be equal to  $R_1 + R_2$ .

Notes

Summary



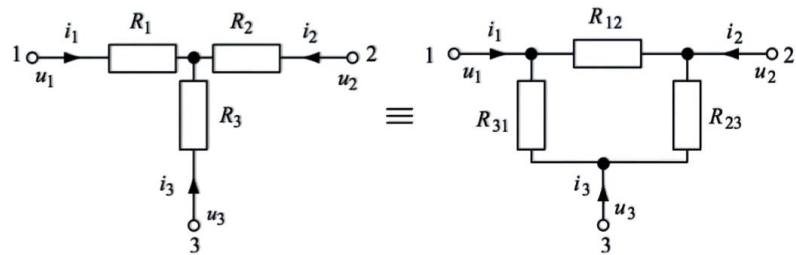

$$R_1 + R_2 = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

$$R_2 + R_3 = \frac{R_{23}(R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

$$R_3 + R_1 = \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}}$$

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23}R_{31}}{R_{12} + R_{23} + R_{31}}$$

Electrotechnique I


We repeat, here, the result obtained for the first equation and if we proceed in an identical way for the boundary pairs 2 and 3, and 3 and 1, we get two extra equations. We are not making the development, but the method is the same. Two supplementary equations, that give a system of three independent equations with three unknowns, from which we easily extract the equivalence relationships that let us replace a circuit in  $\pi$  with a circuit in T. We just need to do the sum of these three equations. So, let's take 0.5 times the first equation, minus equation 2, plus equation 3. Having done all calculations, we fall on this system of three equations letting us pass from one circuit to the other. The resistor linked to the terminal 1 of the circuit in T is the product of two resistors linked to the terminal 1 of the circuit in  $\pi$ , so  $R_{12}$  and  $R_{31}$  here, divided by the sum of the three resistors. And so forth for the resistors  $R_2$  and  $R_3$ .

Notes

Summary



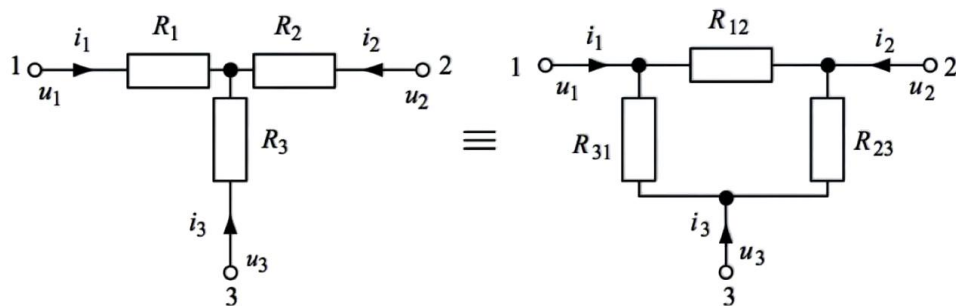

Équivalence de tripôles « en T » et « en  $\pi$  » - Opération inverse

$$R_{12} = R_1 + R_2 + R_1 R_2 / R_3$$

$$R_{23} = R_2 + R_3 + R_2 R_3 / R_1$$

$$R_{31} = R_3 + R_1 + R_3 R_1 / R_2$$

$$= \frac{R_1 R_3 + R_2 R_3 + R_1 R_2}{R_3}$$

Electrotechnique I


By doing a similar calculation at the terminals pair when the third one is disconnected, we get the equivalence relationships that let us replace the elements of a circuit in T by a circuit in  $\pi$ . These equations written in a slightly different manner give the ratio of T double vector product of two resistors taken two by two  $R_1 \times R_3 + R_2 \times R_3 + R_1 \times R_2$  divided by the resistor  $R_3$ .

Notes

Summary



## Exemple

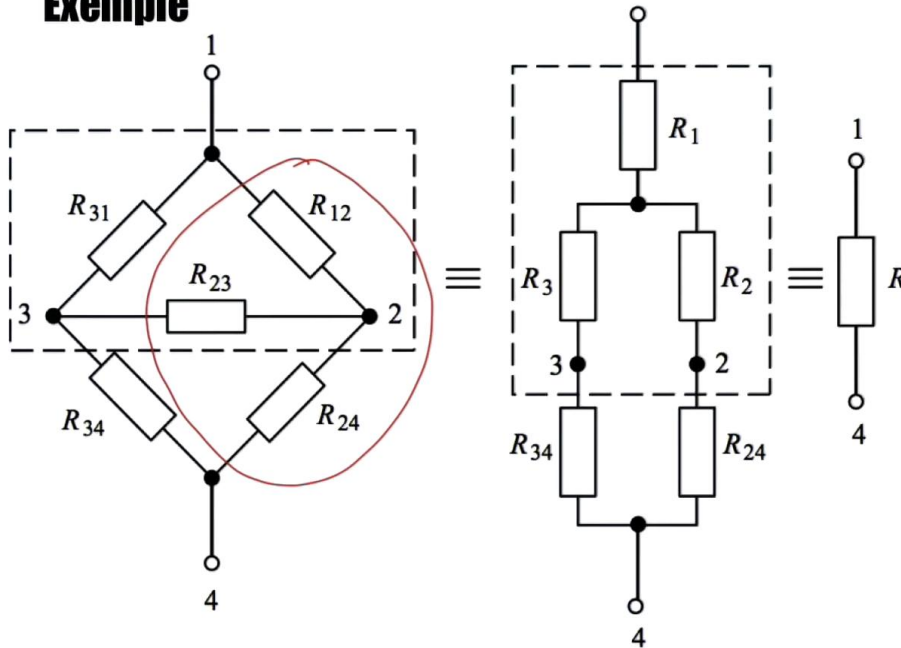

$$R = R_1 + \frac{(R_2 + R_{24})(R_3 + R_{34})}{R_2 + R_{24} + R_3 + R_{34}}$$

Electrotechnique I

Let take the example that we mentioned at the very beginning of the lesson. If we consider this circuit, with this tripole composed of three resistors, well we can favourably replace it by this equivalent circuit from which we can calculate the resistors  $R_1$ ,  $R_2$  and  $R_3$ , by using the equations that we developed, namely the transformation from T to  $\pi$ . It then becomes easy to calculate the equivalent resistors since the resistor  $R_3$  and the resistor  $R_4$  are in series. The resistor  $R_2$  and the resistor  $R_4$  too, that are in parallel, and that we can put in series with  $R_1$ . We obtain the result for the equivalent resistance of the whole circuit that is equal to  $R = R_1 +$  these two equivalent resistances in parallel, so their product over their sum. The product of these two resistors in series gives  $R_2 + R_{24}$  multiplied by  $R_3 + R_{34}$  divided by the sum of these two equivalent resistances, namely  $R_2 + R_4 + R_3 + R_{34}$ . This is the final result. Lets also note that we could have seen the problem differently by considering this time these three elements, here, which are three resistors connected in T and that we could have transformed in  $\pi$  and also easily simplify the circuit. We won't do the calculation here.

Notes

Summary



7m 17s



- Tripôles
- Passage :  $\pi \rightarrow T$  ou inverse
- Importance pour les systèmes triphasés

Electrotechnique I

There, we have considered the case of three elements that are connected either in  $\pi$ , either in T at its three boundaries. We have the equivalence letting us pass from a  $\pi$  connection to a T connection. All this in the aim of simplifying this circuit and continuing to reduce it. We will see that this method is very important for three-phase systems that we will cover in the next semester.

Notes

Summary



9m 28s