



## Généralités



- Lieu géométrique dans le plan complexe
  - Impédances  $Z_R$ ,  $Z_L$  et  $Z_C$
  - Représentation graphique – Sommes vectorielles
  - Dépendance de la fréquence – Lieu complexe
  - Exemple
  - Calcul du courant en fonction de la fréquence
- Conclusion

Electrotechnique I


Hello. Welcome to this new lecture of the Electrotechnics course. So far, we have studied many aspects of an electrical circuit but always with a power supply either in DC steady state, or at a certain frequency, eventually at multiple frequencies but simultaneous, it was the case of the principle of superposition. We will see how a circuit behaves over a big range of frequencies. Today we will start by defining what a geometric locus is, then we will see the behaviour of an impedance while varying one of its parameters, in this instance, the frequency, we will see an example, and finally we will look at the current in the circuit, because if we change the impedance the current will also change, we will then compute the current as a function of the frequency.

Notes


Summary



## Lieux géométriques

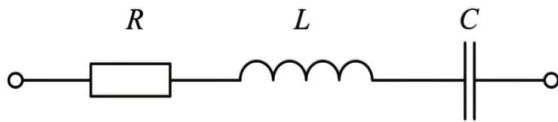
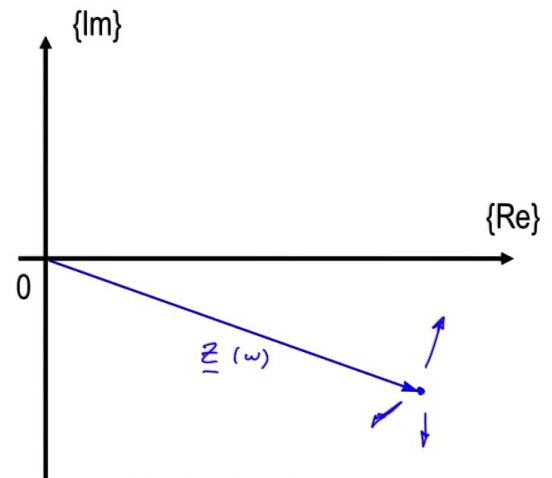
$$\underline{Z} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$



Déf. : Lieu complexe relatif à une grandeur complexe quelconque :  
Lieu ou (courbe) décrit par l'extrémité du vecteur représentant  
cette grandeur lorsqu'on fait varier un paramètre du réseau ( $\omega$ )

Electrotechnique I


We start then by a definition, the definition of the complex domain. We call complex domain relative to any complex variable, here it would be the impedance  $Z$ , thus any complex variable, the location, or the curve, the path, described by the extremity of the vector representing this variable when we vary a parameter of the network, usually it is the pulsation, the frequency, but it could be the resistor, the inductance or the capacitor. And today, we will only look at the pulsation. For a given circuit, for example this RLC circuit in series, we can write the expression of its total impedance that has a real part and an imaginary part. We can represent it on the complex plane. We have here  $Z$ .  $Z$  of  $\omega$ . And we would like to know how varies this extremity of the vector  $Z$  when we move, modify the frequency. For a given circuit, powered by an AC supply, the goal is to compute the curve covered here by the total impedance when we vary the frequency.

Notes

Summary



## Lieux géométriques

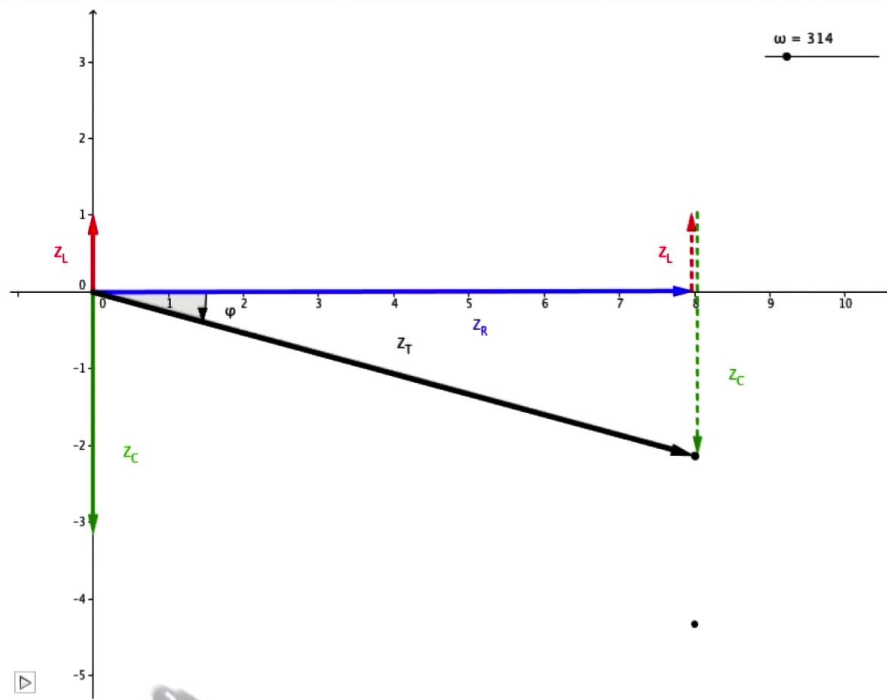

Electrotechnique I

So in the given example, the RLC circuit in series, we are facing three components, because there are three elements. We have the impedance  $Z_R$  which is equal to  $R$ , which doesn't depend on the frequency. We have the component  $Z_L$  here.  $Z_L$  which is equal to  $j\omega L$ . And the last component  $Z_C$ .  $Z_C$  is equal to  $-j(1/\omega C)$ . The two impedances  $Z_L$  and  $Z_C$  are not dependent on the frequency  $Z_C$ , the inverse of the frequency, and  $Z_L$  is proportional to the frequency. To get the total impedance of the circuit we will conduct a sum, since they are in series, these three impedances. Therefore, the sum of these three impedances, using the property of the vector addition, we have this first impedance  $Z_R$  to which we will add  $Z_L$ , which is represented here, We add and we add again  $Z_C$  which is negative in order to get the total impedance. This total impedance has a norm and an angle, a phase shift, with respect to the real axis and the end of this vector is given here for a frequency of, for example here,  $\omega$  equal 200 radians per second. If now we change this frequency value and raise it, that's it, we are here at  $\omega$  equals 314 radians per second. We see that  $Z_L$  increased slightly, and linearly with  $\omega$  because  $Z_L$  is  $\omega L$ .


Notes

Summary



2m 37s

## Lieux géométriques

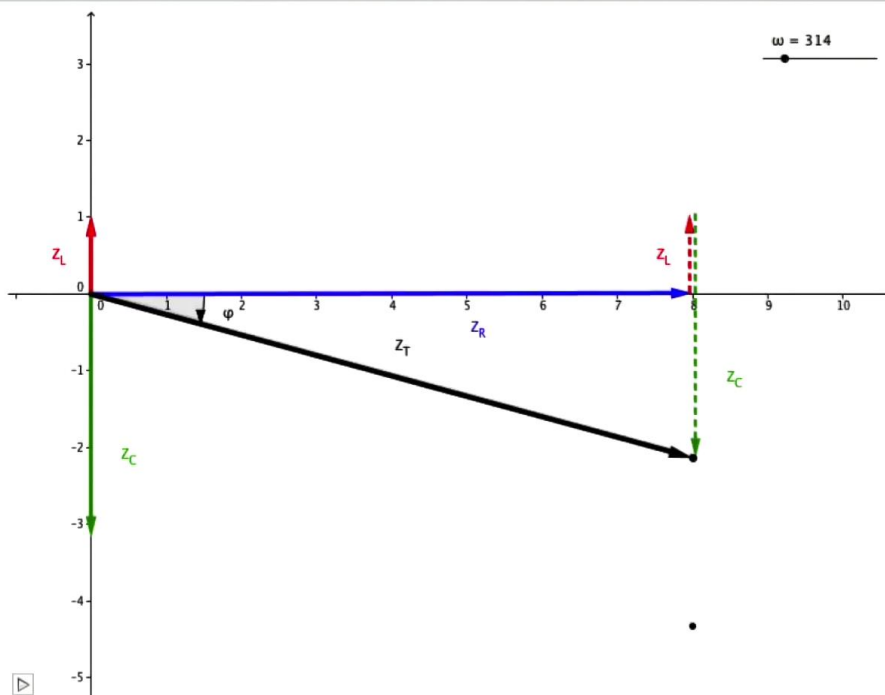

Electrotechnique I


$Z_C$ , has decreased because its expression is  $1 / \omega C$ , and then the final result, the sum of these three vectors, give a new point here for  $\omega$  equals 314 radians per second, a new point that corresponds to the new norm and a new phase shift of the impedance with respect to the real axis.

Notes

Summary



## Lieux géométriques

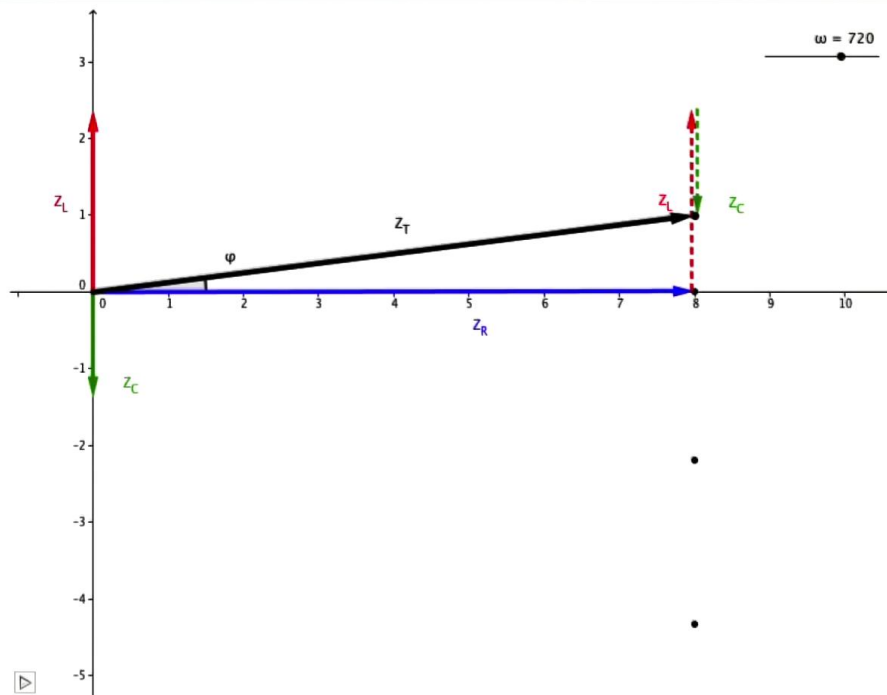

Electrotechnique I

If we increase again the frequency, we have increased once again the frequency or the pulsation, this time we are at 550 radians per second. We see that  $Z_L$  has again increased and  $Z_C$  decreased in order to end up with a value so that both offset each other and we end up here with a total impedance, this point here, at 550 radians per second, a total impedance purely resistive. We will threat this particular case in the next lecture. Increasing again the frequency, this time we have omega which is at 720 radians per second for example, so  $Z_L$  becomes bigger than  $Z_C$ . Thus the nature of the impedance has become inductive, with a positive reactive part, whereas until now it was capacitive.


Notes

Summary



4m 56s

## Lieux géométriques

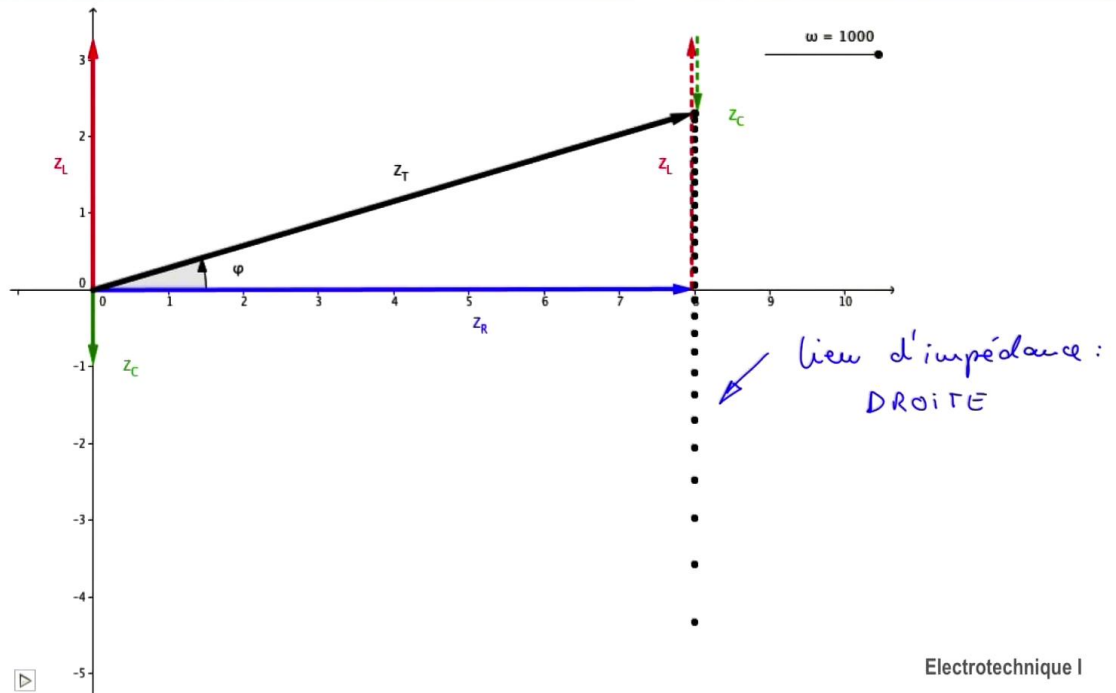

Electrotechnique I

And increasing again the frequency we finally get a total impedance,  $Z_T$  which this time even more inductive than before and see our spot, namely the curve described by the end of the vector  $Z$  as a function of the frequency, that is taking shape. I represent it but for more values of  $\omega$  and we see that the spot of our impedance which is a RLC circuit in series is finally a straight line. This straight line goes from minus infinity to plus infinity on the imaginary axis, when the pulsation is null we have in fact the term  $1/\omega C$  which goes to infinity and when the frequency is infinite we have the term  $Z_L$  that is worth  $\omega L$  and tends to infinity.

Notes


Summary



5m 55s

## Lieux géométriques

## Exemple

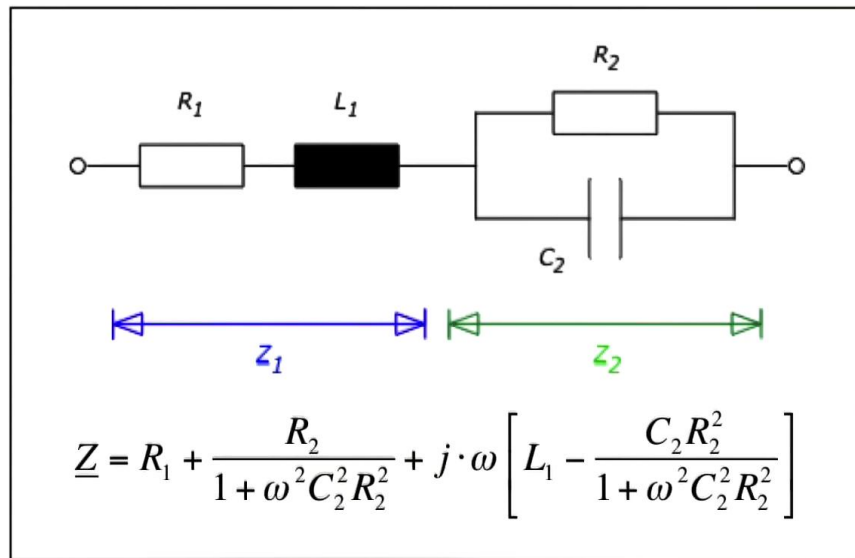

Electrotechnique I

That's it, we will work on a concrete case. We will take this circuit example where we see we have a resistor in series with an inductance, and all in series with a resistor in parallel with a capacitor. So we will define this first part as  $Z_1$  and this second part as  $Z_2$ . These two impedances,  $Z_1$  and  $Z_2$ , are in series. That's it, we can write the equivalent impedance of all this circuit, of all these impedances in series. We see that we have a term that corresponds to  $Z_1$  with its part, here, resistive,  $R_1$ , and the reactive part,  $j\omega L_1$ . Then for the  $Z_2$  part, you can refer to the table that we've given you in the previous lectures, but we can rewrite the real part, here, of this impedance as being this plus the reactive part which is equal to  $j\omega$  times this term here. Now, we would like to compute or determine the place of the impedance  $Z$  when we vary the pulse, the frequency,  $\omega$ . The result, we give it to you in the following slide.

Notes


Summary



7m 04s



## Lieux géométriques Exemple

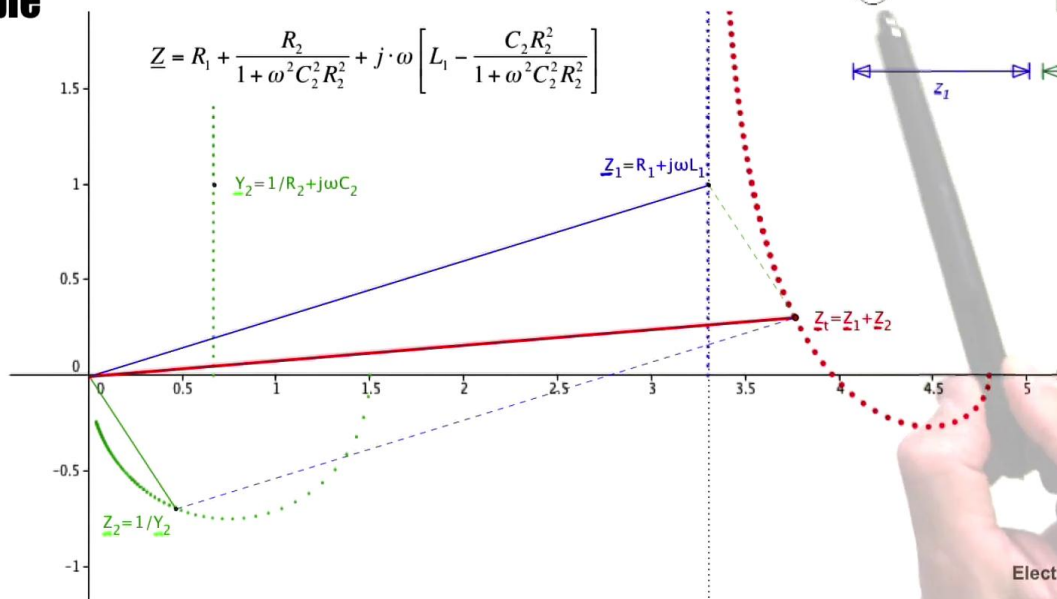

We have here this result that i will comment. So we represent here the impedance  $Z_1$  and the impedance  $Z_2$ . The first impedance here,  $Z_1$ , is given by, here, this  $Z_1$  which has a real part and an imaginary part, it is this term  $R_1$  plus  $j\omega L_1$ . A small remark because of the software i use that is not able to underline, we have actually to write correctly this equation, we have to underline here the  $Y_2$ , the  $Z_2$  times all the impedances, even these ones to be correct. Thus I said that the first part here of the impedance  $Z_1$ , which corresponds to this term  $R_1$  and this term  $j\omega L_1$ , indeed, we find it here if we vary the frequency from zero to infinite. This term does not vary, we still have  $R_1$  which is this point here, and the impedance will increase gradually with the increase of the frequency, it's the term  $j\omega L_1$ , of a resistor and an inductance in series, it is a straight line that tends from zero to  $j$  infinity.


Notes

Summary



8m 30s

## Lieux géométriques Exemple

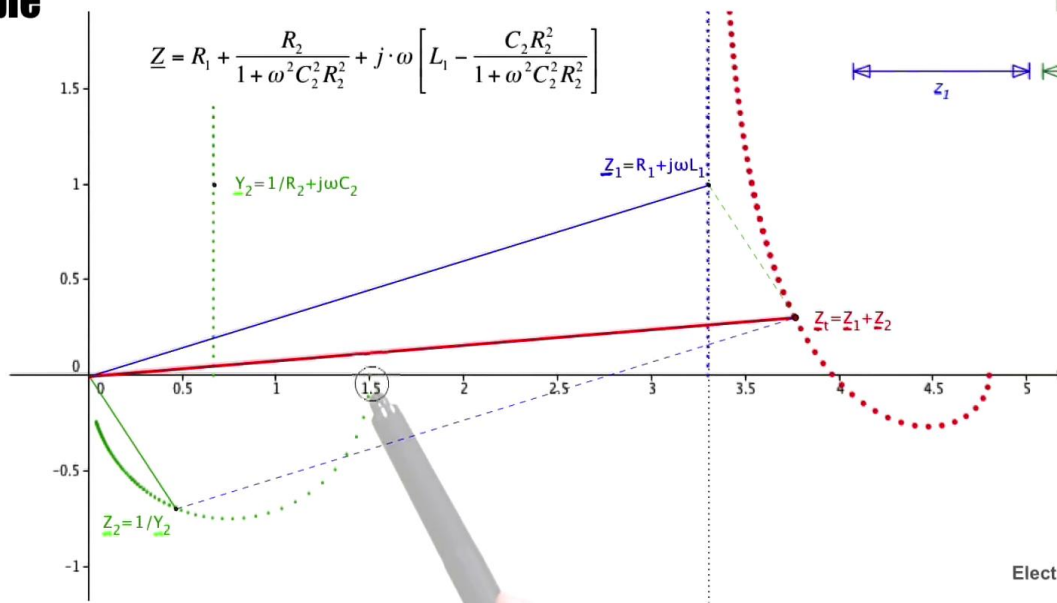


Now for the second part of the circuit, the impedance  $Z_2$  here, we can advantageously use the admittances, because we know that the parallel admittances can be added, and it allows us to describe the location of  $Y_2$ , that is to say that  $Y_2$  is the sum of these two admittances, the admittance of  $R_2$  is here, it is  $1/R_2$ , it is the inverse, and the admittance of  $C_2$  it is  $j\omega C_2$  and we see that this term here, these terms, are very similar to these two terms here, something constant for the real case, we have this term here,  $1/R_2$ , and we add an imaginary term which is proportional to the frequency. It also gives us a place, here, which is half-right that goes from  $j$  null to  $j$  infinite. So we can do the mathematical demonstration but we will not do it here. Making the mathematical demonstration that the inverse of a line in the complex plane, so that goes from  $j0$  to  $j$  infinite, from the zero imaginary part to an infinite imaginary part, is a semicircle. So the image or the inverse of a straight line is a semicircle that starts from this value here for  $\omega$  equals to zero and tends to this value here.

Notes

Summary



## Lieux géométriques Exemple

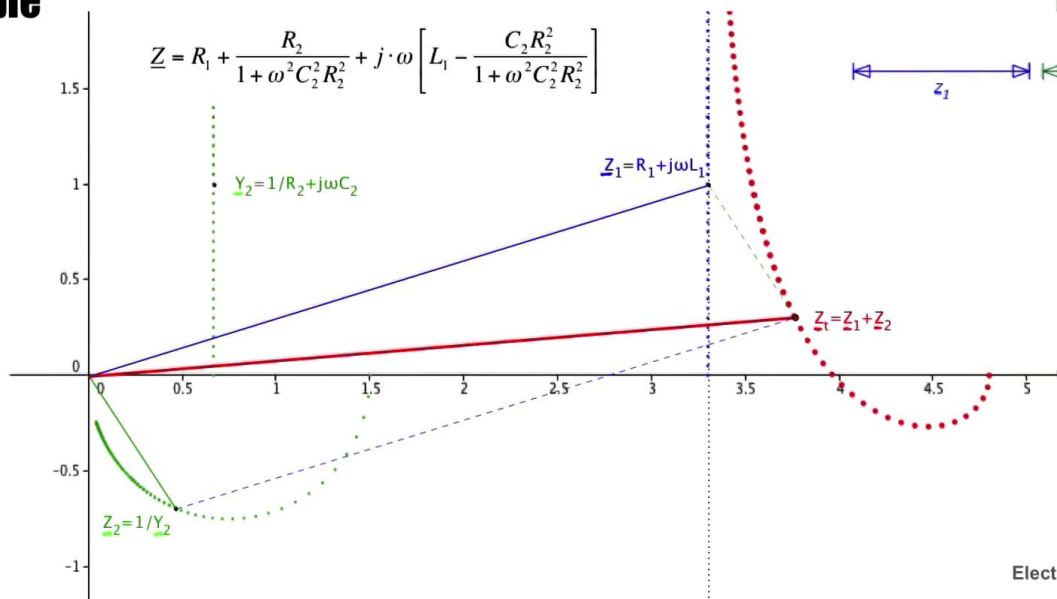


To get the final result, one must add the impedance  $Z_1$ , is this place here, and this impedance  $Z_2$  we found in doing the opposite of this straight line here, it's this semicircle here, the sum of the two, is this impedance plus this one, which is here, which gives this result:  $Z_1$  plus  $Z_2$ . The sum of these two impedances for  $\omega$  equals zero, we go from this point here where we have the sum of  $R_1$  plus  $R_2$ . And increasing the frequency, first we will be negative, which means capacitive, because at low frequency the impedance  $Z_2$  is very high, it is capacitive. So we will first be capacitive, we arrive at a particular value where we are purely resistive and when the frequency increases further, we will become very inductive to follow this curve here.

Notes

Summary


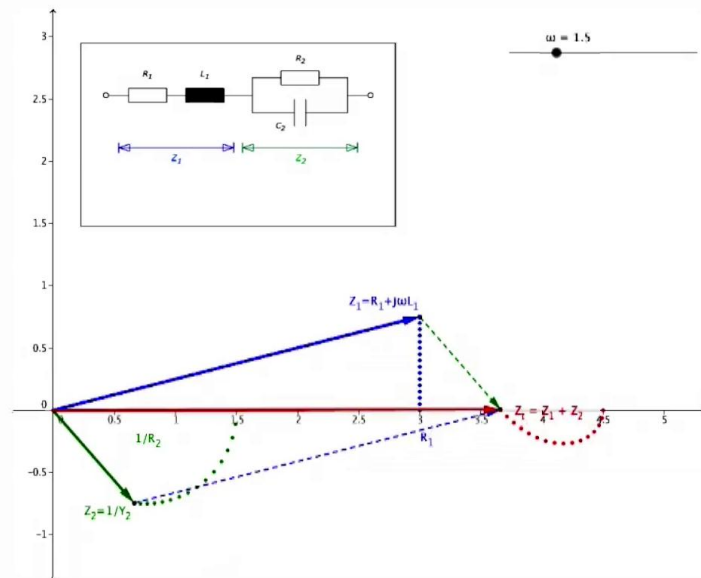
## Lieux géométriques Exemple animé $0 < \omega < \omega_{\max}$



Electrotechnique I

So, we start with a total impedance value for a frequency, a pulsation, null from this point here. We have actually the sum of the two resistors  $R_1$  and  $R_2$ . Why? Because  $j\omega L_1$  is null and  $1/\omega C$  is infinite, So we have an open circuit here. Instead of  $C_2$  we have only  $R_1$  plus  $R_2$ , it is this starting point.


Notes

Summary



12m 37s
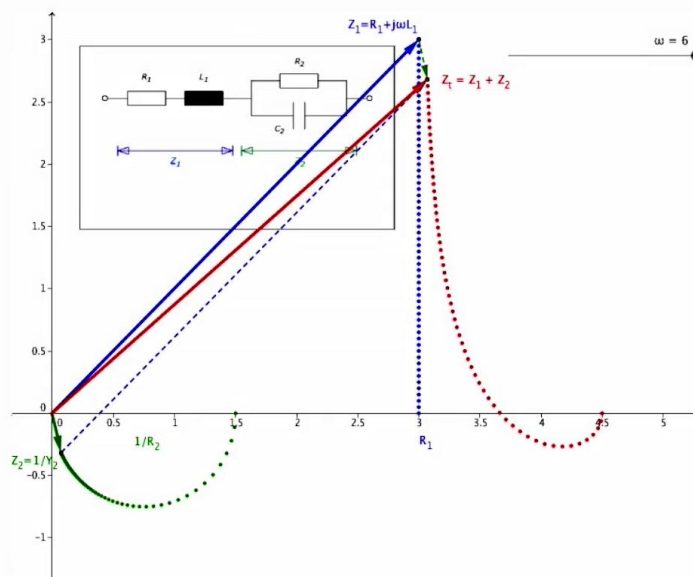
## Lieux géométriques Exemple animé $0 < \omega < \omega_{\max}$



Electrotechnique I

That's it, i launch the video and we see that the impedance is first capacitive, resistive, and she becomes more and more inductive progressively as the frequency increases.


Notes

Summary



13m 02s
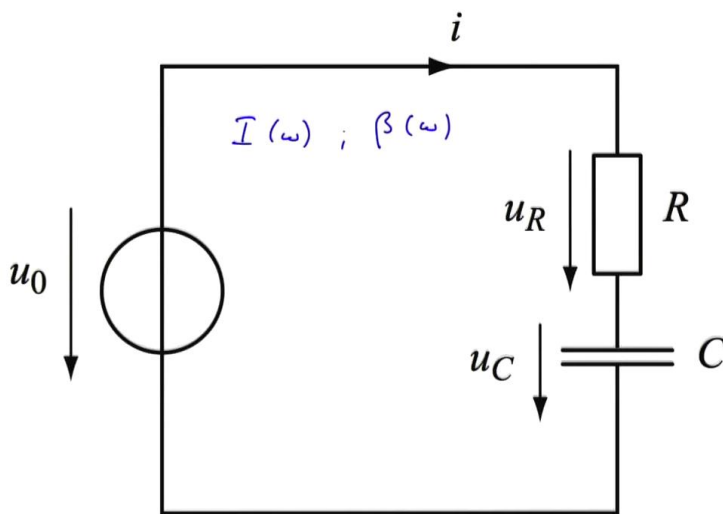
## Dépendance de la fréquence – Exemple pour un circuit RC série



$$\underline{Z} = R - j \frac{1}{\omega C} \rightarrow Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$\varphi = \arctg \frac{-1}{\omega C R}$$

$$\underline{I} = \frac{\underline{U}_0}{\underline{Z}}$$

Electrotechnique I


We have seen what happens at the impedance, at its norm, at its phase in the complex plan when we increase the frequency of the circuit. We will now, for this example given here, get interested in the current, namely, its norm and its phase, once again depending on the frequency. So we try to compute  $I$  of  $\omega$  and  $\beta$ , the current argument. So to know the current which passes through the circuit, we need, knowing here the supply voltage  $U_0$ , we need to know the impedance here of the RC circuit in series. So we can write that  $Z = R - j(1/\omega C)$  and then that its norm is equal to, by Pythagoras, to the real part squared plus the imaginary part squared. So we have that the norm of  $Z$  it is  $\sqrt{R^2 + (1/\omega^2 C^2)}$ . This is the norm. Now the phase shift. The phase shift of the impedance, it is given by the arc tangent of the imaginary part over the real part, namely the imaginary part  $1/\omega C$  divided by the real part  $R$ . That's it, we have completely defined here the impedance  $Z$ , and now to compute the current. The current is given by the ratio of  $u_0$  to  $Z$ . So, if I express  $u_0$  in function of the argument, we have  $u_0$  times  $e^{j\alpha}$ , usually we put  $\alpha$  equal to zero, and the impedance  $Z$  which is given by the norm we have just computed multiplied by  $e^{j\varphi}$ .

Notes

Summary


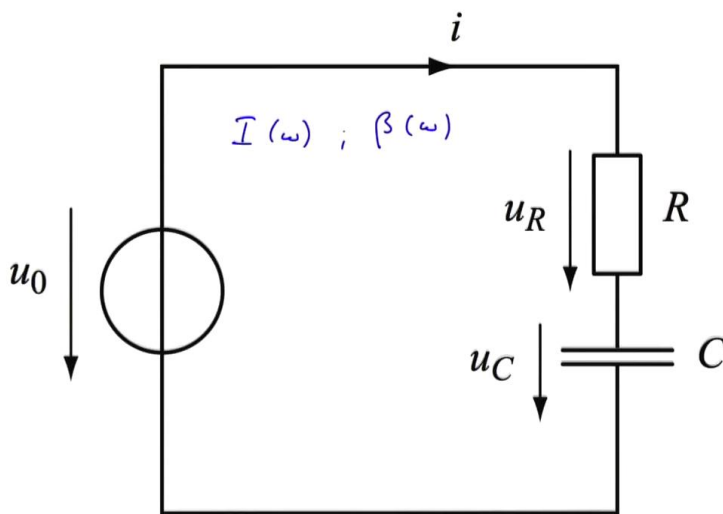
## Dépendance de la fréquence – Exemple pour un circuit RC série



$$\underline{Z} = R - j \frac{1}{\omega C} \rightarrow Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$\varphi = \arctg \frac{-1}{\omega C R}$$

$$\underline{I} = \frac{\underline{U}_0}{\underline{Z}} = \frac{U_0 \cdot e^{j\alpha}}{Z \cdot e^{j\varphi}} = \underbrace{\frac{U_0}{Z}}_I \cdot \underbrace{e^{j(\alpha - \varphi)}}_{\beta}$$

Electrotechnique I


From this equation we can write the norm of the current, which is  $u_0$  over  $Z$ , multiplied by  $e^{j(\alpha - \varphi)}$ . With identification, we have that this term here is the norm of  $I$  and this term here, is the argument of  $I$ , it is  $\beta$ .

Notes

Summary




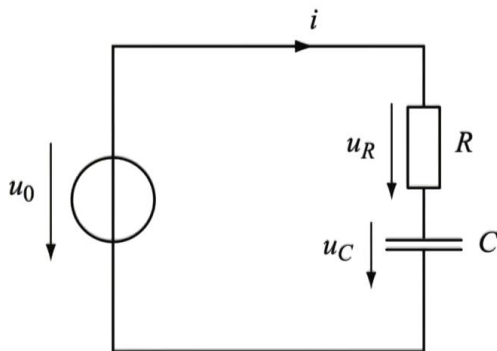
## Dépendance de la fréquence – Exemple pour un circuit RC série



$$\omega = 0 \Rightarrow I = 0 \quad \beta = \pi/2$$
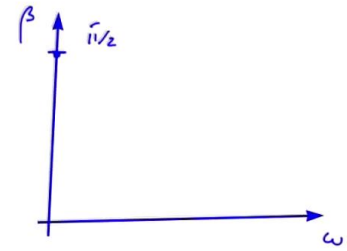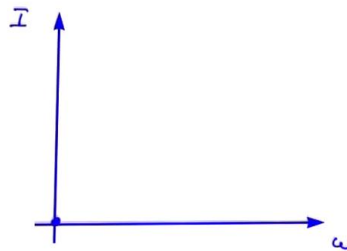
$$I = \frac{u_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \quad ; \quad \beta = -\varphi = \operatorname{atg}\left(\frac{1}{\omega RC}\right)$$



Electrotechnique I

We can express the norm of  $I$ , we develop. We have that  $I$  is  $u_0$ , the supply voltage, divided by the norm of  $Z$ , namely  $R^2 + (1/\omega^2 C^2)$ , and the angle  $\beta$ , the argument of the current, it is given by  $-\varphi$ , namely tangent arc of  $1/\omega RC$ . We will analyse now these two functions, the norm of  $I$  and the argument of  $I$  in function of  $\omega$  and we will represent them in a plan  $\omega$  is the variable we would like to represent. We will first represent the norm of  $I$  in function of  $\omega$ . And the argument of  $I$  in function of  $\omega$ . For a pulsation  $\omega$  equals zero, we have that  $I$  is equal to zero. why? Because this term becomes very big and then the ratio of  $u$  over something very big is equal to zero. So for a null pulsation, we have a norm of the current that goes from this point here. Concerning the phase, we have that  $\beta$  is equal to  $\pi$  over 2. Why? Because the vector  $Z_C$  is infinite as long as  $\omega$  is equal to zero, therefore the norm of  $C$  is infinite and we have an angle of minus  $\pi$  over 2. and since  $\beta$  is equal to minus  $\varphi$ , we go from this value that worth  $\pi$  over two for a null frequency. In contrast, when the pulsation is infinite, the current tends to a value that is  $u_0/R$ .


Notes

Summary






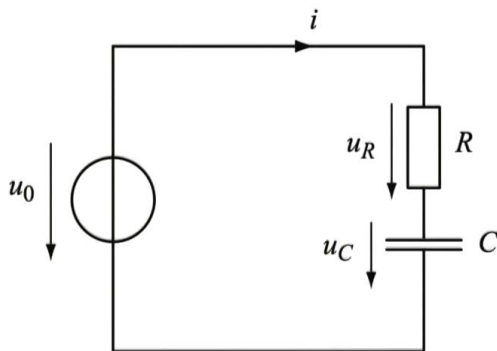
## Dépendance de la fréquence – Exemple pour un circuit RC série



$$\begin{aligned} \omega = 0 & \Rightarrow I = 0 \\ \omega = \infty & \Rightarrow I = \frac{U_0}{R} \end{aligned}$$

$$\begin{aligned} \beta &= \pi/2 \\ \beta &= 0 \end{aligned}$$
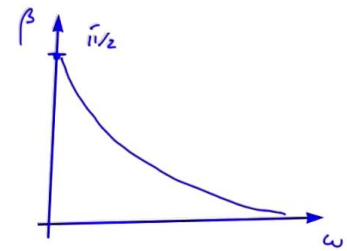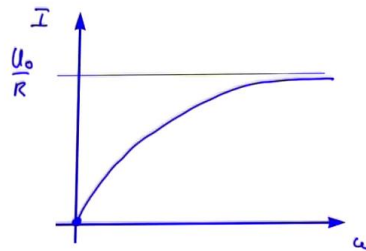
$$I = \frac{U_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} ; \quad \beta = -\varphi = \operatorname{atg}\left(\frac{1}{\omega RC}\right)$$



Electrotechnique I

We see that in this equation. The pulsation being infinite, this term is equal to zero and we have then  $u_0/\sqrt{R^2}$ , is  $u_0/R$ . The current, when  $\omega$  equals infinite, tends to  $u_0/R$ . In between, we will increase that way. For the argument of the current,  $\beta$  at infinite equals zero. Why? Because for an infinite value, the capacitor behaves as a Short Circuit and this term here tends to zero. The curve of the argument goes from  $\pi/2$  and tends to zero for  $\omega$  equals infinite. We have completely defined the behavior of the current which passes through the circuit as a function of the frequency in terms of the norm and the argument. Thus a steady-state capacitor acts as an impedance infinite, then no current. We are at this point here.

Notes

Summary





- Définition et construction d'un *lieu géométrique*
- Un circuit peut changer de nature selon la fréquence à laquelle il est alimenté
- Supprimer la partie réactive d'une impédance
- Supprimer la puissance réactive
- Étudié le courant dans un circuit en fonction de la fréquence

Electrotechnique I

And a capacitor at an infinite frequency behaves as a short-circuit and then we only have the resistive part We have defined and built the geometric locus of an impedance, here in function of the frequency, but we could also have done it in function of  $R$ ,  $L$  or  $C$  for example if we wanted to take into account the aging of the components where  $R$ ,  $L$  or  $C$  may change, or in function of the load that would be put in this circuit. We have seen that a circuit could change in nature depending on the frequency to which it is supplied, so either capacitive, purely resistive or inductive, and there is a particular value for which it is purely resistive, that is what we will see in the next lecture. We have seen that it is possible to delete the reactive part of an impedance but this is only possible at one given frequency. Consequently, one can also remove the reactive power in a circuit combining the element  $L$  and the element  $C$ . Finally, we have seen that if the impedance  $Z$  changes with the frequency, the current also changes with the frequency, we have shown how it evolves in terms of its norm and its phase shift as a function of the frequency. Thank you for your attention.

Notes

Summary



19m 19s