





- Introduction
- Amplificateur à charge passive ou active
- Polarisation, couplage et découplage des signaux AC.
- Amplificateurs de tension
- Amplificateurs suiveurs de tension

Electronique II

Good morning everyone. Today we will start a chapter which will open the door on the synthesis of amplifiers. So to begin that study of amplifiers, first we will pass on something called the passive and active charge. So we'll just make the difference between a passive charge that you know very well, a resistance and an active charge that will be the transistor. Once you understand that difference, we can move up in the structure of the amplifier we just quickly revisit the polarization to fix the ideas, we have a look at the diagrams, the models we have already done in previous chapters quickly like that to see the structure and the different steps for realise an amplifier before addressing the voltage amplifiers. And there, we take the time to analyze the voltage amplifiers with passive charge and with active charge and after we pass to push the characteristics of these amplifiers to get the best bandwidth or increase the gain before analyzing the so-called voltage plus followers more later we will see the differential amplifiers. And all that I tell you now will lead us to achieve the famous operational amplifier and we will see that by putting cascaded stages we get the operational amplifier.


Notes

Summary





0m 07s

# Charge passive et charge active

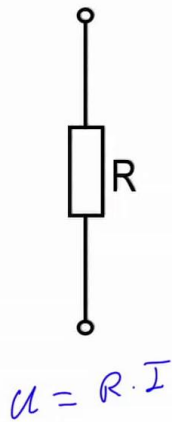

$$u = R \cdot I$$

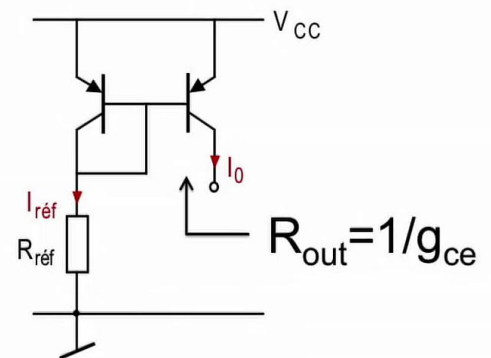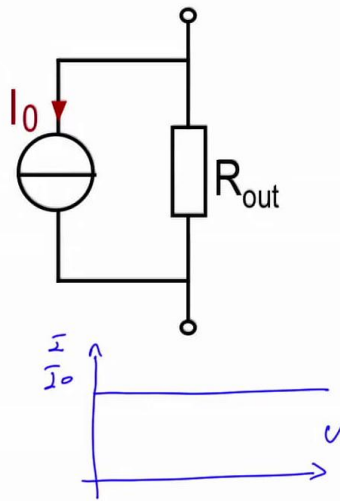

Electronique II

Just to remind you what a charge is. We know that a passive charge is something, it is something in this style this is a law  $U$  which is equal to the resistance multiplied by the current. And that is a current source. If we disregard the resistance, we do not see this resistance and we look at what a current source is we know that as a current source, it has a characteristic:  $I$  according to  $U$  which is something like that. Thus there is a fixed current  $I_0$  which is absolutely independent of  $U$ . Does that actually exist? Probably with complex tri-electronics circuits, one can achieve something of this. But generally, it has already been learned that a transistor can be taken and a current source can be made with, because the output of a transistor has a very high output impedance. This output impedance  $R_{out}$  is the one that I symbolize here and that we will find it every time we make a current source, it's the parasitic impedance which is due to the fact that the transistor still has a sufficiently high resistance that can even be increased and boosted. We will see how or we have already seen that by putting an assembly break elbow we can improve the output impedance.


Notes

Summary



1m 35s

# Charge passive et charge active

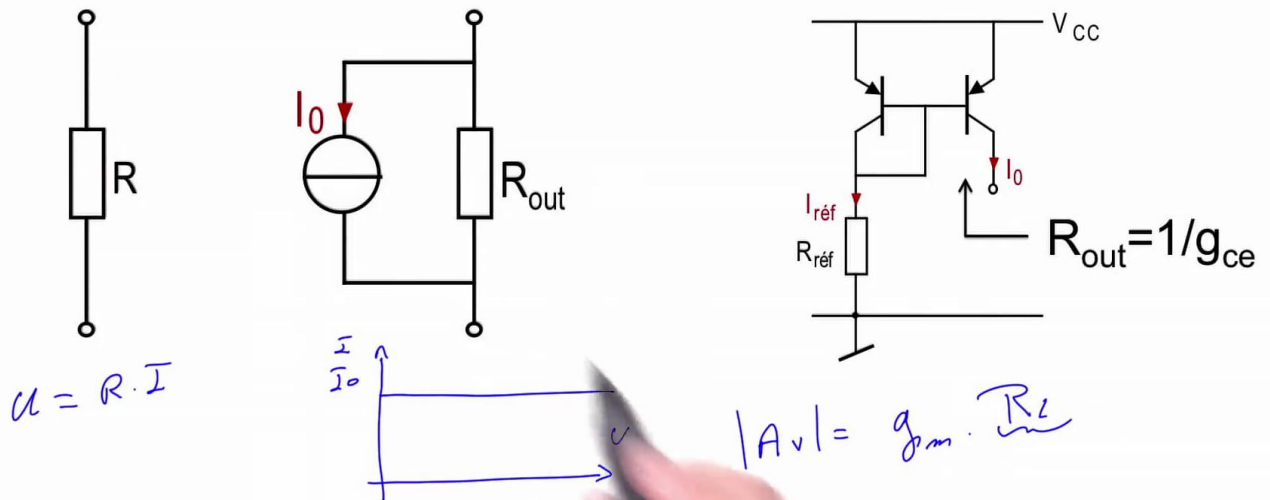

Electronique II

Nevertheless, this output resistance can be extremely high, which leads us to the implementation of a current source. Why do I come back to these bases of so-called passive or active elements? It's because I'm interested in apply the relationship that we had seen before: that whenever we wish to make a transistor assembly and create an AU voltage gain, we found that in absolute value this gain, it is proportional to the transistor transconductance multiplied by a load resistor. And if by chance, we can use this load resistance that we call  $R_L$  as "load" to increase the gain, more this resistance is high, more high is the gain. Therefore the transconductance of a transistor depends on its polarization in contrast the resistance load that will be put to this transistor could be very high, even infinity. So if we do not possess this resistance here and we put a current source like here to a transistor that we will connect just now and you'll quickly see here and we link that to that, Well this transistor there, it will do the conversion  $\Delta U$  voltage into a  $\Delta I$  current and which will go to a very high resistance and this very high resistance will ensure that the gain increases.




Notes

Summary



2m 53s

# Charge passive et charge active

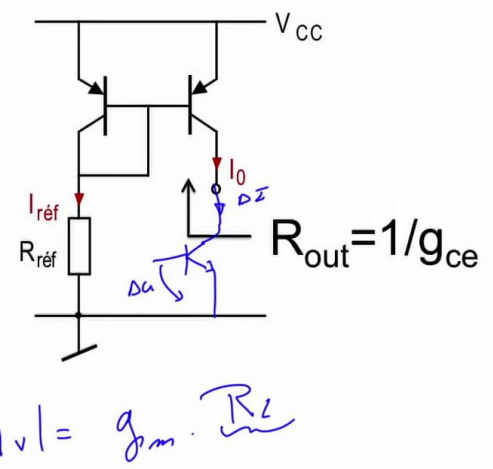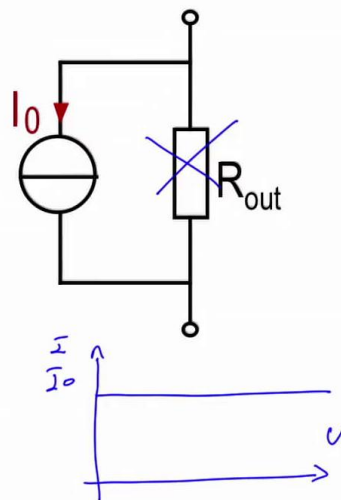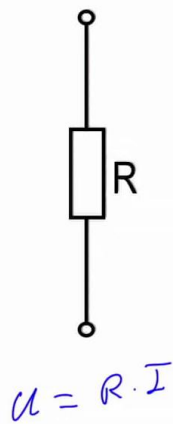

Electronique II

And this kind of assembly we will call it an "common emitter of active load" assembly. And that will make all the difference in relation to... to rather connect a resistor to the collector. And you will see that this kind of installation, it's typically what we will use in integrated circuits later and allowing to get infinite gains as an operational amplifier.


Notes

Summary



4m 23s

# Amplificateurs AC petits signaux

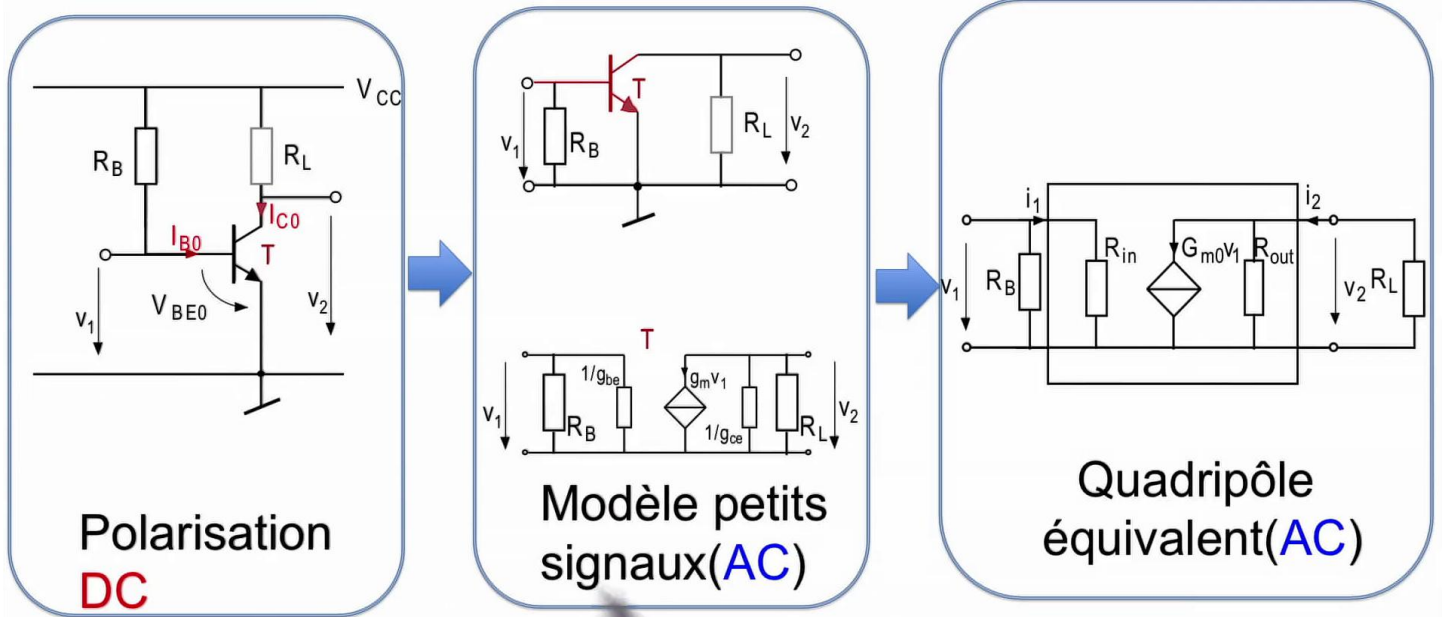

Electronique II

I repeat what I have called an amplifier and I will remember the sequences of achievement and I've added an AC amplifier. So this is an amplifier which can only amplify the signals of variable nature of the small signals increments. Why? Because if you connect your amplifier and you look at the 3 presentations representations of your amp, the actual pattern of the amp, I chose one of the amp possible polarizations and I choose the one by which I polarize the current in the base by a resistance which brings back the current from here and injecte it into the base. And this current multiplied by the transistor beta becomes a current of polarization  $I_{C0}$ . It's a way to do, that is didactic very easy which just requires a resistor to be performed and it polarizes the transistor. Beside, I showed what I call the small signals model that we studied. So if you remember when you plug the transistor in that way and it is polarized, we can ignore this scheme and go to a scheme that we draw on a piece of paper to only see the transistor when we apply to him an increase or variation or small variable signals.


Notes

Summary



4m 48s

# Amplificateurs AC petits signaux

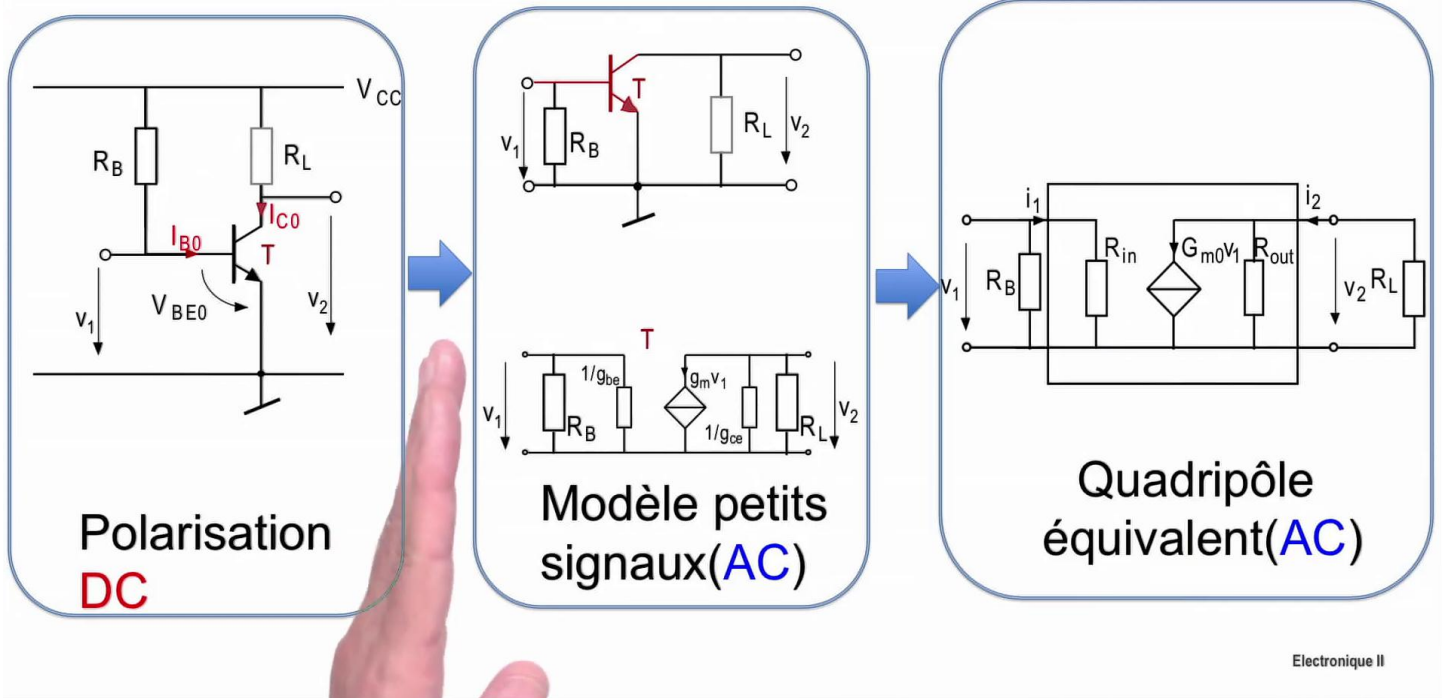

Electronique II

So we will connect it signals that vary in time and as we are only interested in the amplification of these variations, and well continued tensions, we make them disappear because we will be interested in all that is variable so whose derivative  $\Delta V$  on  $\Delta I$  and the  $\Delta V$  on  $\Delta I$  of a voltage source is a ground. So we convert it into a model that gets all fixed voltage sources and brings them back to the ground. And we replace the transistor by those derived therefore the different impedances of sight between base-emitter collector-emitter and the fact that there is a controlled current source and we replace the transistor by this. So we've already seen all this and made an analysis that from that, we can represent thanks to the circuit theory that any block having a voltage at the input which will be converted into a voltage at the output. It can be presented or represented by the input impedance an output impedance, a controlled current source and it's called the equivalent quadripole. So from here to there and the reality from here to there, this is the model and the simplification for us to be able to solve and analyze transistor scheme.

Notes


Summary



6m 09s



# Amplificateurs AC petits signaux

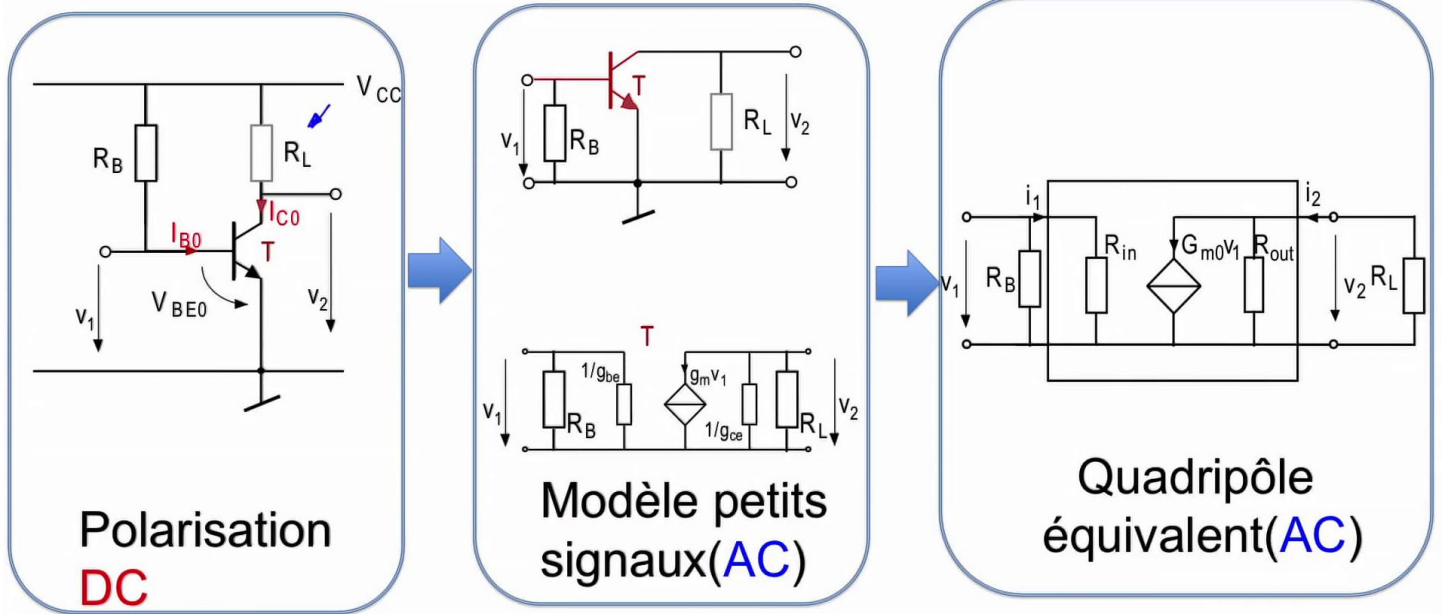

Electronique II

Here is a simple vision of what we'll see, but I want to draw your attention that when you put your finger here or this pen there, we will realize that here I have a voltage difference from here to there of DC nature And I will continue this explanation taking the polarization of transistor, the one we were told that this is the most appropriate polarization when you have a passive load. So the load is this one. So we connected a load in the transistor collector which is  $R_L$ .

Notes

Summary




7m 24s




# Polarisation du transistor

## • Composants discrets

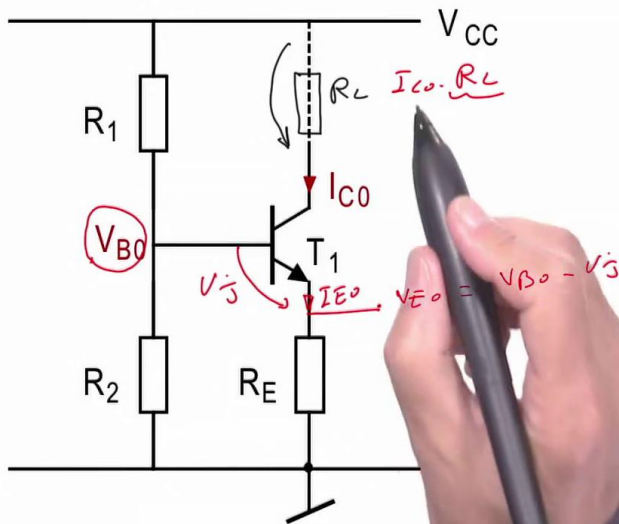

## • Circuits intégrés

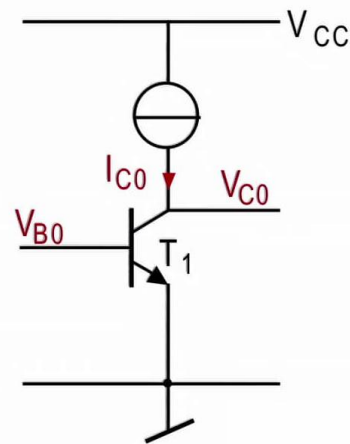

Electronique II

I repeat the polarization of transistor, the one we presented as really being the polarization to use, which imposes a fixed potential on the base. And to generate a constant current  $I_{C0}$ , we impose a transistor and a current  $I_{E0}$  in its transmitter. Well, these two currents are approximately the same seeing the beta of the transistor that exists between the two. So in other words, we impose the current  $I_{C0}$  via  $I_{E0}$  so it's a current that we have imposed, but to get it it was necessary to impose a fixed voltage on the base. I will repeat this phrase: on the base, I have a  $V_{B0}$  voltage, it is a BC voltage. On the transmitter, here I have a voltage  $V_{E0}$  and this tension there, she's  $V_{B0}$  minus the voltage  $U_J$  drop. So I have again a tension which appears here, which is of DC nature. What happens here with the tension at the collector? Do I know it? No. It will depend on the load. There, I have not drawn a load But imagine that someone accidentally adds a load here, a resistance. If you put a resistance there, this resistance, it will have a voltage drop here and that voltage drop, it will be equal to  $I_{C0}$  times  $R_L$ . So  $R_L$ , your passive load exists. The current of polarization you need it, you just create it.

Notes


Summary




8m 03s

# Polarisation du transistor

## • Composants discrets

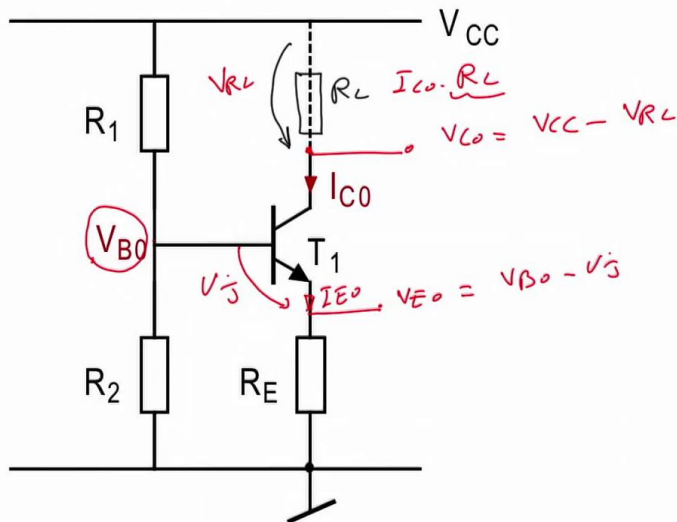

## • Circuits intégrés

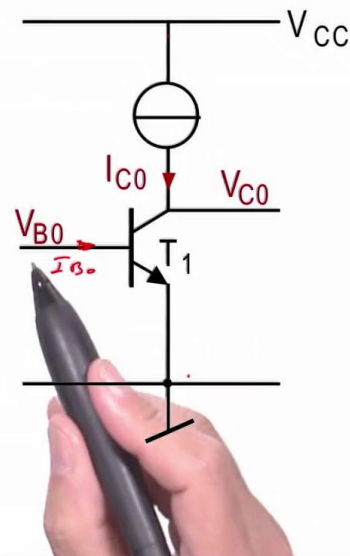

Electronique II

The voltage drop here, it will make you a tension  $V_{CE0}$  which is equal to  $V_{CC}$  minus the voltage we will call here  $V_{RL}$ , minus  $V_{RL}$  and that's it ! This  $V_{CE0}$  voltage, it is defined, it is known, it hadn't been brought to a signal to be amplified, but we already see that we have a DC voltage here. So I have a DC voltage there, I have a DC voltage there and I have a DC voltage there, and you just created it yourself depending on the required polarization when you have a passive load and we can know values such as I just write here. I would like to compare it to this assembly. I take my transistor, and I put it here, instead of putting a resistance in the transmitter which was essential for creating  $I_{E0}$  in this case  $I_{C0}$ , I directly connect to the ground and I come and put it a current source, so this ideal current source that I just plug here will impose a  $I_{C0}$  current that will pass in my transistor. This current there, it will immediately generate a  $I_{B0}$  current that will come from? Well, it's coming from the assembly which is here. this assembly that I have not drawn. What is the value of  $V_{BE0}$ , do I know it? Yes !  $V_{BE0}$ , it is actually proportional to this  $V_{BE}$  voltage which is of the order of magnitude of  $U_j$ .

Notes


Summary




9m 43s

# Polarisation du transistor

## • Composants discrets

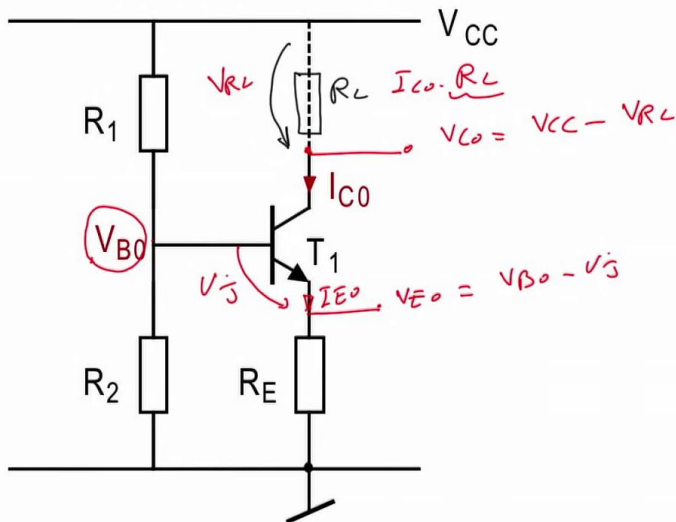

## • Circuits intégrés

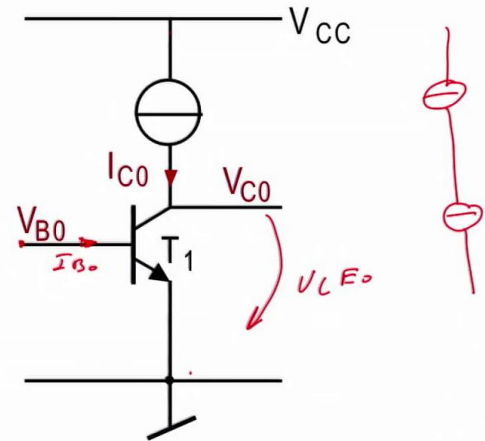

Electronique II

While this tension there, it will be fixed. So this almost constant tension depends on the stage just before we plug. So if you plug something here, this thing that would come before the stage that would come before, should accept the fact that a voltage  $V_{B0}$  is imposed on it. What happens with this  $V_{C0}$  tension? Do I know it? Absolutely not ! See why I can not know it as it is presented here. Do I know  $U_{C0}$  ? To know a voltage,  $I_{C0}$  must be multiplied by a resistance that I see here, between this and that, imposing a voltage  $U_{C0}$  to say  $V_{CC}$  minus  $U_{C0}$  is equal to the voltage drop here. But what happens is that this transistor there behaves as a current source. Suppose it has no output conductance, that the effect "Early" the Early voltage of this transistor is equal to infinity. So it's like I tell you, the output resistance is infinite here. And suppose that you have a current source as drawn here and below, you will also have a power source. And this current source absorbs, everything is perfect inside: the  $I_{C0}$  current flows through your transistor, it is able to absorb the same  $I_{C0}$  current and someone asks you, when you'll assemble this between  $V_{CC}$  and 0, what is the voltage that appears here?


Notes

Summary




# Polarisation du transistor

## • Composants discrets

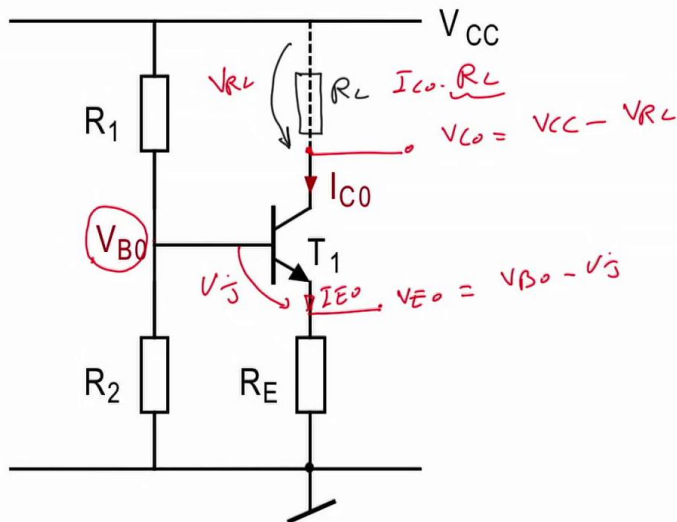

## • Circuits intégrés

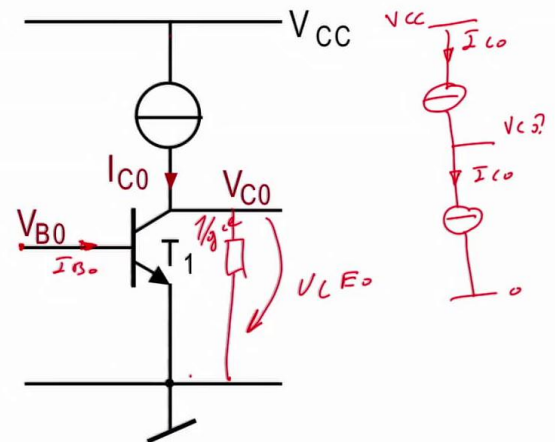

Electronique II

You could not say. Because this tension, it could not be defined it can be anywhere in that range. It may actually go up and down anywhere within this range. Actually this kind of assembly exists, it is used in integrated circuits and usually when you make an output this way we add a circuit to fix what is called the common mode output. So the tension  $V_{C0}$  contrary to what you see there, that we directly see in this assembly there, it could not be known, it will depend on what you will connect yourself on that side. If it's a similar assembly as we said here, if you come here to connect a transistor like this, this tension from here to there if it is a PNP transistor, it will be of a voltage junction nature. But for the moment, nobody could tell you what is the  $V_{C0}$  tension. One can of course ignore or make a guess that there here I have a resistance which is the output transistor of that resistance which is  $1 / G_{CE}$  and this resistance there allows me to find the test potential that is at output. But what I want to said there comparing these two approaches, that's an assembly which takes into account the discrete components in which I had to use: a resistance to impose  $I_{C0}$  current, two resistors to impose the potential  $V_{B0}$  and there, I had to use a component which is a current source, we will see just now how we will do it to impose the  $I_{C0}$  current.


Notes

Summary




# Polarisation du transistor

## • Composants discrets

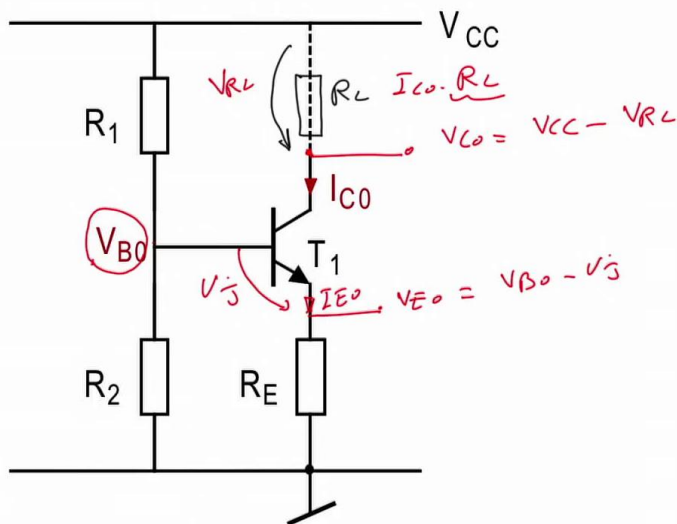

## • Circuits intégrés

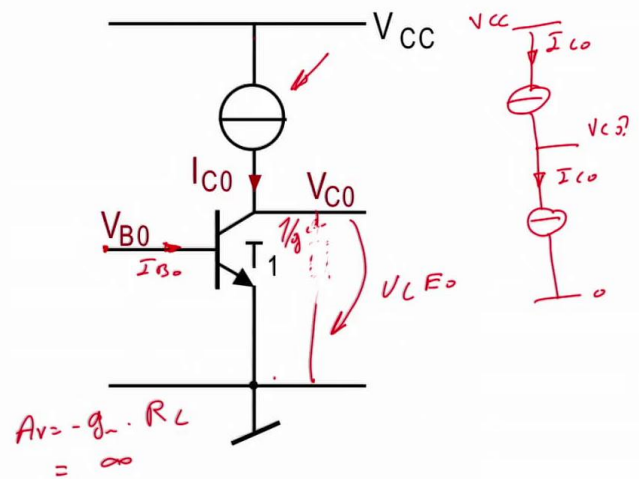

Electronique II

In this case, when I write the gain, it is really the gain of a common transmitter assembly, So this is the gain which will be equal minus GM times a load resistor. I consider that this resistance there, it is infinite so it does not exist, I erase this. There, there is no resistance here and there it is an infinite resistance, we have just seen it. So what is the gain of this circuit? Well the gain of this assembly, it can only be infinite, because  $R_L$  is infinite. We have just seen that a power source it's great, I just realized an assembly whose the gain is infinite. I remind you that in an operational amplifier when you take an ampliOP, it displays theoretically an infinite gain if not very very large. So it's probably inside, we used an assembly in the integrated circuit which mold the operational amplifier, we used an assembly of that nature here. And it is absolutely the case because we use active charges because thanks to that, we have the very high resistance if not infinite, and we can cascade 2 stages which lead us to extremely high gains.

Notes


Summary



14m 20s

# Couplage et découplage AC

## • Couplage

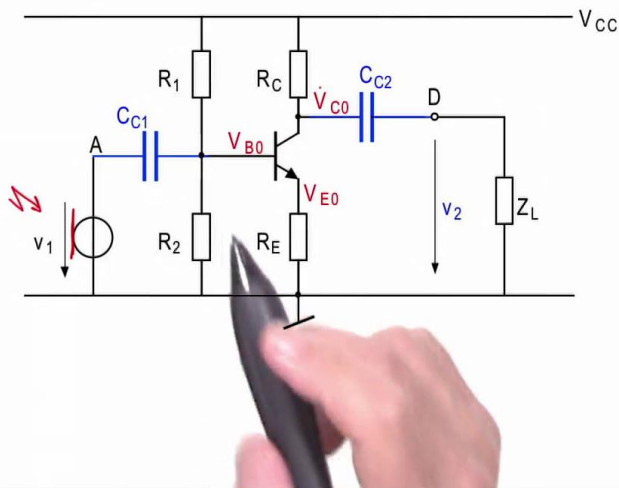

Electronique II

I go back to the analysis of this circuit we just saw before. That is to say the assembly, I hide these 2 parts, I show it like this, It is the famous montage where it was necessary to polarize I points back potentials  $V_{B0}$  -  $V_{E0}$  -  $V_{C0}$  that we called resting points or operating points. An operating point, is that, at rest, when you plug it and you take a voltmeter according to ground and measure that point, it displays the  $V_{B0}$  voltage, we measure this, it displays  $V_{E0}$  and here we see  $V_{C0}$ . But when you take an alternative signal so this which is in red represents the DC components. Suppose that here you have a sensor which varies over time, we can take an example of an audio signal coming from a microphone. So suppose that is a microphone and then you bring a signal and you want to amplify, you want to amplify the signal that arrives here this signal is of AC nature in this node A which is an AC signal therefore which varies in time. That is a source of tension. How could we connect this tension there on a DC point? If the capacity that you see here does not exist, so if you're in that situation, so I'll delete this capacity and I will replace it with a short-circuit If I do not have that capacity and look what will happen to you.


Notes

Summary



# Couplage et découplage AC

## • Couplage

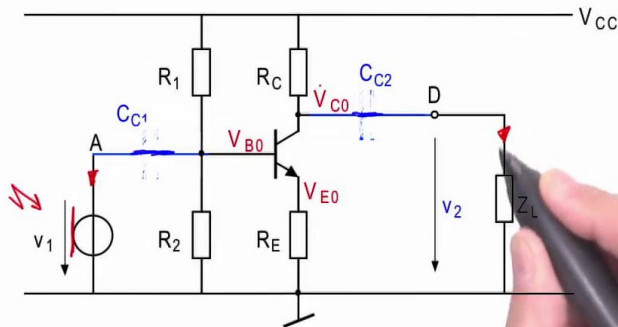

Electronique II

You take this, you plug this line directly like that, you find that the  $V_{B0}$  appears across your source. If it were a microphone, your microphone it will never work because it will have a DC potential which is imposed so it will have a current that will go through it that goes in that direction there, it comes a current that goes into your microphone that comes from that connection here. So that, that's wrong! Same, if you come this way and you connect, we will say a loudspeaker to facilitate the task and you put a signal transducer which will convert the audio signal and that the capacity which is there doesn't exist and well you find yourself with this capacity which is again replaced by a short circuit. So as if your speaker, it is connected to a DC potential. So I take my signal here and I connect it to that, So this: the  $V_{C0}$ , it will tackle a DC voltage on your speaker. So a scheme of this style, there to which you connected a resistance which comes to putting on a DC potential will be covered by a DC current of course. So in a speaker, it'll make a hell of a noise when you plug it because it will pull the membrane and it will make passing a constant current and there on that side, your microphone it will also be browsed by a constant current and this assembly it could not be used.

Notes


Summary





# Couplage et découplage AC

## • Couplage

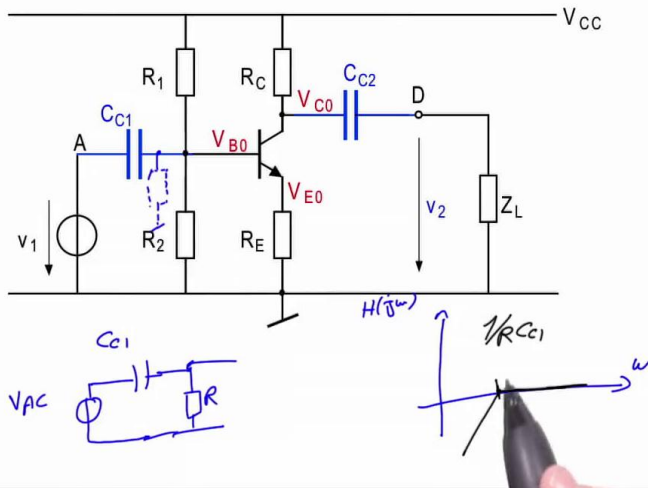

Electronique II

So what we can do, I return to the previous diagram, I put my capacities back and I observe what happens. If I look at this capacity and I imagine that there, I have an impedance, we will consider that it is purely resistive. I will draw what I see there, I hide all this part there and I say all this, it is equivalent to a resistance, this is something that appears as a resistance. And if I look at this circuit which is there, so this whole part there comes down to that resistance there. And I draw below what I see. I see a capacity  $C_{C1}$  and an impedance which appears here. I apply here a variable AC source and I go into this kind of circuit. Well it's this kind of circuit, this is typically a circuit of high-pass nature. I see that the C and R, I represent them in a Bode diagram So  $H$  of  $J$  omega module according to omega, it would give me something of this style with a point here that is equal To  $1 / R \times C_{C1}$ . Therefore knowing the resistance  $R$ , I can calculate the capacity  $C_{C1}$  and deciding that from a point, I strongly attenuates the low frequencies and I have a bandwidth in which I transit my AC signal.


Notes

Summary



# Couplage et découplage AC

## • Couplage

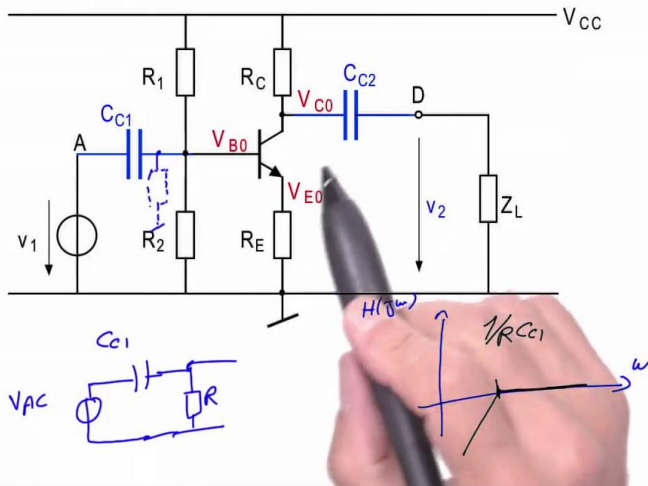

Electronique II

So when I take an AC signal, I correctly calculate my capacity, which couples the increases through this assembly, the DC voltage can not pass in this direction there, there is no DC current which crosses my capacity it is well known. So my capacity, it will act on the alternative current that will cross it in this direction and it will come in my assembly and it will overlap with the component  $V_{B0}$  which is here. So I find myself with a high-pass circuit where low frequencies have been eliminated so the DC components as well. And I can do the same on that side. From that side, I put a coupling capacity, This capacity it will take the alternative signal here which is superimposed on  $V_{C0}$ . When I vary the tension there, I will vary the tension there. And the capacity, it will behave as a closed circuit for variations and it will decouple the DC voltage, so the DC voltage does not appear on that side except of course the index response when I have a voltage jump and I put in tension all of this. So the capacity is loading to this potential  $V_{C0}$ , on the other hand, the signal AC passes through and again, here if you analyze what you observe here, it is again a circuit of CZL nature and there you have a high-pass filter if this is a resistor.

Notes


Summary

20m 30s



# Couplage et découplage AC

## • Couplage

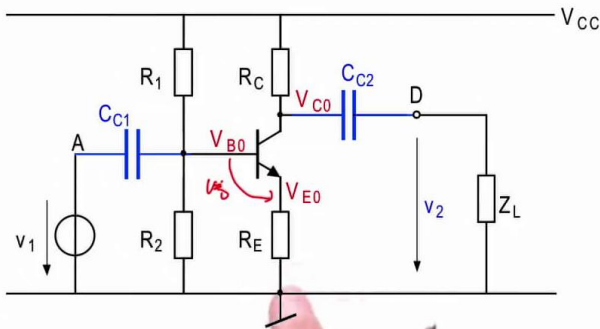

Electronique II

So we realise a filter on that side, a filter on that side and these 2 filters are of this nature to pass the high frequency components. I return to the assembly. So I think we located the capacity used to prevent the AC signal to be shorted or rather the DC signal to come on our source and load and we decoupled the variation by capacities, it was called capacity-decoupling or capacities-decoupling. When we studied the common transmitter assembly, the transistor transmitter was connected to ground and there, we had to add it the resistance  $R_E$ , so the transmitter is not connected to ground. If you have a variation here and you have a variation, you have an almost constant drop voltage which is  $V_{BE}$  there, so you will end up with your variation which moves and turns on  $V_E$ . The variations there and the variations there are the same if tensions between the two, the voltage is constant. So you will end up with that tension there copied here. So on this resistance there you have a varying voltage. Same on  $V_{CE}$ , you'll have a tension that varies. When the transmitter has been grounded, there wasn't this resistance  $R_E$  and it was considered that the gain of this assembly, The gain of this assembly was calculated and we had seen that this gain equaled less  $G_M$  times the load resistance.

Notes


Summary




22m 02s

# Couplage et découplage AC

## • Couplage

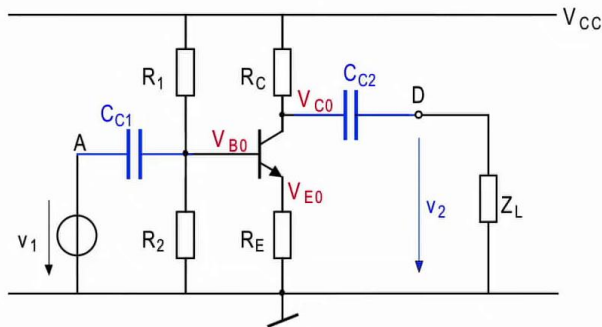

## • Découplage

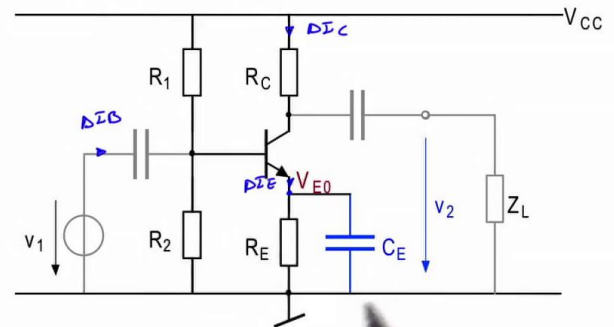

Electronique II

Is this is the case? when I add a resistor in the transmitter This is valid when the transmitter was to the grounded. Now I'll add him a resistance and well that is not the case. You will do this in an exercise and you will see that the gain of this assembly When we put a resistance, this gain is not this, the gain will be of the order of less  $R_C$  divided by  $R_E$ . So we do not have the high gain we will have a gain which is relatively low compared to this. so how do we do? How to bring the transmitter to the ground? Well what we're going to do, We will do the following: we will add in the same way a capacity which would short-circuited the resistance  $R_E$  for the alternating current to pass By capacity not by resistance and again from the AC point of view this resistance is short-circuited. And here it is! this is the assembly when using a decoupling of the transmitter. so if you have an AC current that happens here, I will get a current here, a  $I_B$  delta which will generate a  $I_C$  current delta. This current is approximately the same  $I_E$  delta, this current arrives in this node there, it has a capacity in parallel and it has a resistor in parallel. The impedance of the  $Z_C$  capacity is proportional to  $1/2 \times \pi \times F \times C$ .


Notes

Summary




# Couplage et découplage AC

## • Couplage

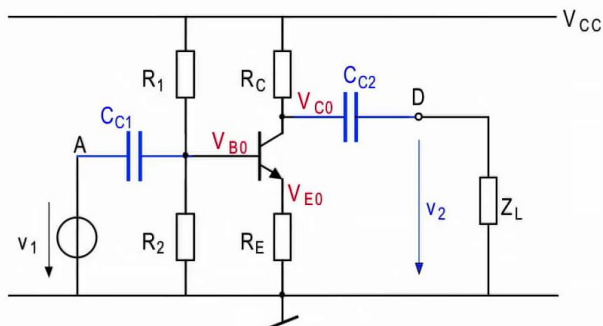

## • Découplage

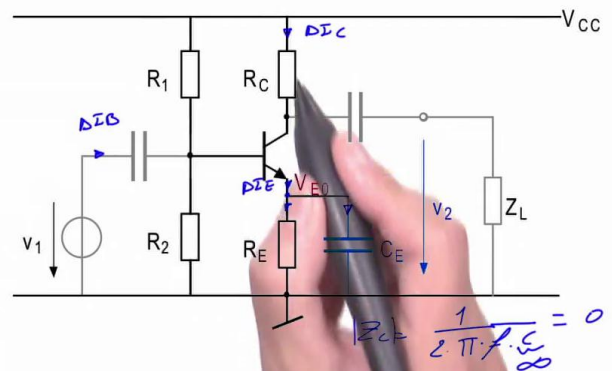

Electronique II

So if you consider that it is infinite or a very very high capacity this ZC it will be equal to 0. and the impedance of the capacity ends to 0 or when the frequency is high, the ability is high. So what IE delta, he sees himself in a node where it can go here and there and of course it will go through the lowest impedance in this case the impedance of the capacity, so the capacity which is there will short-circuit your RE resistance. And from the AC point of view, from the point of view Alternating current, it will rather by your ability. which brings you back to say That the transmitter goes to ground by a short circuit performed by a decoupling capacitor. And here are two names: coupling and decoupling that will allow us to create assembly in which one will superimpose of the DC components and AC components and in which we removed the effect of the RE resistor which is essential to the DC. And when there is a variation, It is shorted-circuited despite the current continues, continues to cross it because the direct current, the one we had seen, that we would see red here. If I put a DC here IC0 which is pretty much the same here it will go through the step resistance capacity because it is continuous in nature and capacity is an open circuit because F equal to 0 for a direct current.

Notes


Summary




25m 20s

# Couplage et découplage AC

## • Couplage

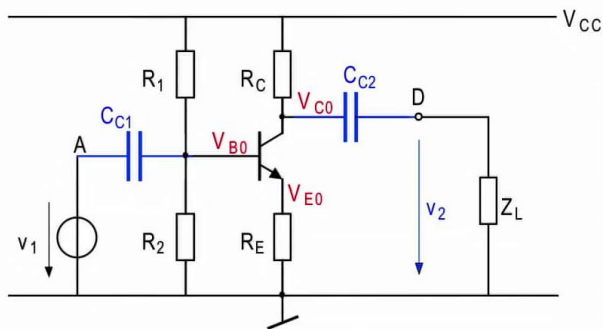

## • Découplage

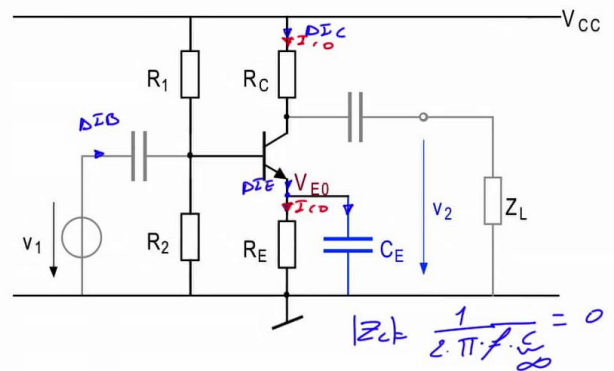

Electronique II

So the DC goes through there, Alternative here and there it is, we arrive on a diagram complete assembly which amplifies The AC signals while superimposing them to DC components and improving the assembly by placing a decoupling capacitor to eliminate the effect of polarization.


Notes

Summary



# Couplage direct en circuits intégrés

- Assurer que la source ou l'étage précédent fournissent le courant de base du transistor

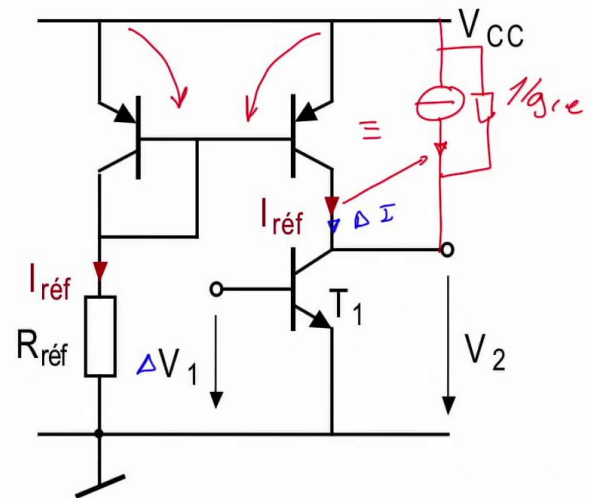

Electronique II

I come now on the same assembly but I'm replacing all that I have just seen before by a current source. so I remind you that this assembly which has a current mirror, this is identical to a current source here having a parallel impedance which is equal to  $1/g_{ce}$  of this transistor. So it's a pretty high impedance in parallel with a current source whose value of the flow of this current is this, that's the  $I_{ref}$ . So we fall back on what has been discussed and has been called the active load. This part I refer you to the course on the mirrors of the currents, it simply serves to impose  $I_{ref}$  and which would generate a voltage  $V_{EB}$  here who is copied the same here. So it will spark this current and impose it on the other side. And this transistor there, it will have a delta  $V$  variation, so I could put in blue to talk about a variation. And this change will generate a current in delta  $I$ . Here the delta  $I$ , it will see as an open circuit for the current source, it will stay to it  $1/g_{ce}$  that is to say it will remain to it a great resistance, so it will realize a gain  $AV$  equals minus  $GM1$ .

Notes

Summary



27m 18s




# Couplage direct en circuits intégrés

- Assurer que la source ou l'étage précédent fournissent le courant de base du transistor

$$A_V = \frac{-g_{m1}}{g_{ce1} + g_{ce2}}$$

$$\downarrow$$

$$\frac{I_{ref}}{V_{A1}} + \frac{I_{ref}}{V_{A2}}$$

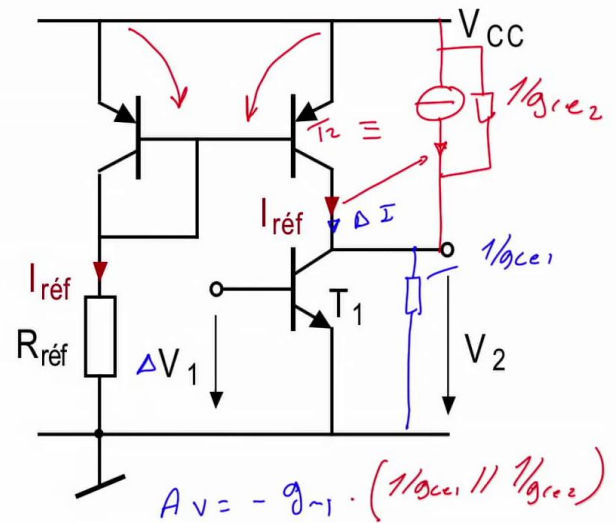

Electronique II

If we consider that this transistor has no output impedance or even if you consider it, you would have drawn here an impedance of a value  $1 / G_{CE1}$ ,  $1 / G_{CE1}$  and here we would have written  $1 / G_{CE2}$  and there I call it transistor T2 therefore the gain of such an assembly would become minus  $G_{M1}$  multiplied by the parallel setting. You remember that I must short-circuit  $V_{CC}$  to ground, so I would put  $1 / G_{CE1}$  parallel to  $1 / G_{CE2}$ . and this would give me an  $A_V$  gain equal minus  $G_{M1}$  divided by  $G_{CE1}$  plus  $G_{CE2}$ . And this kind of installation, we will also make a simplified abstraction, suppose that  $G_{CE1}$  is  $I_{ref}$  divided by the Early voltage of transistor 1 and the other is  $I_{ref}$ , it is the same current in both divided by  $V_{A2}$  which is the Early voltage of the transistor 2. And the  $G_{M1}$ , this transistor it has a current  $I_{ref}$  which passes through it divided by  $U_T$  and look what will happen with this kind of montage: if you consider that  $V_{A1}$  and  $V_{A2}$  is the same value, that the two transistors have the same tensions of Early and that the same currents cross it therefore the  $I_{ref}$ ,  $I_{ref}$ ,  $I_{ref}$  will disappear.

Notes

Summary



# Couplage direct en circuits intégrés


- Assurer que la source ou l'étage précédent fournissent le courant de base du transistor

$$A_V = - \frac{g_{m1}}{g_{ce1} + g_{ce2}}$$

$$\downarrow$$

$$\frac{I_{réf}}{V_{A1}} + \frac{I_{réf}}{V_{A2}}$$

$$A_V = - \frac{2 \cdot V_A}{U_T} = 26 \cdot 10^{-3} V$$

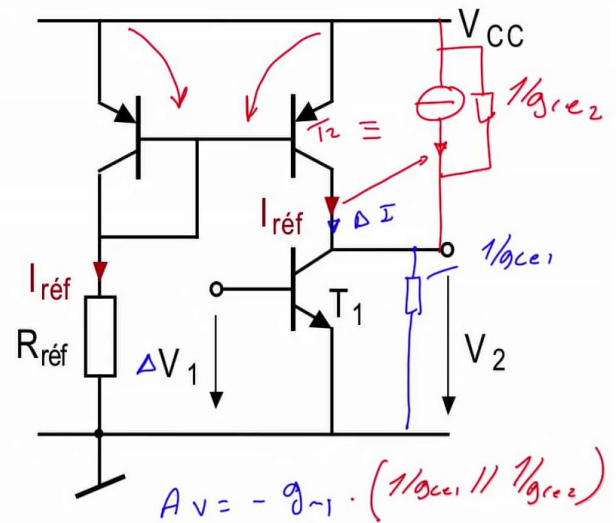

Electronique II

Look at what's going on: you end up with a gain which is proportional to, if we replace  $V_{A1}$  equal to  $V_{A2}$ , therefore you are with 2 times, so that the  $A_V$  gain would become less than 2  $V_A$  divided by the thermodynamic voltage  $U_T$ . And you can do what you want with this assembly, you do not change the gain. It depends on the Early voltage and you remember in the bipolar transistor, it is linked to the width of the base and it's not you who are going to do it, it is part of the characteristic of your transistors and the thermodynamic voltage this is the 26 millivolt. So here it is a constant value at room temperature and there it is a value related to your transistor, so you can not change it, it would give you a fairly high gain independent of your design. but then you will tell me: "It's great!" Yes, it's great. It makes a gain. As soon as you plug it in, technology that you would use impose the Early voltage to you. It is linked to the physical law, you can not change it and you get a gain. And this gain is quite high because you have at the denominator 10 minus 3, therefore there is a factor 1000 that will multiply the ratio of  $V_A / U_T$  multiplied by 2 and the Early voltage is of the order of hundred volts for a low power transistor and there it is you find your self with a gain that automatically is high.

Notes

Summary



