

Redresseur non-inverseur simple alternance



Electronique I

Once we've finished with linear applications, we're going to move on to non-linear applications. A non-linear application means that the relationship between input and output is not linear. It's not $y = x$. Typically, under non-linear applications we often study rectifiers. So, we take a circuit which manages to replace the famous diode. So this component which lets the current pass in only one direction, we can do it with components such as diodes, but to which we've added an operational amplifier arrangement. So, fulfilling the dream of an engineer is the super diode. Because a diode is unfortunately a passive component. The output voltage, when we leave it, when we use a diode, there's a junction voltage that we lose between the applied voltage and the output voltage, and this junction voltage is around 0.6 to 0.7V, or even less in some types of diode. We'd like to rectify a voltage with an amplitude of 100 mV. We can't use a diode, because the diode needs a certain level of voltage, and above that, it starts to act like a circuit which lets the current pass in only one direction. So, we're going to do it with operational amplifiers and by using diodes.



Notes

Summary



0m 04s

Redresseur non-inverseur simple alternance

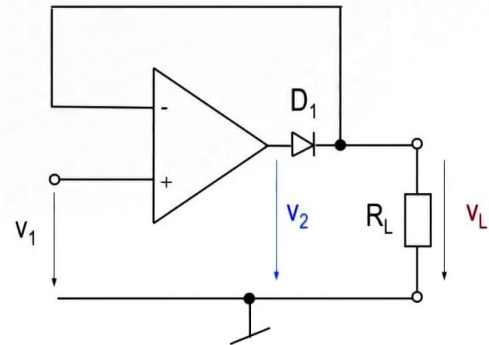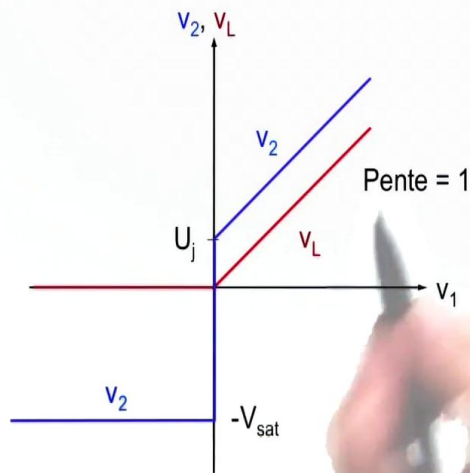

Electronique I

To begin, I'd like to speak about the non- inverting half-wave rectifier. I'm going to analyse this line here, which shows what this arrangement can give us. The V_L output voltage, the V_1 input voltage, and we've added a diode. Of course, we have our operational amplifier which is here. This is what we expect of this circuit. I'm going to present and comment on it here, and analyse why we get something like this from this circuit. If you look at what happens to the V_1 voltage here, as opposed to the V_2 voltage then... Sorry, I rather want to talk about the V_L voltage. If you look at what happens with the V_L voltage, compared to the V_1 voltage, then we can see that V_L in accordance with V_1 , corresponds to this straight line here, where the output voltage, in relation to the input, has a slope = 1, so $V_1 = V_L$. This voltage is equal to that, when V_1 is positive. The red line corresponds to the output V_L . And we see that this red line will only follow the V_1 voltage when V_1 is positive. If V_1 becomes negative, there it is, V_L becomes equal to 0. So, $V_L = 0$ if V_1 is negative. $V_L = V_1$ if the V_1 voltage is positive. Therefore it's non-linear. It's a non-linear curve. It's not a straight line.

Notes



Summary



1m 26s

Redresseur non-inverseur simple alternance

• $v_1 < 0, v_2 = -V_{sat}, v_L = 0$

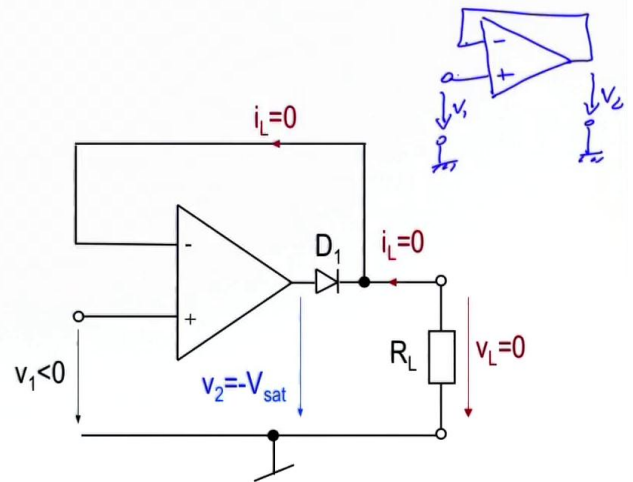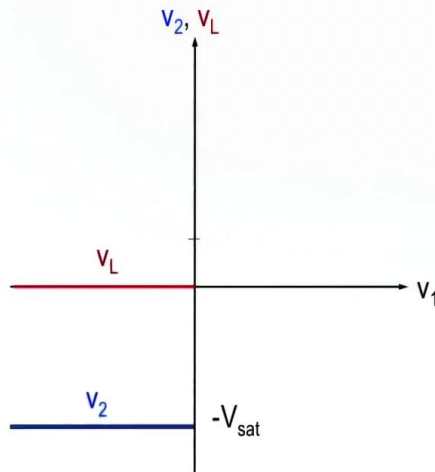

Electronique I

That's absolutely not the case. It's simply: look at the sign of the voltage and rectify it. So, if the voltage is positive, we find the component positive. And if the voltage is negative, the output voltage is cancelled out. We're going to analyse this circuit in the following way. I would like to analyse this circuit step by step, and explain how we analyse this type of circuit. So, you've seen that there is a diode. If we disregard this diode, I'm going to draw the circuit which is that without the diode. So, we have an operational amp, we have a voltage follower, and we have an input here, and here, we've connected a V_1 voltage. And we're looking at the V_L output voltage. So, theoretically, this type of circuit gives $V_1 = V_L$, this voltage equals this voltage, this voltage is the same as the output, there's no current passing here, it's the amp which provides the output current. And we have a voltage follower. We add a diode. This diode will be inserted between the amp output and the charge that we connected there. I started first by analysing what happens if the V_1 voltage is negative, what happens with the V_L voltage at the output. I said if V_1 is negative.



Notes

Summary



Redresseur non-inverseur simple alternance

- $v_1 < 0, v_2 = -V_{sat}, v_L = 0$

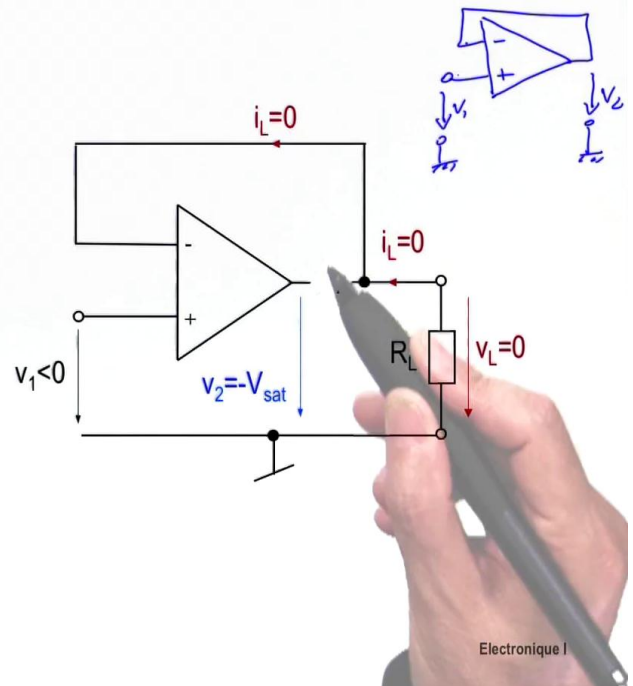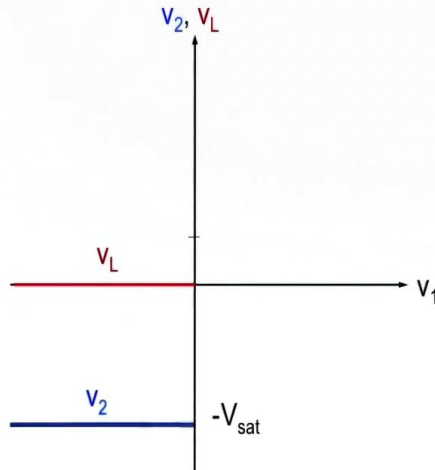

Electronique I

Logically, in this circuit, if V_1 is negative, V_L is negative. When we say: a V_L voltage is negative, if that voltage had been negative, the current passes in this direction, I deliberately connected an R_L resistor to simplify it and make it easier to understand. So, if you look at what happens with this resistor when it has a negative voltage, we expect there to be a current that passes from the earth and which should come out like that, arrive in this node here. It can't go over here, because the amp doesn't absorb current at the negative terminal. Generally, it passes the amp. It continues its path towards $-V_{CC}$. But it can't do it, because we added a diode, and this diode blocks in this direction. So, this current can't at all get past this diode to go towards the amp. So, what will happen is that this current arrives, it can't go in this direction, $i = 0$ here, $i = 0$ here. And we'll get a voltage $V_L = 0$. If we want to look at this arrangement another way, you just have to imagine it with a blocking diode. The current wants to cross it, so, logic says: it's as if we don't have this diode, as if this diode had disappeared. We have nothing at all here. Look what happens with this circuit.

Notes



Summary



4m 39s

Redresseur non-inverseur simple alternance

• $v_1 < 0, v_2 = -V_{\text{sat}}, v_L = 0$

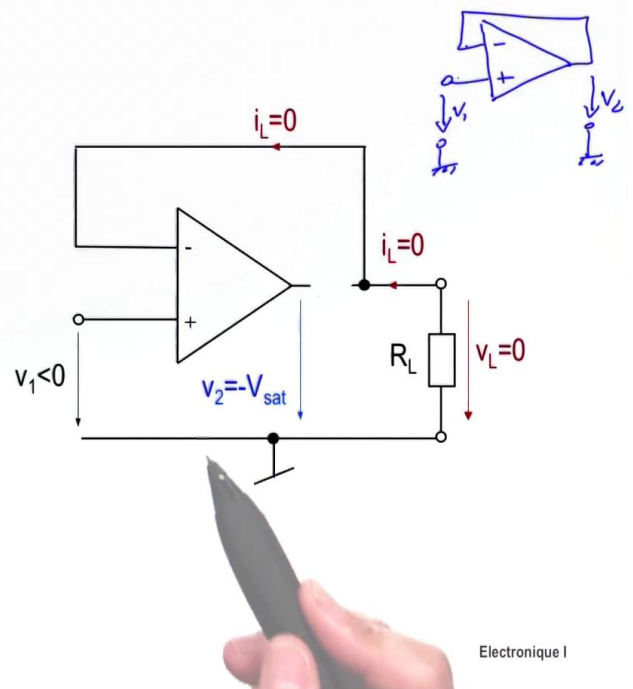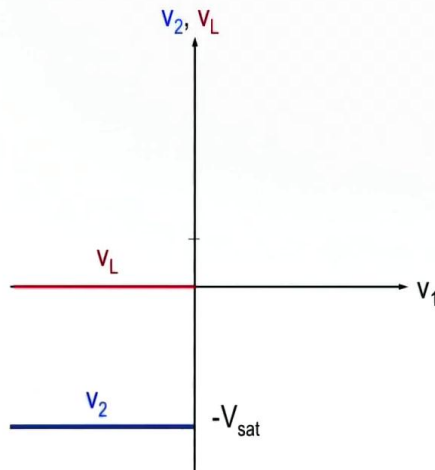

Electronique I

You find yourself with a circuit which is exactly this. The diode disappeared, because it has no role to play. The current here can't pass through there. The voltage, here, it finds itself on the positive terminal. But what can be found here as potential? We definitely have an $i_L = 0$. In a charge where there's no current, the voltage $V_L = 0$. So, your terminal or the negative input of your amp is connected to earth, through a resistor that plays no role, because there's a potential difference equal to zero, there's no current passing through anywhere, So you find yourself with a V_2 voltage from your amplifier, disconnected from V_L , and V_L will show you a voltage equal to zero. And this is only applicable when V_1 is negative. So analysing that on the curve, it's what I've described there. If V_1 is negative, so we're below zero, $V_L = 0$, we can see that here. V_2 , unfortunately, at that moment sees this potential connected to zero, sees this potential with a negative value, we can imagine at -1. If you have -1 here and 0 there, it's going to tell you that your amp will act as a comparator. It compares the -1 to 0, and it'll find itself with the $0 > -1$, so it'll saturate towards $V_{\text{sat}} -$.

Notes



Summary



6m 02s

Redresseur non-inverseur simple alternance

- $v_1 > 0, v_2 = v_L + U_j, v_L = v_1$

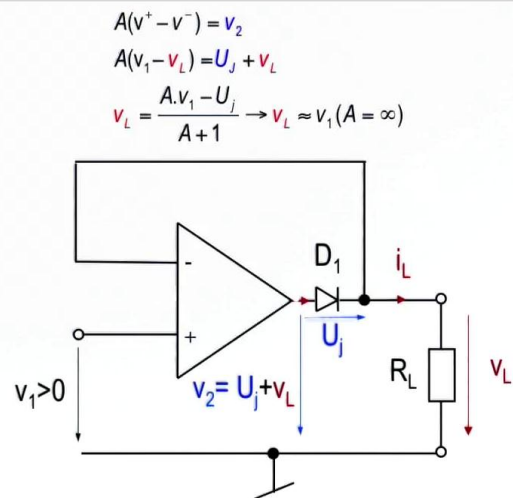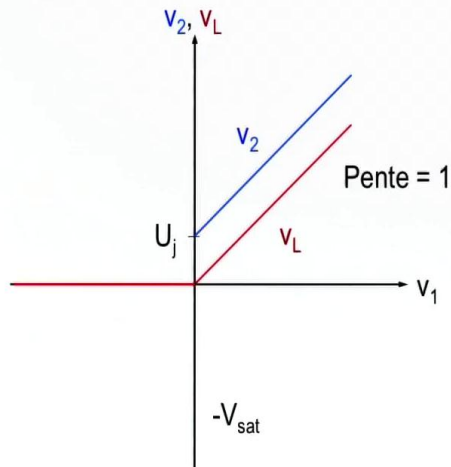

Electronique I

The output of your amp will then have $V_2 = -V_{sat}$. And that corresponds to what we've just seen here. V_1 negative, V_2 , which we can't see, because we subdue it at the output. But at the output, our $V_L = 0$. I'm going to take the same setup and this time analyse the case when V_1 is positive. This time, V_1 is positive. If you remember, the feedback, when V_1 is positive and has a voltage follower, we expect V_L to follow V_1 , so V_L will have the value of V_1 , it'll be positive. A positive voltage means that the current i_L is passing in this direction in the R_L resistor. That means that there's a current which will come out of my amp through this diode, but this time the diode is in the right direction. And in this direction which lets the current flow, if the current passes through, there will definitely be a threshold voltage equal to U_j . The output of my amp which is there, V_2 , will see a U_j voltage plus the V_L voltage. And we can see it here. So, when this current passes through this diode, the feedback is established. And I'm going to show now that the fact we added a diode won't hugely change what happens with this type of arrangement. We have V_1 equal to this node here.


Notes

Summary



Redresseur non-inverseur simple alternance


- $v_1 > 0, v_2 = v_L + U_j, v_L = v_1$

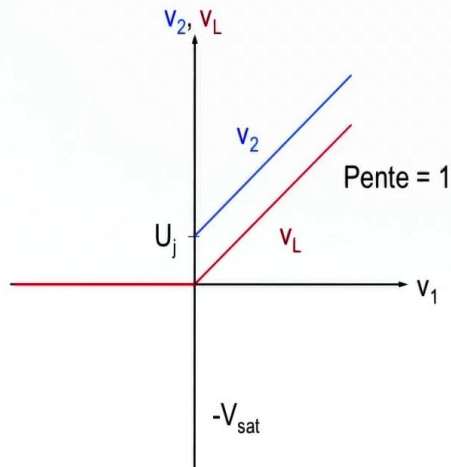

$$A(v^+ - v^-) = v_2$$

$$A(v_1 - v_L) = U_j + v_L$$

$$v_L = \frac{A \cdot v_1 - U_j}{A + 1} \rightarrow v_L \approx v_1 (A = \infty)$$

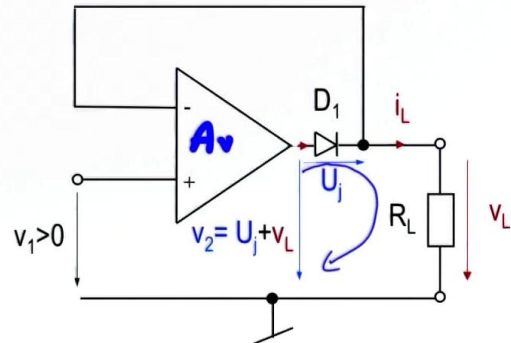

Electronique I

Remember that when an amplifier has feedback, this V_1 here is copied there, and if you follow this line, it will go towards V_L , so V_1 is equal to V_L . And that's exactly what we want from this circuit. We want it to become a follower when V_1 is positive. So the positive component is returned at the output. I just wanted to give a little demonstration. By taking our operational amplifier, saying, as we've always seen, that the potential on the negative terminal, and the potential on the positive terminal, that's $V^+ - V^-$, is multiplied by the amplifier's gain, and this gain is infinite. If that gain is infinite, and we have the equation that V_2 which is here, equals this infinite gain, which multiplies $V^+ - V^-$, and that this V_2 voltage, I'll write it, this voltage is equal to U_j , if I take the Kirchhoff circuit laws from here to here, I'll say that $V_2 = U_j + V_L$, which is written here. So, this $V_2 = U_j + V_L$, and if I replace V^+ and V^- by their values, $V^+ = V_1$, which I put here. $V^- = V_L$, connected through here, and I write this equation. And I'd like to look at V_L in accordance with the rest. This is saying that $V_L = (A \cdot V_1 - U_j) / (A + 1)$.



Notes

Summary



9m 10s

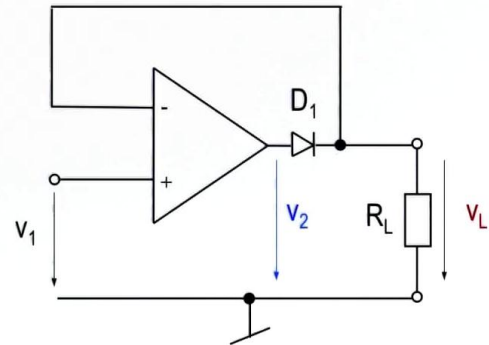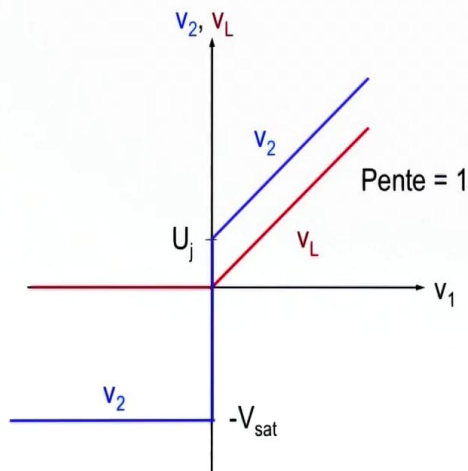Redresseur non-inverseur simple alternance



⊗ Limité en fréquence (slew rate, réponse en fréquence de l'AO)

Electronique I

Remember that A is infinite. Remember that if A is infinite, and we look at $\infty + 1$, I can easily say that I can discard this 1, in relation to this A . I also have $A \cdot V_1$, minus a certain relatively small amount, which is from around 0.6 to 0.7 V, this is the junction voltage at the diode's terminals. So I can also discard this component here. At that moment, I only have to look at the equation which is left, which is, of course... an estimation. It's $A \cdot V_1 / A$, so I can eliminate A and A and I get $V_L = V_1$, which is exactly what I expected. Definitely this U_j enters into our equation, but compared to $A \cdot V_1$ with a gain which is extreme, this doesn't affect it at all, or really affects this type of circuit very very lightly. So, with that we've got what we wanted. With that we've got that when the V_1 component is positive, the V_1 output will follow, or rather the V_L output follows the V_1 voltage, we see it there. When this is positive, we have a voltage follower with V_2 which is still affected by U_j compared to V_L , so that corresponds to this straight line here. To summarise, our circuit is this, with the results we got. If the voltage is positive at the input, the output will follow it.



Notes

Summary



10m 43s

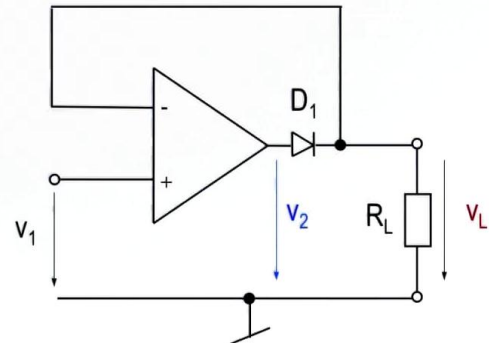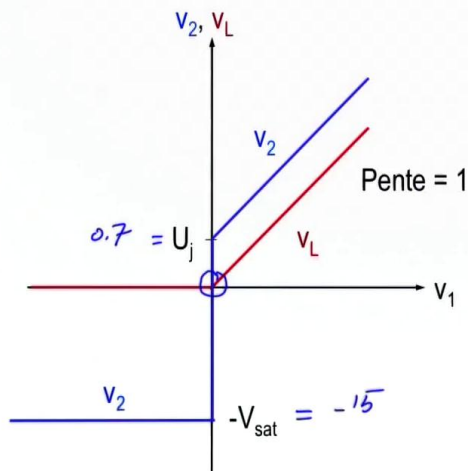Redresseur non-inverseur simple alternance



⊗ Limité en fréquence (slew rate, réponse en fréquence de l'AO)

Electronique I

Every time the voltage we wanted to rectify goes from a negative value to a positive one, the amplifier doesn't manage to follow if the amplitude of the V_2 voltage is high. So, remember that the *slew rate* affects the frequency response of the operational amplifier, but the *slew rate*, if you lower the value of V_1 so in this case V_2 , so in this case V_L , you perhaps manage to better follow, but this difference is quite excessive, and this has a big impact on the frequencies that we can get when we use a circuit like this. So we have really a big frequency limitation on this type of circuit.

Notes

Summary



13m 57s