
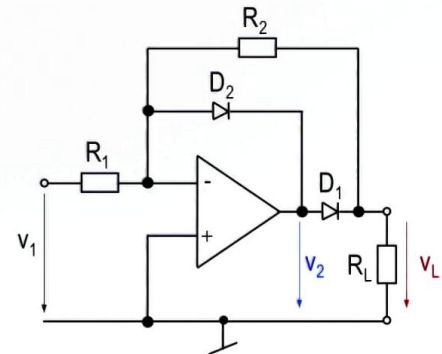


Redresseur inverseur simple-alternance

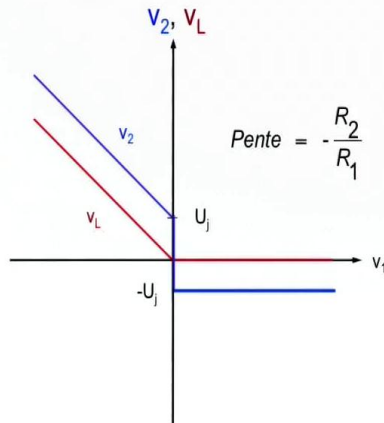

Notes



Now I would like to start with rectifying a signal, but do the opposite to what we did earlier. Earlier, we made a non-inverting rectifier, now, we are going to make an inverting rectifier. We would like to make a function if the input voltage v_1 is positive, I would like the output voltage v_L , to be equal to zero. However, if my v_1 voltage is negative, I would like the output to be opposite, so it's positive. So I'll take the negative component of v_1 and rectify it, I'll make it positive. And if v_1 is positive, I'll put the v_L voltage equal to zero. And we are going to analyse the montage based on an inverting montage. I am going to outline it without diodes. Compared to the montage that we've just analysed, I'm dealing with two diodes. Earlier, I used a single diode. You will see why I need two diodes. But I'm going to outline it without diodes. I'm going to outline an inverting montage without diodes. So I will try to modify this like that in real time, if I eliminate this diode D_2 , which is no longer there, and in place of this D_1 diode, that I will also remove, I'll replace that with a short-circuit which will join this node here to that node there.

Summary



Redresseur inverseur simple-alternance

$$V_L = - \frac{R_2}{R_1} \cdot V_1$$

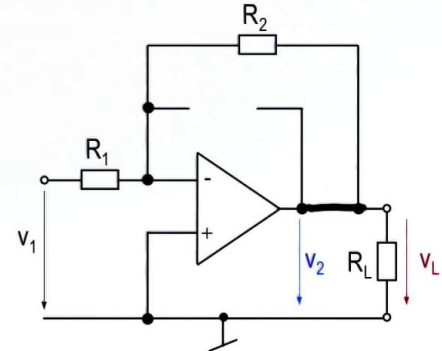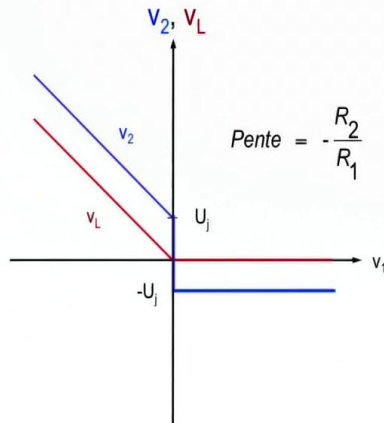

Electronique I

And I'll look at this circuit. This circuit, it's an inverter as we studied before whereby the v_L voltage is equal to $-R_2/R_1$ times v_1 . So I can write it here: $v_L = -R_2/R_1$ which multiplies the v_1 voltage. So if v_1 is positive, I will have a current which will leave the amplifier and descend in the charge. Sorry, I was wrong. If v_1 is positive, I will have v_L which is negative. So I will have a current which will go in this direction there. If, however v_1 is negative, v_L will be positive and the current will go in this direction there. And now, we are going to add these diodes and we will do exactly as we did earlier and by analysing the two conditions: once v_1 is positive, and once v_1 is negative.

Notes



Summary



1m 36s

Redresseur inverseur simple-alternance

- $v_1 > 0$, $v_2 = -U_j$, $v_L = 0$

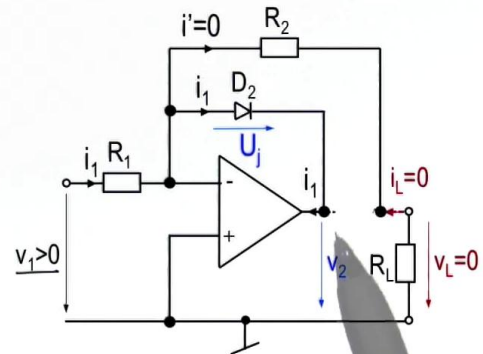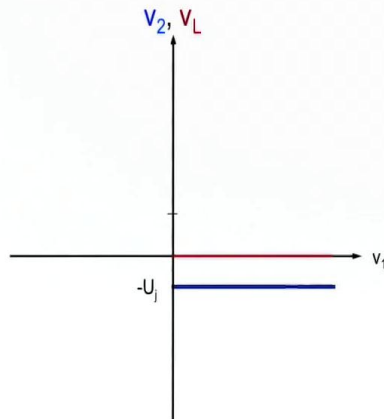

Electronique I

I'll start with the case of v_1 is positive. I'll take my plan, how do we analyse this circuit? To analyse this circuit, you will always reason as if the diodes didn't exist and you will tell yourself that v_1 is positive, v_L should be negative. So there's going to be a current which will go in this direction. And now, we will add the diodes. So we place the condition as if the diodes didn't exist, I'm dealing with an inverter. I place v_1 and I look at v_L and after I add my diodes and I will see how these diodes will behave. So I took v_1 as positive, I expect v_L to be negative because it will be opposite, there is a minus sign. The current will want to pass like that. It comes into this node, this current. There is this diode there. This diode will block its path, it won't let it pass. So it's as if this diode will be removed, and so what I'm going to do straight away, as if D_1 wasn't there. So this D_1 here will disappear and I have this montage. Look at what I have now. This diode is useless. A blocked diode, we can't see it in the plan. So my current which would like to go in there, it can't go. And so, what is happening to this diode?

Notes



Summary



2m 32s

Redresseur inverseur simple-alternance

- $v_1 > 0$, $v_2 = -U_j$, $v_L = 0$

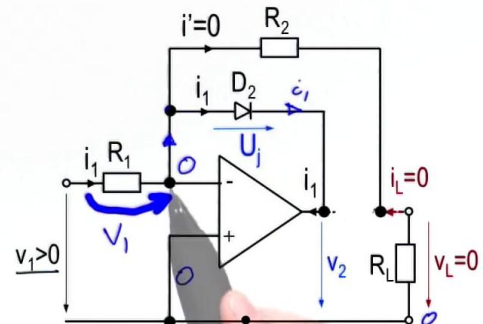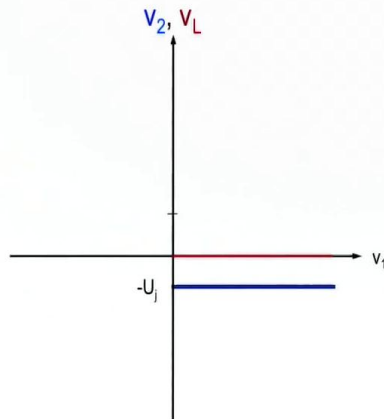

Electronique I

If v_1 is positive and when v_1 is positive, I will have v_1 which, theoretically, will appear there. And there, I will have a v_1 voltage. I have 0V there and the 0V, it's copied by the counter reaction here. And there, you must listen to what happens because we will see that this 0V, which is what I can see here, is copied there. So if this 0V here, and this 0V here, that is the real 0V and that is the virtual 0V, I have no current at all which can't cross this resistance, when this diode is a conductor. Having added this diode there, this diode will have v_1 and i_1 which would like to pass like that. So if i_1 arises here, it comes into this node here. Can i_1 pass through this diode? Yes, the diode is in the right direction. It would be able to let i_1 pass. So the i_1 current will pass through the diode. And if the i_1 current passes via the diode, passes in the amplifier, that's it, we have a counter reaction established. When this counter reaction is established, the potential here is copied here. And there, I have 0V. So having 0V, thanks to this diode there, if this diode hadn't been here, I would have no chance at all of having a copy of this potential towards this potential.

Notes



Summary



3m 55s

Redresseur inverseur simple-alternance

- $v_1 > 0$, $v_2 = -U_j$, $v_L = 0$

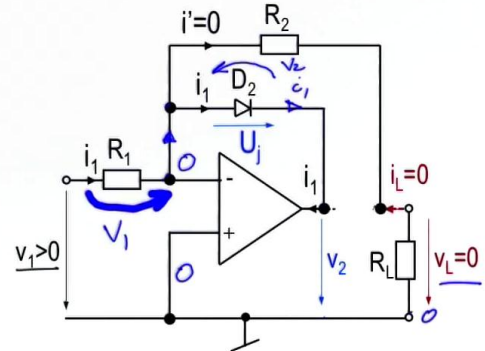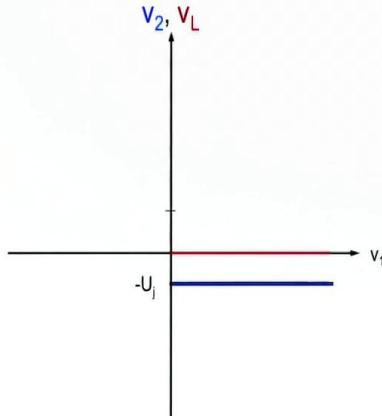

Electronique I

This potential will rely on $R1$, $R2$ and RL and I will have $v1$ which will be on the terminals of these three resistances and that will have a given potential thanks to that. But the diode, when it conducted, created a counter reaction so the amplifier created the virtual mass. So I have 0V there and I have 0V here because 0V from there to there doesn't allow a current to pass through RL and $R2$ which gives me $i' = 0$ and therefore I have zero current. And I have the voltage $vL = 0$. So we've just found straight away that if $v1$ is positive, a diode creates the counter reaction, the other, we can't see it on a plan. And this enables us to have $vL = 0$ and this gives us that. What happens with $v2$? $v2$, is from this node towards the mass. And this potential is the same as this one so $v2$, I have it here. So that is exactly the $v2$ voltage. So $v2$ is equal to a $-Uj$ voltage. When the diode will conduct, it will create a connection voltage that I call Uj . So $v2$, it's from this node here to this node there, on the terminals of the same diode so $v2$ is located at $-Uj$.

Notes



Summary



5m 27s

Redresseur inverseur simple-alternance

- $v_1 > 0$, $v_2 = -U_j$, $v_L = 0$

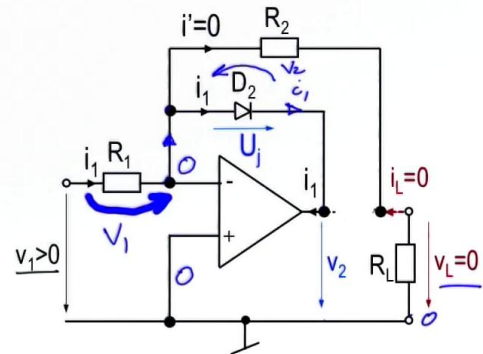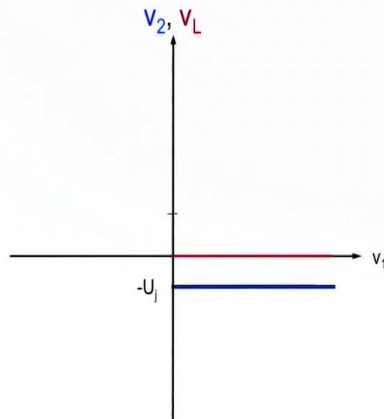

Electronique I

I would just like to insist on that. In the case of a non-inverter rectifying amplifier, that we studied earlier, we found that when the output voltage was zero, we found that v_2 was equal to $-V_{sat}$. There, it's already better. Instead of going towards the saturation voltage which is quite high, to a relatively weak voltage compared to V_{sat} , which is on an order of -0.6 to $-0.7V$ which is a connection voltage.

Notes



Summary



6m 45s

Redresseur inverseur simple-alternance

- $v_1 < 0, v_2 = U_j + v_L, v_L = -\frac{R_2}{R_1} v_1$

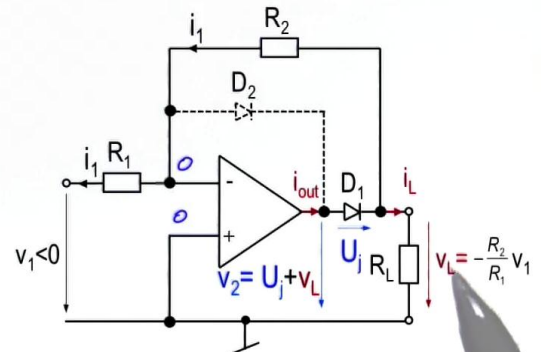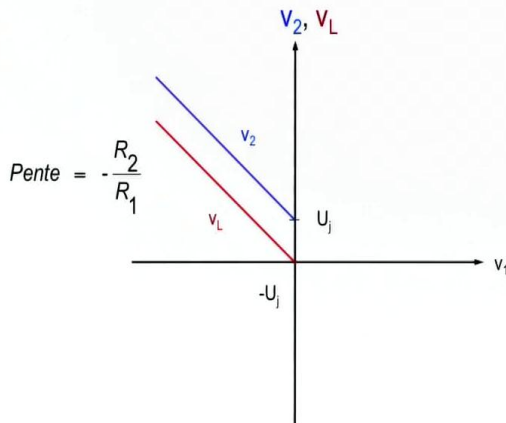

Electronique I

We will now analyse what will happen with the same plan, but taking an alternation for which v_1 is negative. So I'll put v_1 negative. Same logic. If I apply a negative voltage, I reason as if my diodes didn't exist and I would say in an inverter amplifier when v_1 is negative, I will find myself with a v_L positive voltage. So the current will want to come in this direction there. There is a diode. This diode this time is in the right direction of the current flow. So the amplifier which provides the current passes through the diode and continues its path. So the counter reaction is established through the R_2 and R_1 resistances and allows the counter reaction to happen. But what happens with the D_2 diode? The D_2 diode has 0V here, so the counter-reacting amplifier will impose 0V there. And there, the voltage will be positive. So we said v_1 negative, v_L will be positive, so this voltage is quite high. So if this voltage is quite high, this voltage there will also be high compared to zero. So v_2 is positive and higher than zero, so this diode is blocked, so we can remove it. We can imagine that this diode doesn't exist.



Notes

Summary



Redresseur inverseur simple-alternance

- $v_1 < 0, v_2 = U_j + v_L, v_L = -\frac{R_2}{R_1} v_1$

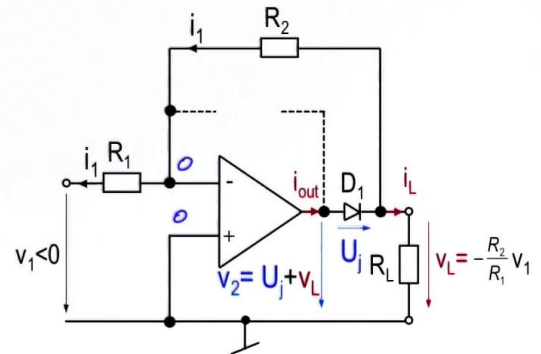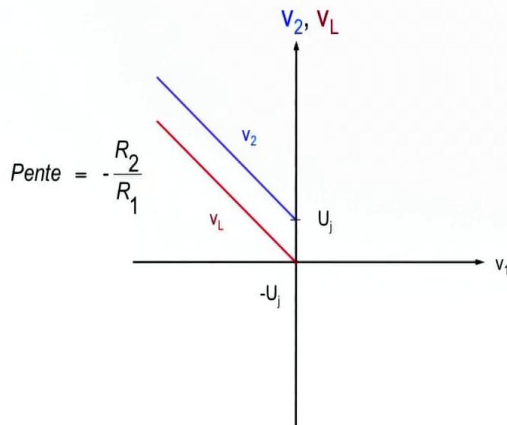

Electronique I

I'll remove it from my circuit and I have a circuit in which there is simply a $D1$ diode which created the counter reaction and the inverter plan, we can also demonstrate like earlier, that adding a serial U_j threshold voltage, if you bring this voltage to the input, you will take U_j divided by the gain of the amplifier which is very, very big, so U_j divided by infinity, there's no real effect of U_j if the gain is very, very big. In this case, in this type of plan, we can clearly see that the amplifier becomes an inverter amplifier, as we know, as usual, which will take a v_L voltage and which will multiply by a constant $-R_2/R_1$ multiplied by v_1 , which is what we expect from an inverter amplifier and which will give us a slope which, for a negative voltage, makes it positive. It multiplies it by a R_2/R_1 value. And that's it, we have this famous relation that the negative voltage v_1 would be multiplied by a minus sign so it becomes positive again, multiplied by a constant R_2/R_1 . And the v_2 voltage is always behind compared to the v_1 voltage of a quantity which is equal to this U_j voltage.



Notes

Summary



8m 40s

Redresseur inverseur simple-alternance

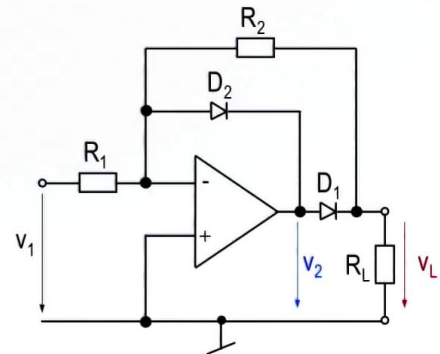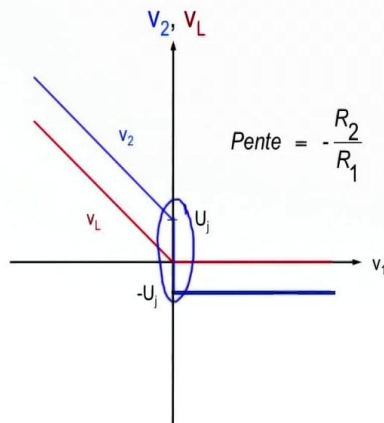

Electronique I



So this U_j voltage is always the voltage that we will see between these two curves. So we have two curves following each other, with a U_j voltage between v_L and v_2 , and we can clearly see that here. And to finish, here is our complete plan with the two diodes, with the characteristics that we analysed earlier. It's a non-linear function. When the voltage is positive, the output is zero and when the voltage is negative, the output becomes positive. And we have this type of plan. There is a big advantage, it's that the v_2 voltage will never look for a saturation voltage, so a high voltage. So we are less irritated by the *slew rate* of the amplifier because the variation of v_2 , when we pass from a positive voltage, when the v_1 voltage passes through zero, we see a variation in size order from 1.2 to 1.4V because it's equal to two times U_j , contrary to what we saw earlier which was 15V plus 0.7V. So the difference is clearly minimal and the impact on the output voltage of a limitation of the amplifier, which is the *slew rate*, is lower. So we always wish, as much as possible, to appeal to this type of montage rather than the alternating simple rectifier when the output is positive, we prefer to use this montage to take advantage of this effect that we've just discussed.

Notes

Summary



TP: Redresseur inverseur simple-alternance

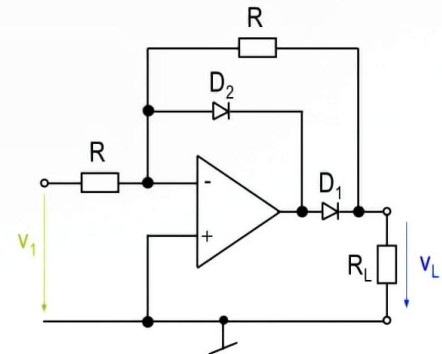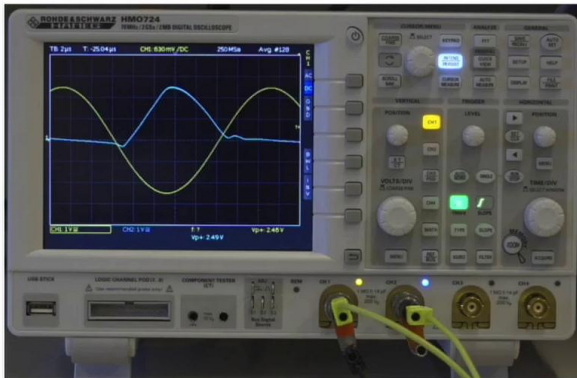

Electronique I

Here is our input voltage which is in yellow and certainly, we will see the rectified voltage at the output, i.e. the positive alternation will give us a zero, however, our negative alternation will be rectified and that is what we can see now on this oscilloscope. I would really like, at this stage, to illustrate what will happen with this type of amplifier when it passes through zero and see what problems will occur, linked to the *slew rate*. So remember that an operational amplifier suffers from an imperfection when we have a voltage deviation at the output and with this voltage deviation, when it has to do be done quickly, there is a phenomenon called the *slew rate*, as it's called in English. And this voltage deviation limits the voltage variation at the output that we can see there. So you see the blue curve. When the voltage in yellow passes through zero, of course, this diode there, is the one that was conducting, the amplifier is counter reacted by the two resistances, but when it passes through zero, it will rectify the voltage and it will pass from $-U_j$ to $+U_j$ and we can see this phenomenon here.



Notes

Summary



11m 29s

TP: Redresseur inverseur simple-alternance

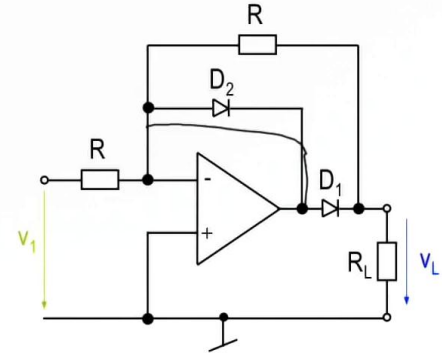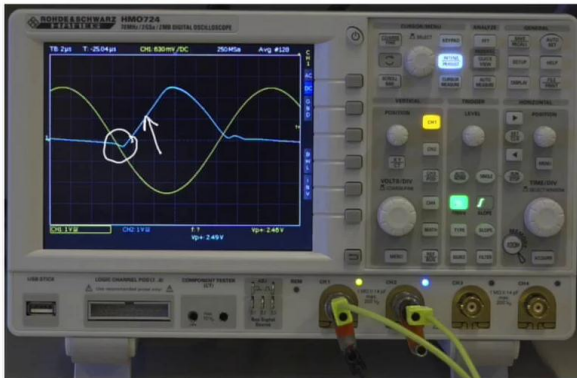

Electronique I



This phenomenon shows us that there's a small change and then, we have this slope and this slope isn't exactly a sinusoidal voltage. It's the tangent slope to the passing through zero of a sinusoidal voltage because the amplifier will take time to follow $-U_j$ to U_j and it will affect the linearity of the rectified voltage at the output. And to solve that, as we saw when we studied the chapter on imperfections, you can lower the voltage and have fewer deviations. There is another phenomenon that I would like to comment on, it's what happens when this diode there will conduct. So this diode here will conduct, it will make a counter reaction. So it will rejoin the current which will pass directly by a counter reaction through the diode by having a drop in U_j voltage in this direction there. That means that at the moment when this diode will conduct, the amplifier will act like a voltage follower it has a plus here, it will place it there, the zero, it will place it here and we would have a follower. And the voltage follower corresponds exactly to what happens there. The amplifier is counter reacted by the D_2 diode.

Notes

Summary



TP: Redresseur inverseur simple-alternance

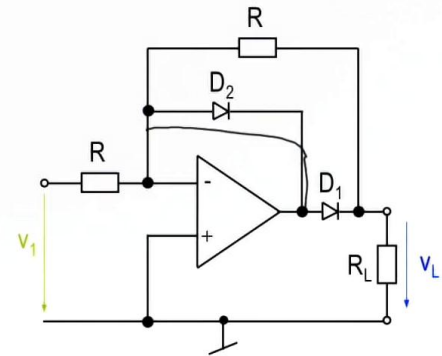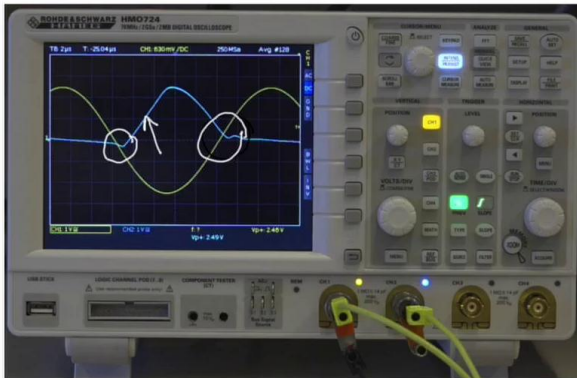

Electronique I

And rightly, when it arrives there, when it arrives here, the amplifier is changing the type of counter reaction. At the start, it was counter reacted by this $D1$ diode. And then, it is counter reacted by the $D2$ diode. And we can see small oscillations that appear here because this amplifier can't quickly follow this passage from one diode to the other and it will take a certain amount of time to counter react and we can see it here by an oscillation which is quite common for these components. To resolve this and to have fewer oscillations which appear here, you need to increase the amplifier's gain and the amplifier's bandwidth, if possible. And that's it, with that, we were able to see that using an active amplifier, which has stability rules that aren't yet studied at this level in electronics, we would still have a rectified voltage which can sometimes suffer from the amplifier's imperfections. And it was the right moment to mention them. And what we've just seen with this amplifier by using the two diodes is much more drastic and has a much more limiting effect when the amplifier is non-inverting.



Notes

Summary

14m 05s



TP: Redresseur inverseur simple-alternance

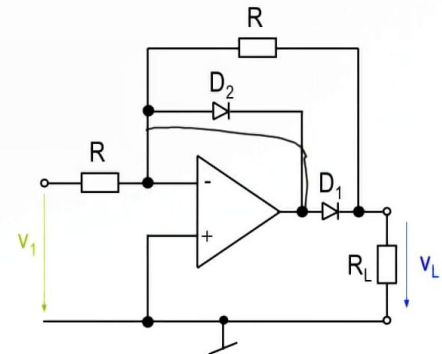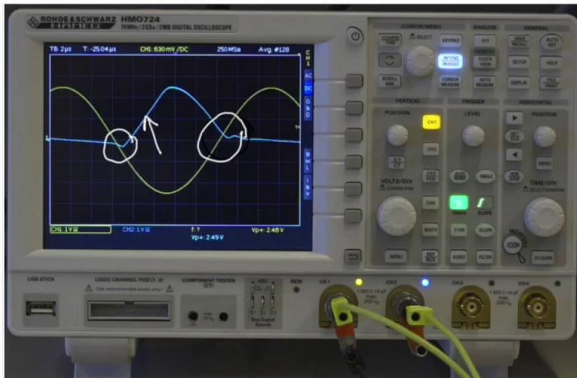

Electronique I

I understand that the montage that we studied at the start, where it's a non-inverting rectifier, this type of phenomenon is much more drastic and strongly limits using this amplifier with applications that have very, very weak frequency and the output voltage deviation is extremely weak, especially when passing through zero. I remind you that when the rectifier is non-inverting, the output voltage of the amplifier has to leave from $-V_{sat}$ to $+U_j$. And there, we already see this phenomenon when it leaves from $-U_j$ to $+U_j$ so in size order from 1.4V, and in the case of the non-inverter, there's a lot of voltage which passes and the *slew rate* sometimes has to change from voltages like -15V to 0.7V, which is enormous.

Notes

Summary

